

ECD - HW 4

① a) Assume F.A., for 'Thv. Conversion':

$$V_{TH} = V_{CC} \cdot \frac{R_2}{R_1 + R_2} = 5 \cdot \frac{22k}{(22+33)k} = 2V, \quad R_m \cdot R_1 // R_2 = 22k // 33k = \underline{\underline{13.2k}}$$

$$\Rightarrow i_B = \frac{V_{TH} - V_{BE(\text{on})}}{R_m + (\rho_H | R_S)} = \frac{2 - 0.7}{13.2 + (10)(3)} = 4.11 \mu A$$


$$\Rightarrow i_C = \beta i_B = 0.41 \text{ mA}, \quad i_E = i_C + i_B = 0.415 \text{ mA}$$

$$\text{Check: } V_C = V_{CC} - i_C R_C = 5 - (0.41)(4) = 3.36V \quad \left\{ \begin{array}{l} V_{CE} = V_C - V_E = 2.115V \\ \text{m F.A.} \end{array} \right.$$

$$(i_C, V_{CE}) = (0.41 \text{ mA}, 2.115V)$$

$$r_\pi = \frac{V_T}{i_B} = \frac{26 \text{ mV}}{4.11 \mu A} = 6.33 \text{ k}\Omega, \quad g_m = \frac{\beta}{r_\pi} = 15.81 \text{ mA/V}$$

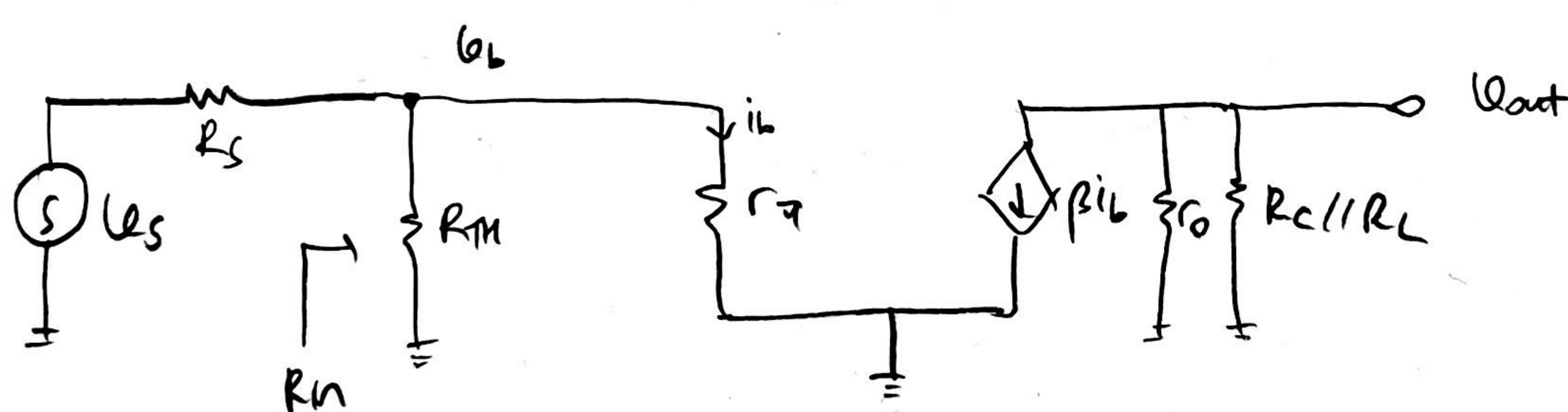b) S.S model in midband (short the caps.):



$$R_{in} = R_m // r_\pi = 13.2k // 6.33k = 4.28 \text{ k}\Omega$$

$$U_b = \frac{R_{in}}{R_m + R_n} U_s, \quad i_b = \frac{U_b}{r_\pi}, \quad U_{out} = -\beta i_b (r_o // R_C // R_L)$$

$$\Rightarrow A_o = \frac{U_{out}}{U_s} = -\frac{\beta (r_o // R_C // R_L)}{r_\pi} \cdot \frac{R_{in}}{R_{in} + R_S}$$

$$= -100 \left(200k // 4k // 5k \right) \cdot \frac{4.28k}{4.28k + 4k} \approx -17.95 \frac{V}{V}$$


$$c) f_T = 700 \text{ MHz}, C_\mu = 1 \text{ pF} \Rightarrow f_T = \frac{g_m}{2\pi(C_\mu + C_\pi)} \Rightarrow 700 \text{ MHz} = \frac{15.81 \text{ mA/V}}{2\pi(1 \text{ pF} + C_\pi)}$$

$$\Rightarrow C_\pi = 2.59 \text{ pF}$$


Using Miller effect, split C_μ as $(1+A)C_\mu, (1+\frac{1}{A})C_\mu$.
 A is the gain between the base and collector $\Rightarrow -A = \frac{U_{out}}{U_b}$

$$A = -34.72 \Leftrightarrow = -\frac{\beta(r_o \parallel R_C \parallel R_L)}{r_\pi}$$

Redraw the circuit:

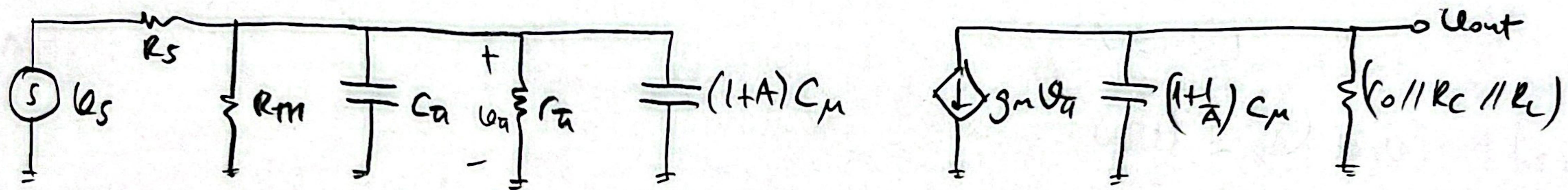


At the input:

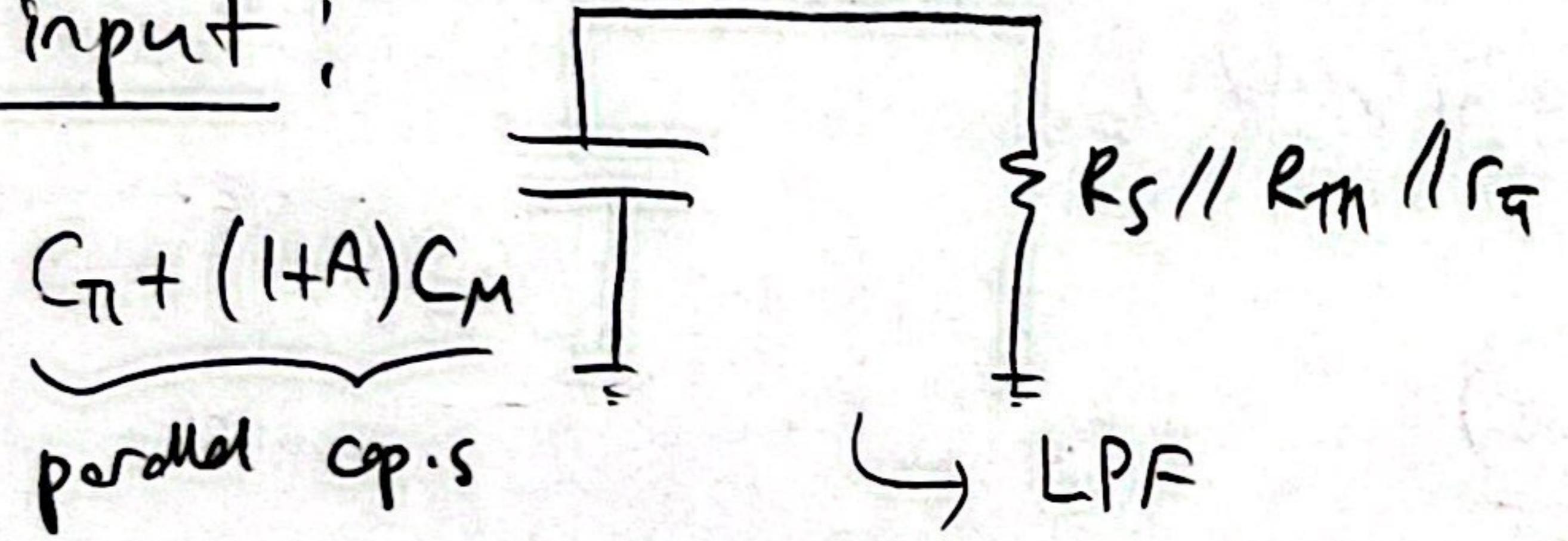

$$\begin{aligned} Z_1 &= (C_\pi + (1+A)C_\mu) \underbrace{(R_s \parallel R_m \parallel r_a)}_{\text{parallel cap.s}} \\ &= (2.59 \text{ pF} + 35.72 \text{ pF})(2.067 \text{ k}\Omega) \\ &= 7.92 \times 10^{-8} \text{ sec.} \end{aligned}$$

At the output:

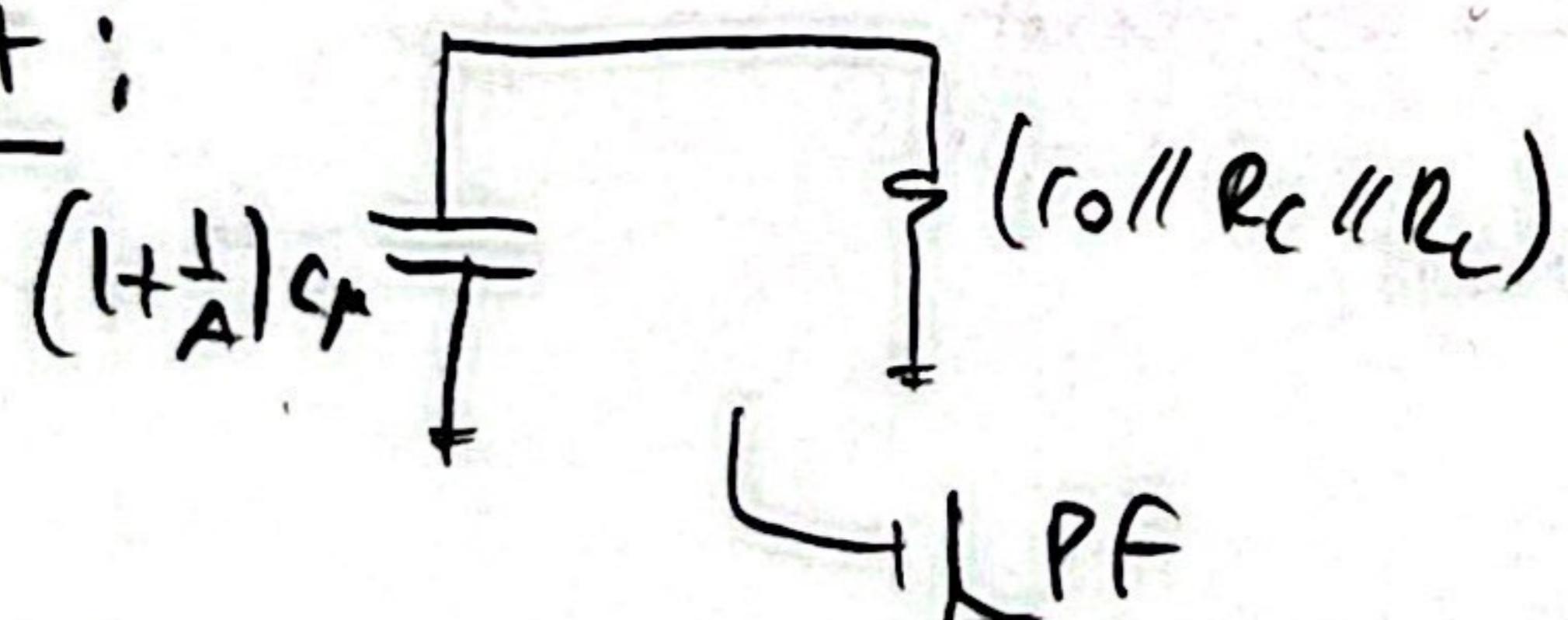

$$\begin{aligned} Z_2 &= ((1+\frac{1}{A})C_\mu)(r_o \parallel R_C \parallel R_L) \\ &= 2.26 \times 10^{-9} \text{ sec} \end{aligned}$$

$$\Rightarrow f_1 = \frac{1}{2\pi Z_1} = 2.01 \text{ MHz}, f_2 = \frac{1}{2\pi Z_2} = 70.42 \text{ MHz}$$

Pick the smaller
 upper cut-off frequency
 f_H as it
 drives

$$\Rightarrow A(j\omega) = -17.95 \left(\frac{1}{1+j\frac{\omega}{f_1}} \right) \left(\frac{1}{1+j\frac{\omega}{f_2}} \right)$$

high freq. response

$$= -17.95 \left(\frac{1}{1+j\frac{\omega}{\omega_1}} \right) \left(\frac{1}{1+j\frac{\omega}{\omega_2}} \right)$$

2) a) Assume SAT: $V_{GS} = V_G - V_S = 5 - 10 I_D$

$$\Rightarrow I_D = k_n (V_{GS} - V_{th})^2 \Rightarrow I_D = 2(4 - 10 I_D)^2$$

$$I_D = 0.36 \text{ mA} \quad \text{or} \quad I_D = 0.45 \text{ mA}$$


into have it ON

$$V_{DS} = 10 - I_D(S + I_0) = 10 - 15(0.36) = 4.6 \text{ V} > \frac{V_{GS} - V_{TN}}{0.4 \mu\text{V}}$$

in SAT

$$V_{GS} = S - 10 I_D = 1.4 \text{ V}$$
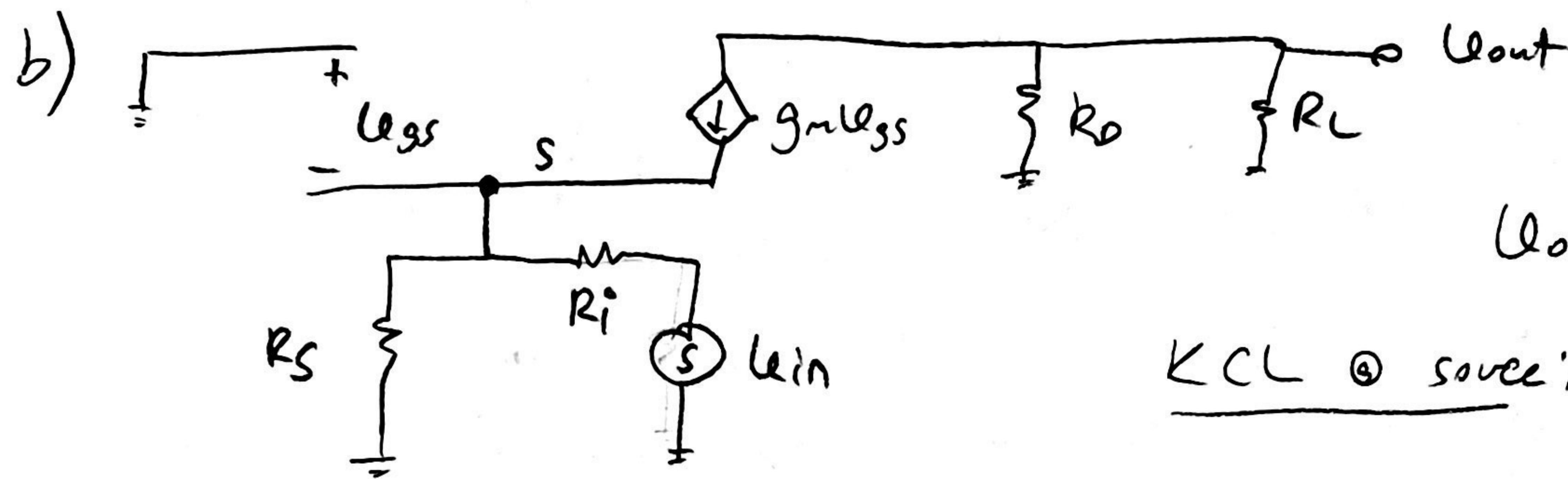
$$\Rightarrow (I_D, V_{DS}) = (0.36 \text{ mA}, 4.6 \text{ V})$$



$$(V_{out} = -g_m V_{gs} (R_D // R_L))$$

$$\text{KCL at source: } \frac{V_{gs}}{R_s} + \frac{V_{gs} - V_{in}}{R_i} - g_m V_{gs} = 0$$

$$\text{and } V_{gs} = -V_{in} \Rightarrow V_{in} = R_i (V_{gs} \left(g_m + \frac{1}{R_s} + \frac{1}{R_i} \right))$$

$$(V_{out} = g_m V_{gs} (R_D // R_L))$$


$$\Rightarrow A_o = \frac{V_{out}}{V_{in}} = \frac{g_m (R_D // R_L)}{R_i \left(g_m + \frac{1}{R_s} \right) + 1} = g_m (R_D // R_L) \frac{\left(R_s // \frac{1}{g_m} \right)}{(R_i + (R_s // \frac{1}{g_m}))}$$

$$= 0.82 \frac{\text{V}}{\text{V}}$$

$$g_m = 2 \sqrt{k_n I_D}$$

$$= 2 \sqrt{2 \cdot 0.36} = 1.8 \text{ mA/V}$$

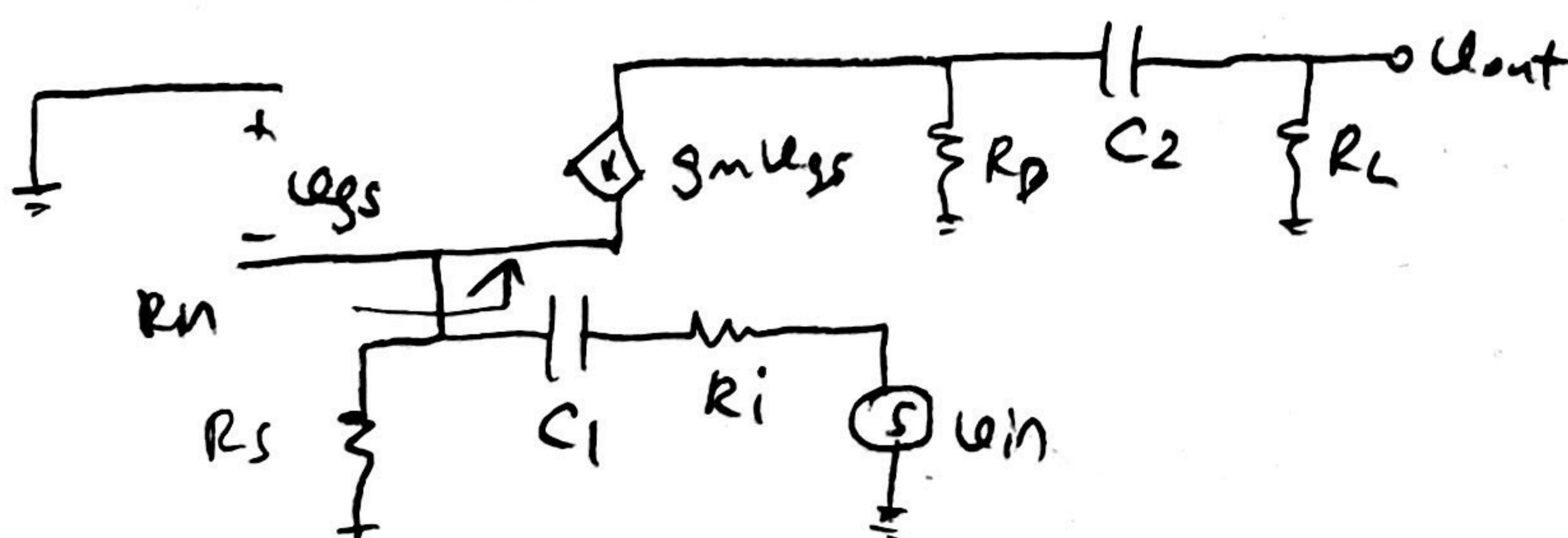c) At lower frequencies, C_{gs} and C_{gd} are open circuited.




At input:

$$R_{in} = \frac{1}{g_m}$$

$$C_1 = C_1 \left(\left(R_s // \frac{1}{g_m} \right) + R_i \right) = 2.55 \text{ ms}$$

$$f_L = \frac{1}{2\pi C_1} = 62.28 \text{ Hz}$$

At output:

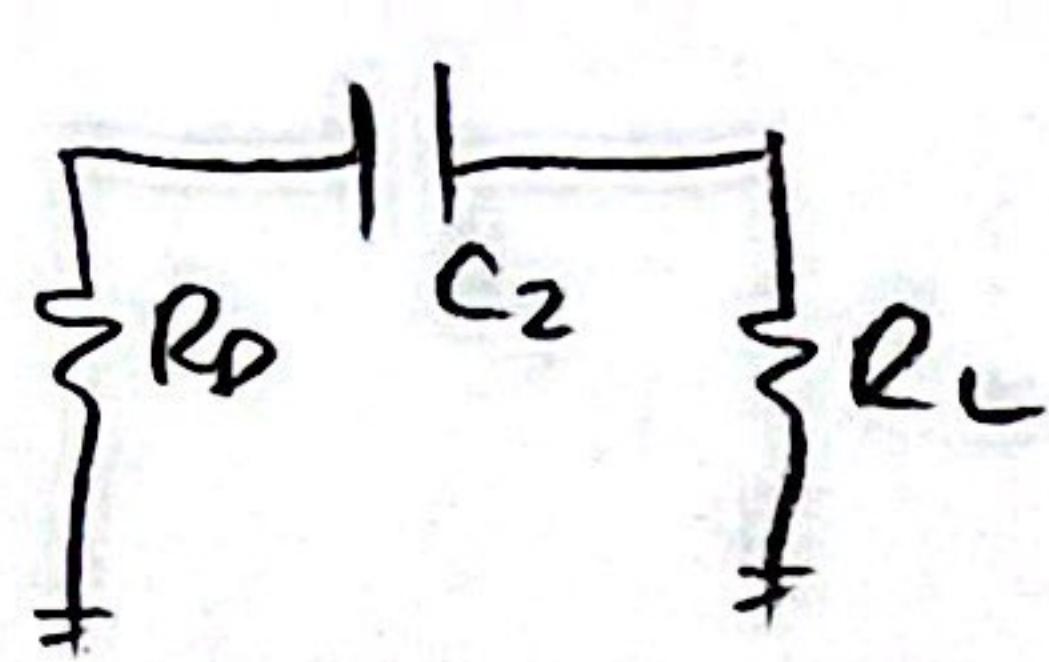


$$Z_2 = C_2 (R_D + R_L) = 18 \text{ ms}$$

$$\omega_{L2} = \frac{1}{2\pi Z_2} = 8.842 \text{ Hz}$$

For ω_L , pick the bigger one since it determines the bandwidth:



$$\omega_L = 62.28 \text{ Hz}$$

$\uparrow A(j\omega)$

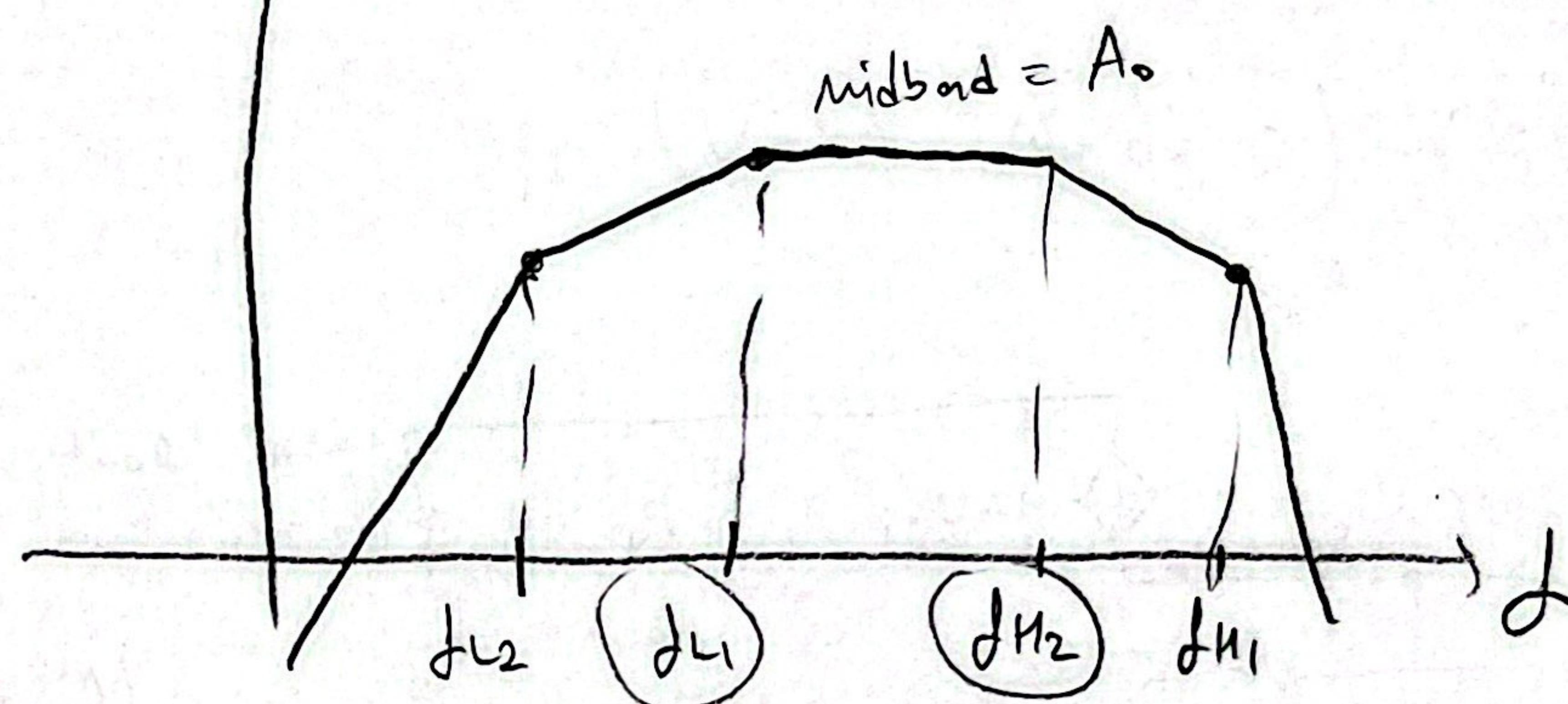

d) At high frequency, assume C_1, C_2 short circ. Note that since gate is grounded, C_{gs} is in between the source and ground, and C_{gd} is between drain and ground.

At input:

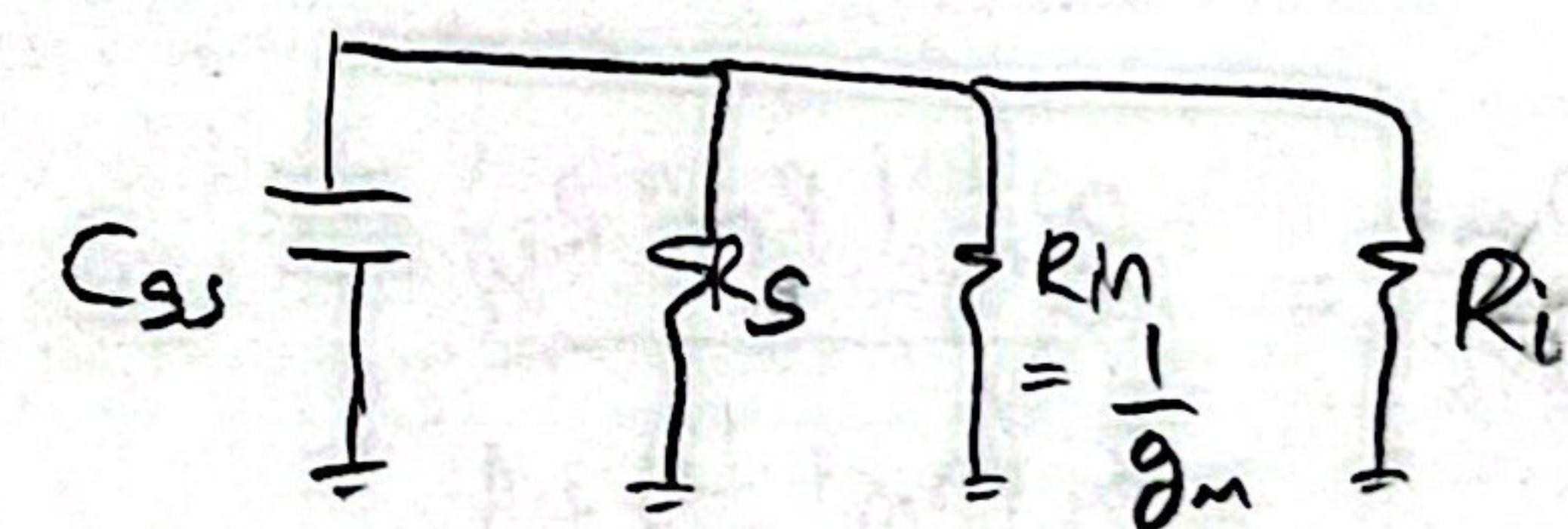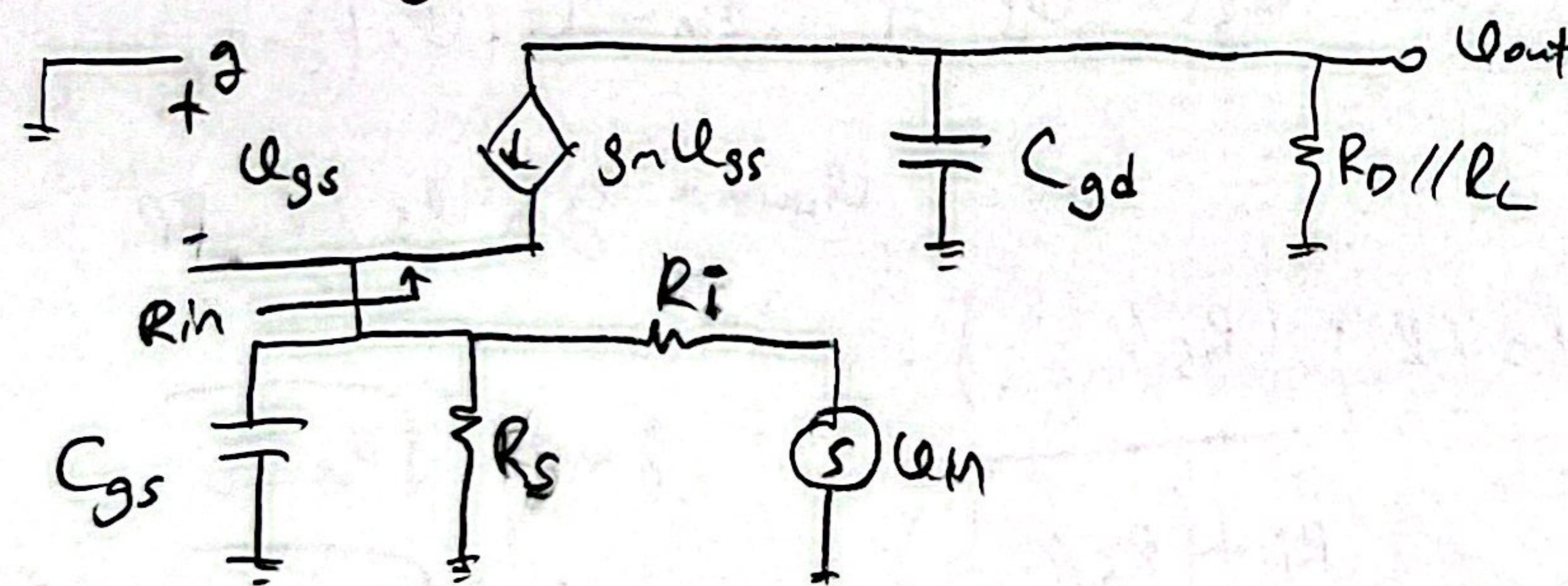


$$\Rightarrow Z_1 = C_{gs} (R_s // R_i // \frac{1}{g_m})$$

$$= 5.22 \times 10^{-9} \text{ sec}$$

$$\Rightarrow \omega_{H1} = \frac{1}{2\pi Z_1} = 30.49 \text{ MHz}$$

At output:

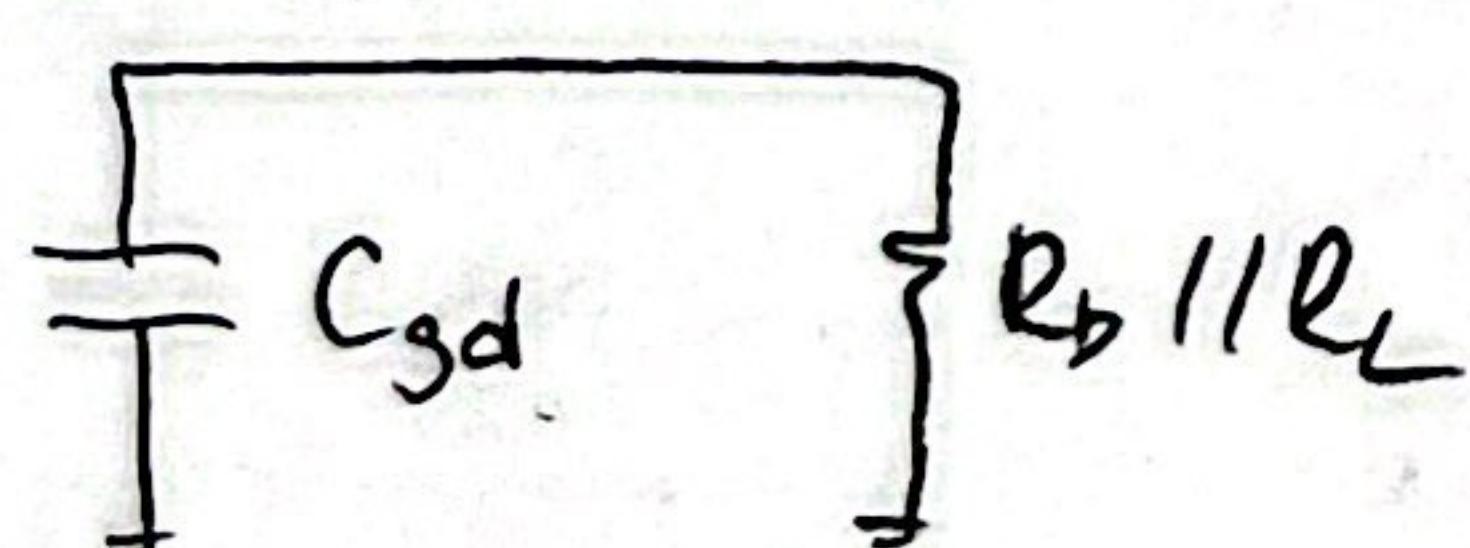



$$Z_2 = C_{sd} (R_D // R_L)$$

$$= 6.66 \times 10^{-9} \text{ sec}$$

$$\Rightarrow \omega_{H2} = \frac{1}{2\pi Z_2} = 23.9 \text{ MHz}$$

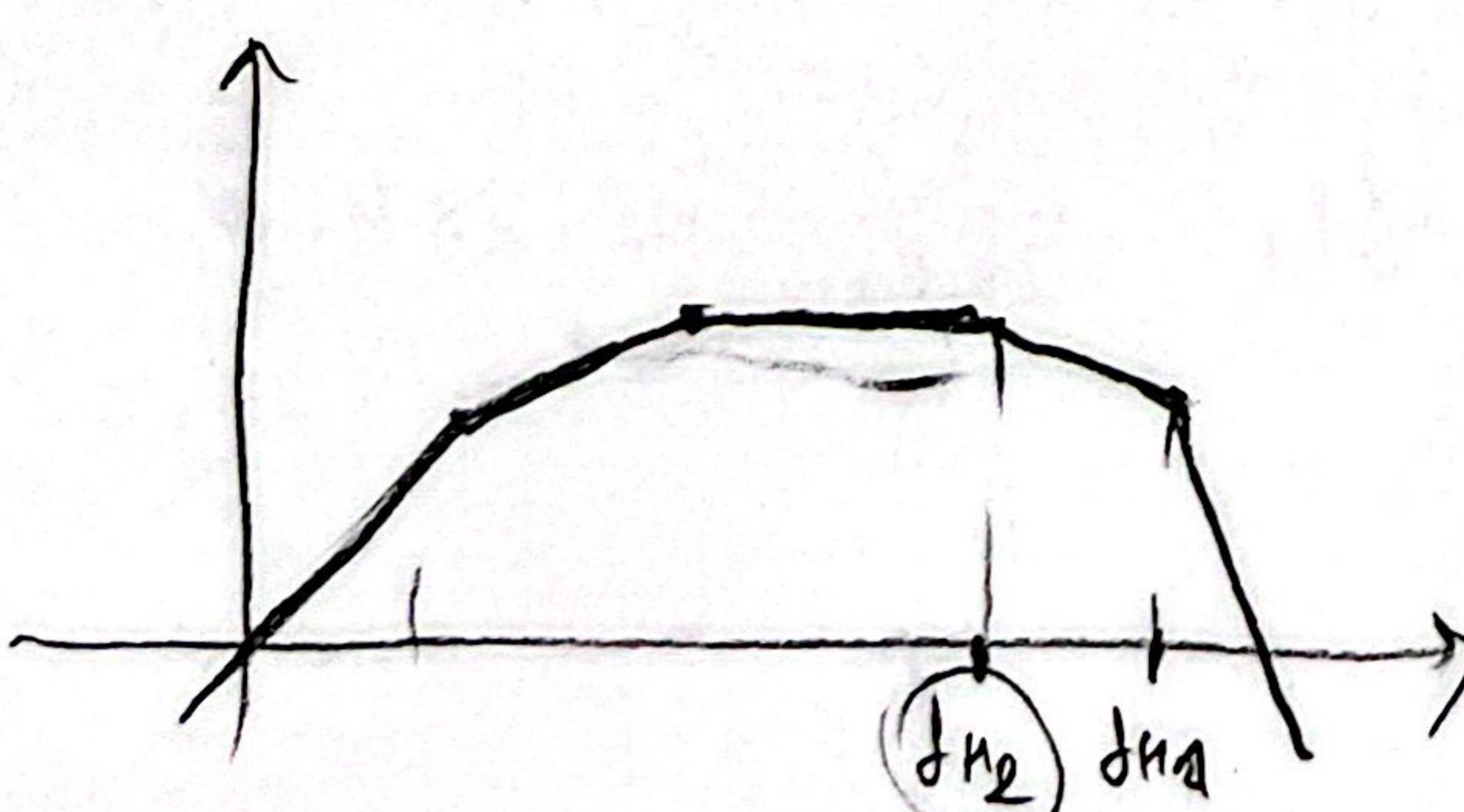
Pick the smaller one for ω_H : $\omega_H = 23.9 \text{ MHz}$



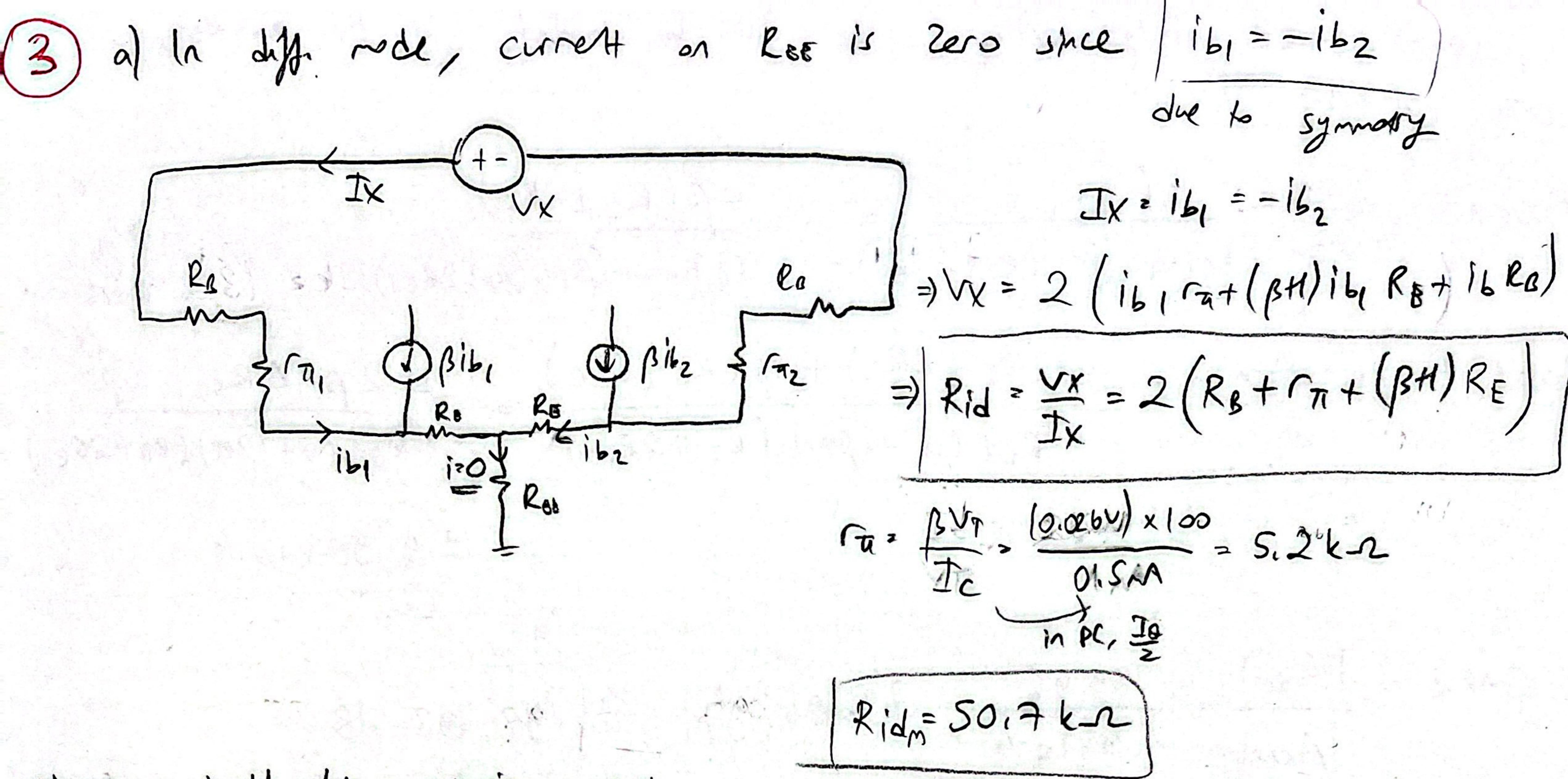

b) Use half ckt. analysis, omit R_{BE} since no current on it in diff mode.

For O_1 :

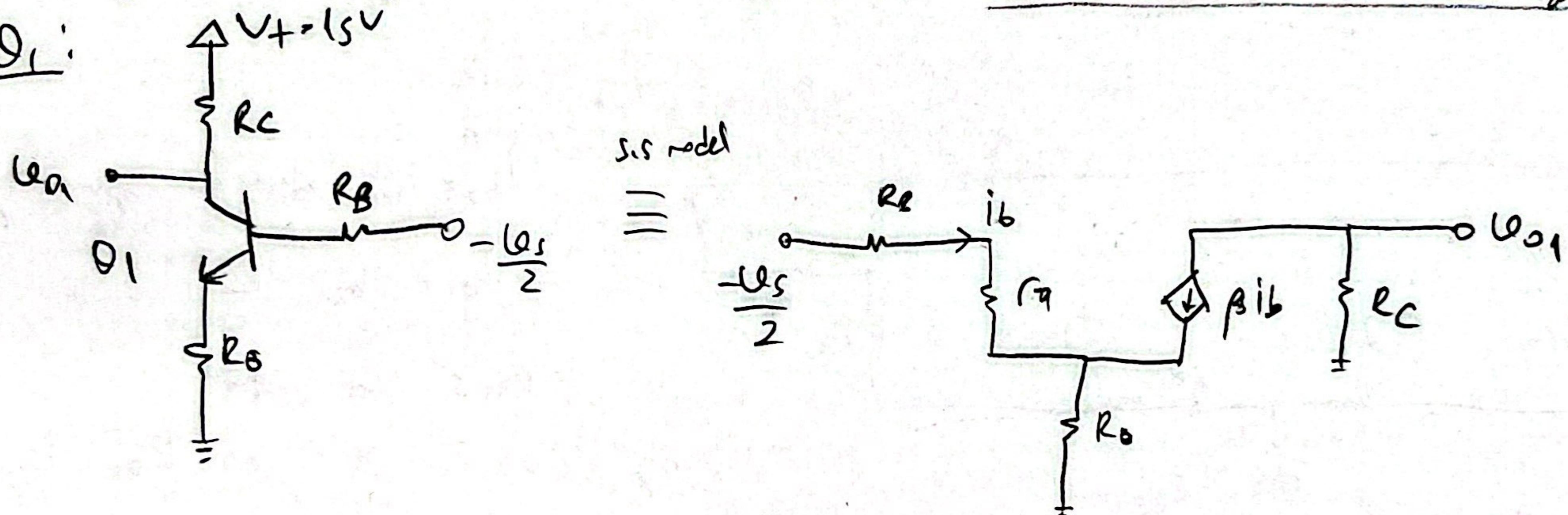

Due to symmetry:

$$A_{dm} = A_{dm1} - \underbrace{A_{dm0}}_{\substack{\text{same input} \\ \text{but negative} \\ \text{of } A_{dm1}}}$$

$$\left. \begin{array}{l} V_{o1} = -\beta i_b R_C \\ -\frac{Us}{2} = i_b (R_E + r_a + (\beta+1)R_S) \end{array} \right\} \Rightarrow A_{dm1} = \frac{V_{o1}}{\frac{Us}{2}} = \frac{\beta R_C}{2(R_E + r_a + (\beta+1)R_S)}$$

$$= 2 \frac{\beta R_C}{2(R_E + r_a + (\beta+1)R_S)}$$

$$\Rightarrow A_{dm} = \frac{V_{out}}{Us} = \frac{\beta R_C}{R_E + r_a + (\beta+1)R_E}$$

$$= 39.45 \frac{V}{V}$$

If R_C accurate to $\pm 1\%$

$$\Rightarrow \Delta R_C = 0.1k\Omega$$

$$A_{dm}' = A_{dm} - \frac{A_{dm0}}{R_C} = \frac{\beta(R_C \pm \Delta R_C) + \beta(R_C + \Delta R_C)}{2(R_E + r_a + (\beta+1)R_S)}$$

$$= \frac{\beta R_C}{R_E + r_a + (\beta+1)R_S} = A_{dm} \quad \begin{matrix} \text{(still ne)} \\ \text{some} \end{matrix}$$

c) In common node, half det., $2R_{BB}$ will be added to the emitter, hence plugging in:


$$A_{CM,1} = \frac{V_{out,1}}{V_{CM}} = \frac{-\beta \tilde{R}_C}{R_B + r_a + (\beta+1)(R_E + 2R_{EE})} = \frac{-\beta (R_C + \Delta R_C)}{R_B + r_a + (\beta+1)(R_E + 2R_{EE})} = A_{CM,1} \approx 4.95 \times 10^{-4}$$

$$A_{CM} = A_{CM,1} - A_{CM,0} = \frac{-\beta (R_C + \Delta R_C) + \beta (R_C - \Delta R_C)}{R_B + r_a + (\beta+1)(R_E + 2R_{EE})} = \frac{\pm 2\beta \cdot (\Delta R_C)}{R_B + r_a + (\beta+1)(R_E + 2R_{EE})} = \pm 4.95 \times 10^{-4}$$

only
 $\pm \Delta R_C \neq \Delta R_C$
due to symmetry,
so are opposite

d) CMRR = $\frac{|A_{CM}|}{|A_{CM}|} = \frac{39.45}{4.95 \times 10^{-4}} = 79696.977 \approx 98.03 \text{ dB}$

e)

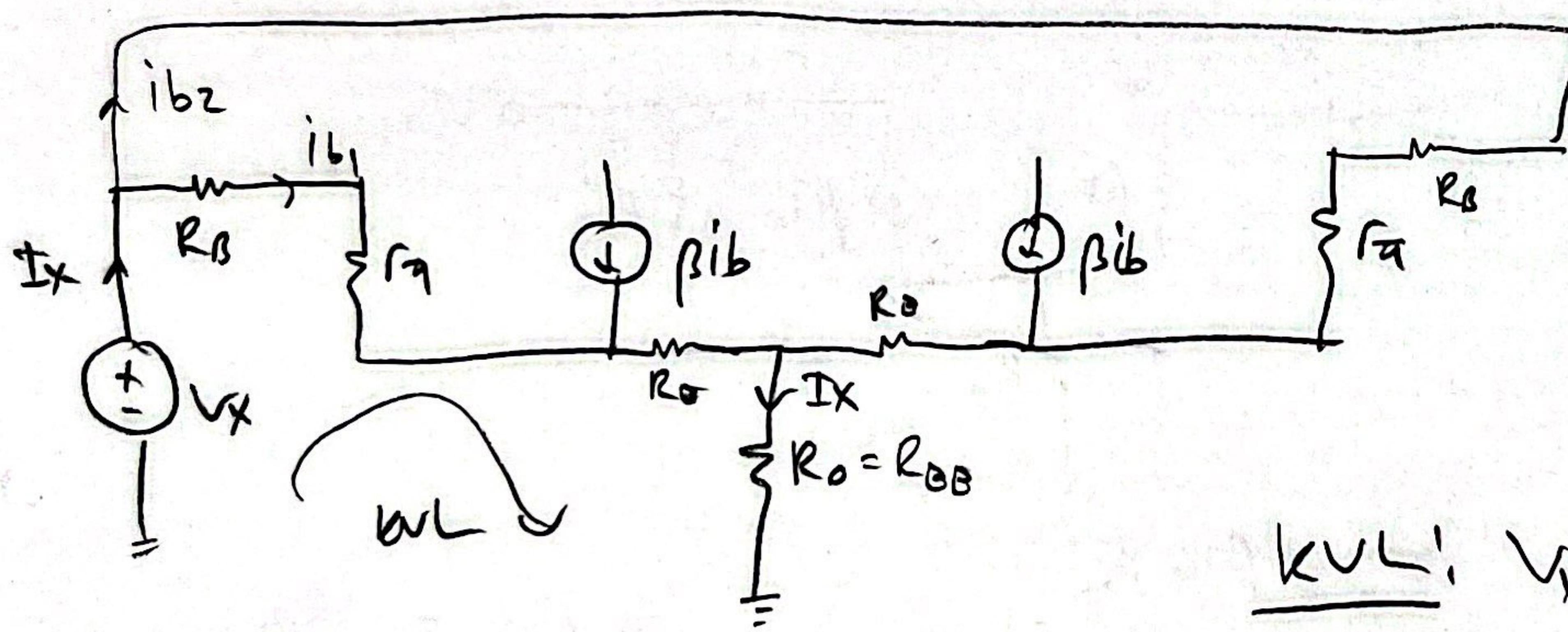

$i_{b2} = i_{b1}$ due to symmetry

$$\Rightarrow i_{b1} = i_{b2} = \frac{I_x}{2}$$

r_a 's are equal

by KCL, current on R_{EE} is I_x

$$\text{KVL: } V_x = \frac{I_x}{2} (R_B + r_a) + (\beta+1) \frac{I_x}{2} R_E + (\beta+1) I_x R_{EE}$$


$$\Rightarrow R_{CM} = \frac{V_x}{I_x} = \frac{R_B + r_a + (\beta+1) R_E}{2} + (\beta+1) R_{EE}$$

$$= 20.21 \text{ M}\Omega \quad \text{very large!}$$

④ DC biasing is the same \rightarrow Currents are proportional wrt k_n 's
and $k_{n2} = 2k_{n1}$ (since $(\frac{w}{l})_2 = 2(\frac{w}{l})_1$)

$$\Rightarrow I_{D2} = 2I_{D1} \text{ and } g_{m1} = 2\sqrt{k_{n1}I_{D1}} \Rightarrow g_{m2} = 2\sqrt{(2k_{n1})(2I_{D1})} = 2g_{m1}$$

in S.S.:

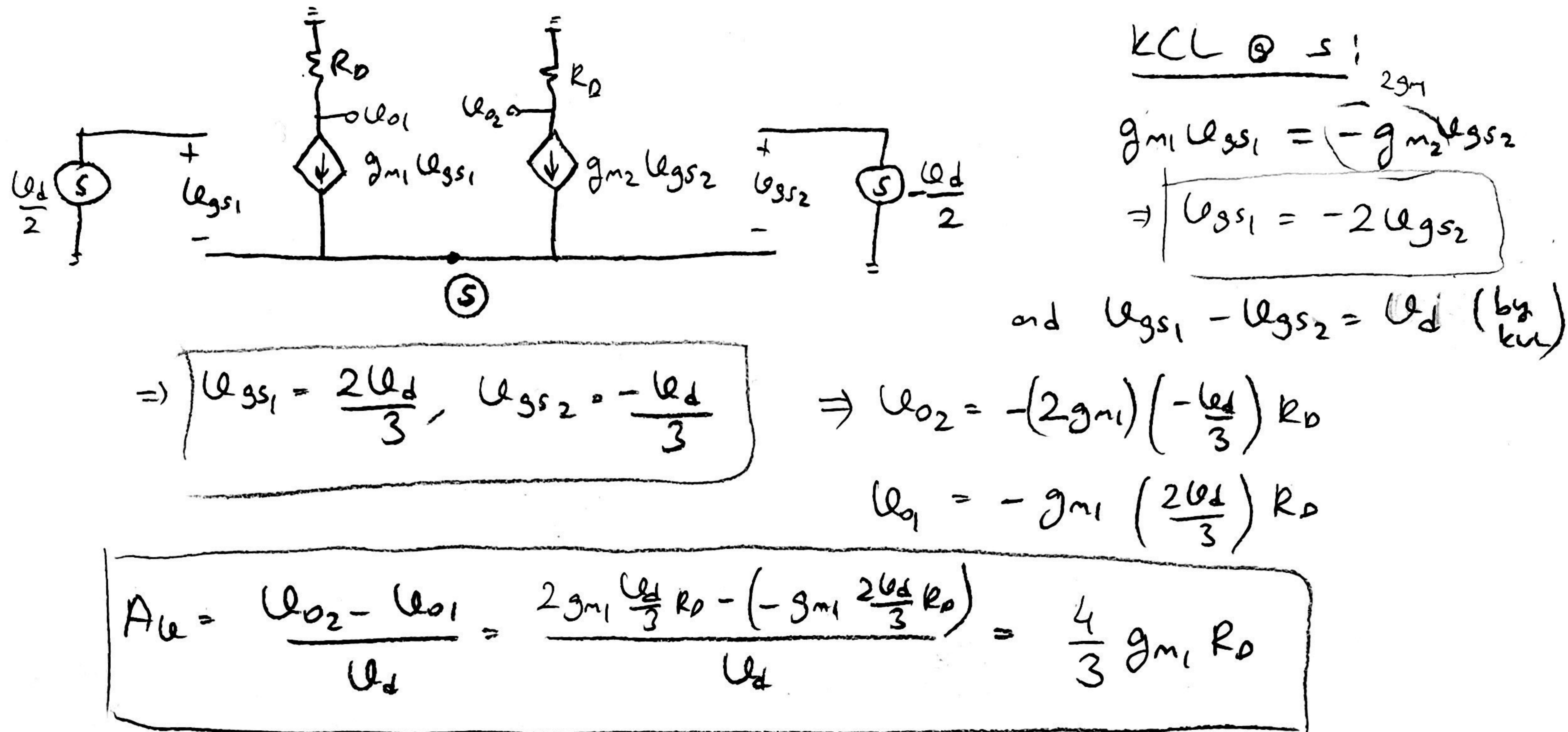

⑤ a) Assume M_1 SAT: $V_{GS1} = 3V \Rightarrow I_D = k_n(V_{GS} - V_{th})^2 = 0.5(3-1)^2 = 2mA$

$$\Rightarrow I_{C1} = I_{C2} \approx I_{D1} = I_{D2} = 1mA$$

As V_{cm} decreases: $V_{E1,2} \downarrow$ to keep V_{BS} constant, hence $V_{D1} \downarrow$, $V_{DS1} \downarrow$
so M_1 may move out of SAT.

We need $V_{DS1} > V_{GS1} - V_{th} \Rightarrow (V_{cm} - \underbrace{0.7}_{V_{BS}(\text{on})}) > 3 - 1 \Rightarrow V_{cm} > 2.7V$


As V_{cm} increases: $V_{B1,2} \uparrow$ so that B-C diode may be turned on,
and Q_1, Q_2 may move into SAT

We need $V_{CE} > V_{CO(\text{SAT})} \Rightarrow (10 - \underbrace{\frac{I_C R_C}{1mA}}_{0.2}) - (V_{cm} - 0.7) > 0.2$
 $\Rightarrow 6.7 - V_{cm} > 0.2 \Rightarrow 6.5 < V_{cm}$

Hence, we need

$$6.5V > V_{cm} > 2.7V$$

b) In S.S.:

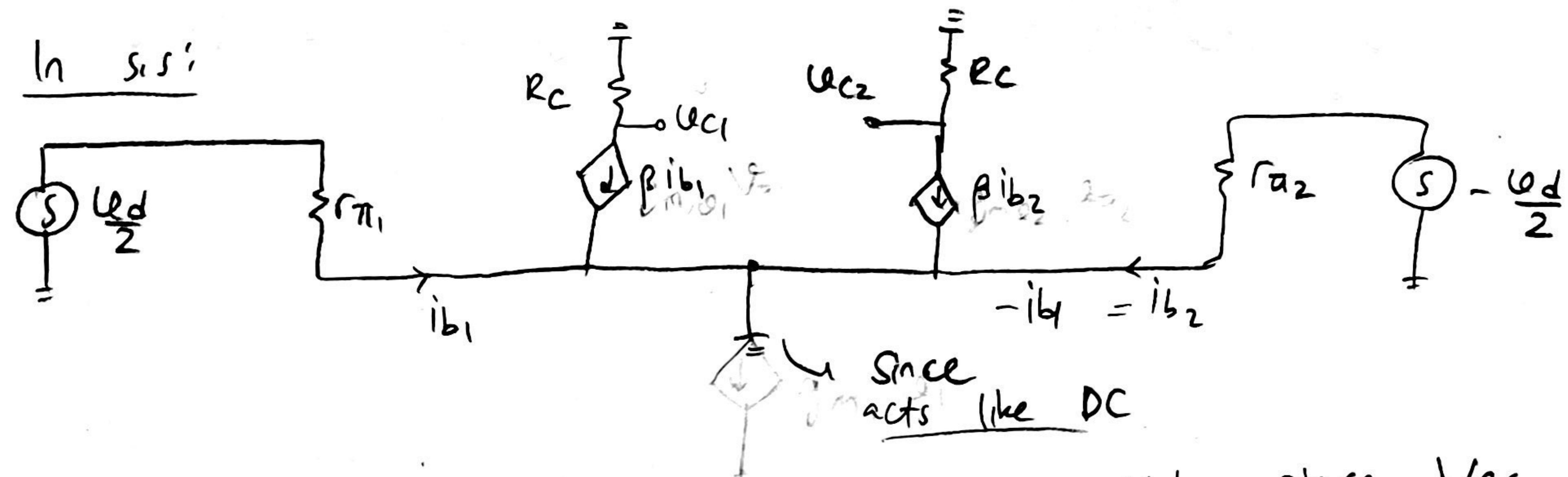


In DC, we have a varying current on M1 since V_{GS} is varying. This causes a change in I_C 's of the BJT's \Rightarrow change in g_m 's.

$$g_m = \frac{I_C}{V_T} + \frac{\Delta I_C}{V_T}$$

Coming from 2V bias

Coming from U_1

Since U_1 is S.S., the model of M1:

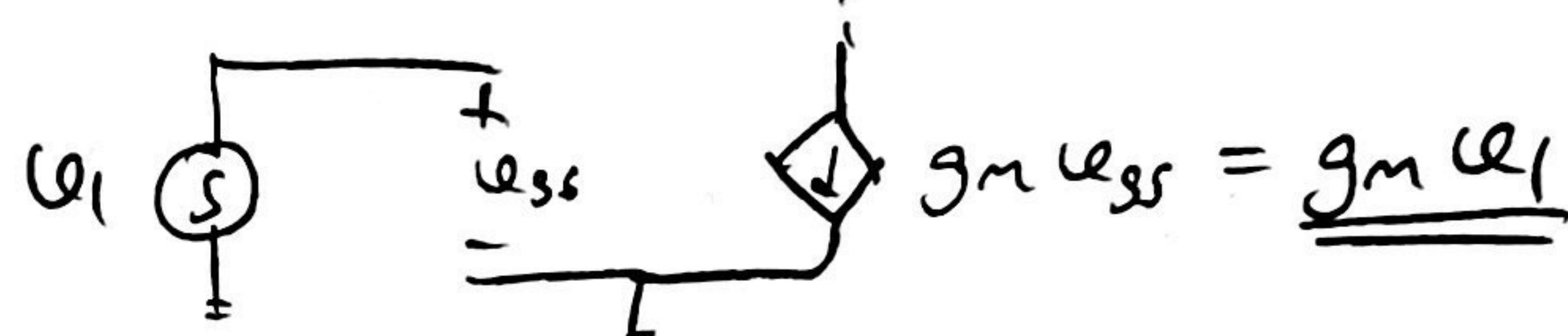

This means that the sum of I_C 's of Q1 and Q2 should be

$$I_{C1} + I_{C2} = I_D + \frac{I_d}{2} = 2mA + g_m U_1 \Rightarrow \left| \begin{array}{l} \text{Due to symmetry:} \\ I_{C1} = I_{C2} = 1mA + \frac{g_m U_1}{2} \end{array} \right.$$

and

$$g_{m1} = g_{m2} = \frac{I_{C1/2}}{V_T} = \frac{1mA}{V_T} + \frac{g_m U_1}{2V_T}$$

$$\text{Now, } U_{C1} = -\beta(i_b) R_C = -\frac{\beta}{r_a} \frac{U_d}{2} R_C = \boxed{-g_{m1} R_C \frac{U_d}{2}}$$

$$U_{C2} = -\beta i_b R_C = \left(-\frac{\beta}{r_a} \left(-\frac{U_d}{2} \right) \right) R_C = \boxed{g_{m2} R_C \frac{U_d}{2}}$$

$$\Rightarrow \boxed{U_{out} = g_{m1,2} R_C U_d = \left(\frac{1mA}{V_T} + \frac{g_m U_1}{2V_T} \right) R_C U_d}$$

$$g_m = 2\sqrt{k_I I_D} \cdot 2\sqrt{\rho_s l^2} \\ = 2mA/V$$

$$= \left(\frac{1mA}{0.026V} + \frac{(2mA/V) U_1}{2(0.026)} \right) (4k) U_d = \boxed{153.85 U_d + (153.85)(U_1, U_2)}$$

This is a multiplier circuit whose output is AM modulated. The frequencies present are (using the identity:

$$cos a \cdot cos b = \frac{1}{2} [cos(a+b) + cos(a-b)]$$

$$\Rightarrow \boxed{w_{01} = w_1 + w_2}$$

$$w_{02} = w_2 - w_1$$

These frequencies will also be present in the output


$$\Rightarrow \boxed{U_{out} = 0.153 \cos(w_1 t) + 0.0153 \cos(w_2 t) \cos(w_1 t)}$$

multiplied.

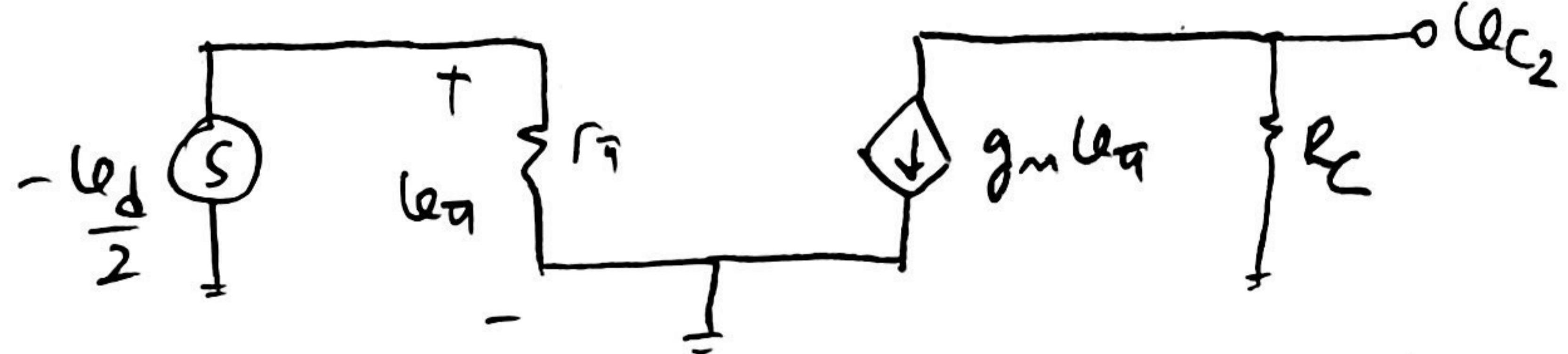c) Since M1 has no s.s. on it, it will act like a resistance with r_o in S.S.

$$r_o = \frac{1}{\lambda I_D} \cdot \frac{1}{(0.02)(2)} = 25k\Omega$$

A_{dm2} : Omit r_o since no current passes on diff. mode




$$A_{dm2} = \frac{U_{C2}}{-U_d} = \frac{g_m R_C}{2}$$

$$U_{C2} = g_m U_a R_C \\ = g_m \frac{U_d}{2} R_C$$

$$g_m \text{ of } Q_1, Q_2: \frac{I_C}{V_T} = \frac{1mA}{0.026V} = 38.46 \text{ mA/V}$$

$$\Rightarrow A_{dm2} = 76.92 \frac{V}{V}$$

$$r_\pi = \frac{f}{g_m} = 2.6k\Omega$$

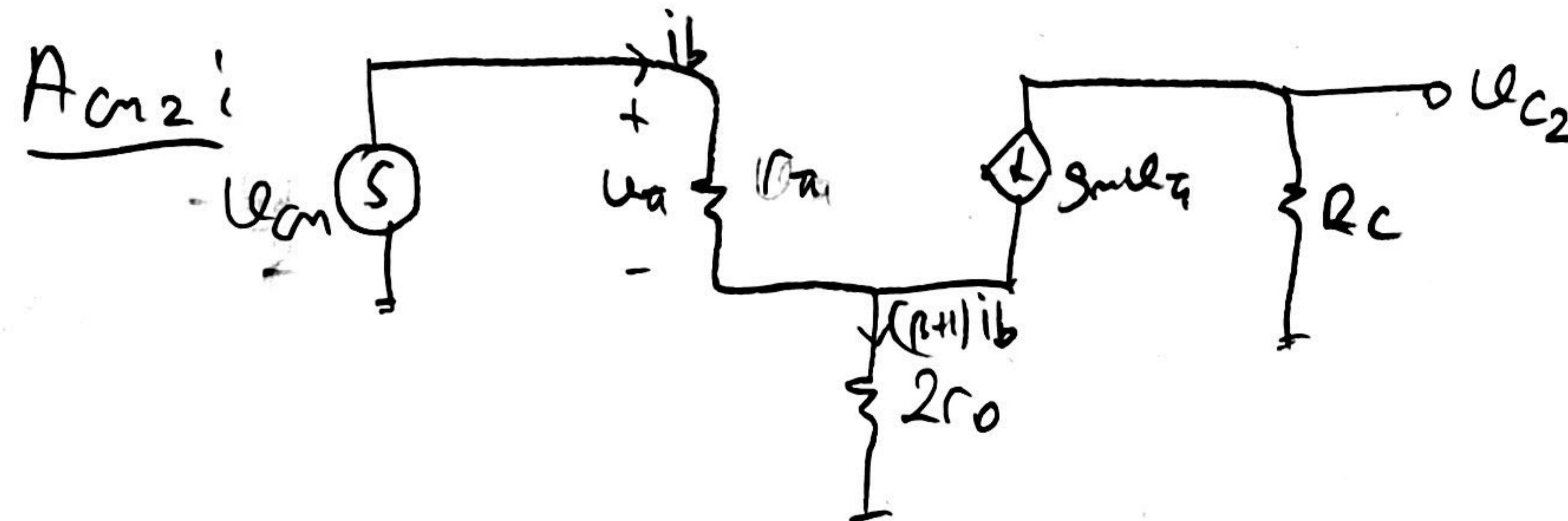

$$U_{H2} = -\frac{U_{cm}}{R_\pi + 2(\beta+1)r_o}$$

$$U_{C2} = -g_m U_a R_C = -U_{cm} \frac{(g_m r_\pi) R_C}{r_\pi + 2(\beta+1)r_o}$$

$$\Rightarrow A_{cm2} = \frac{U_{C2}}{U_{cm}} = -\frac{\beta R_C}{r_\pi + 2(\beta+1)r_o}$$

$$A_{cm} = -0.079 \frac{V}{V}$$

$$\Rightarrow CMRR = \left| \frac{A_{dm2}}{A_{cm2}} \right| = \frac{76.92}{0.079} = 973.67 \approx 59.77 \text{ dB}$$