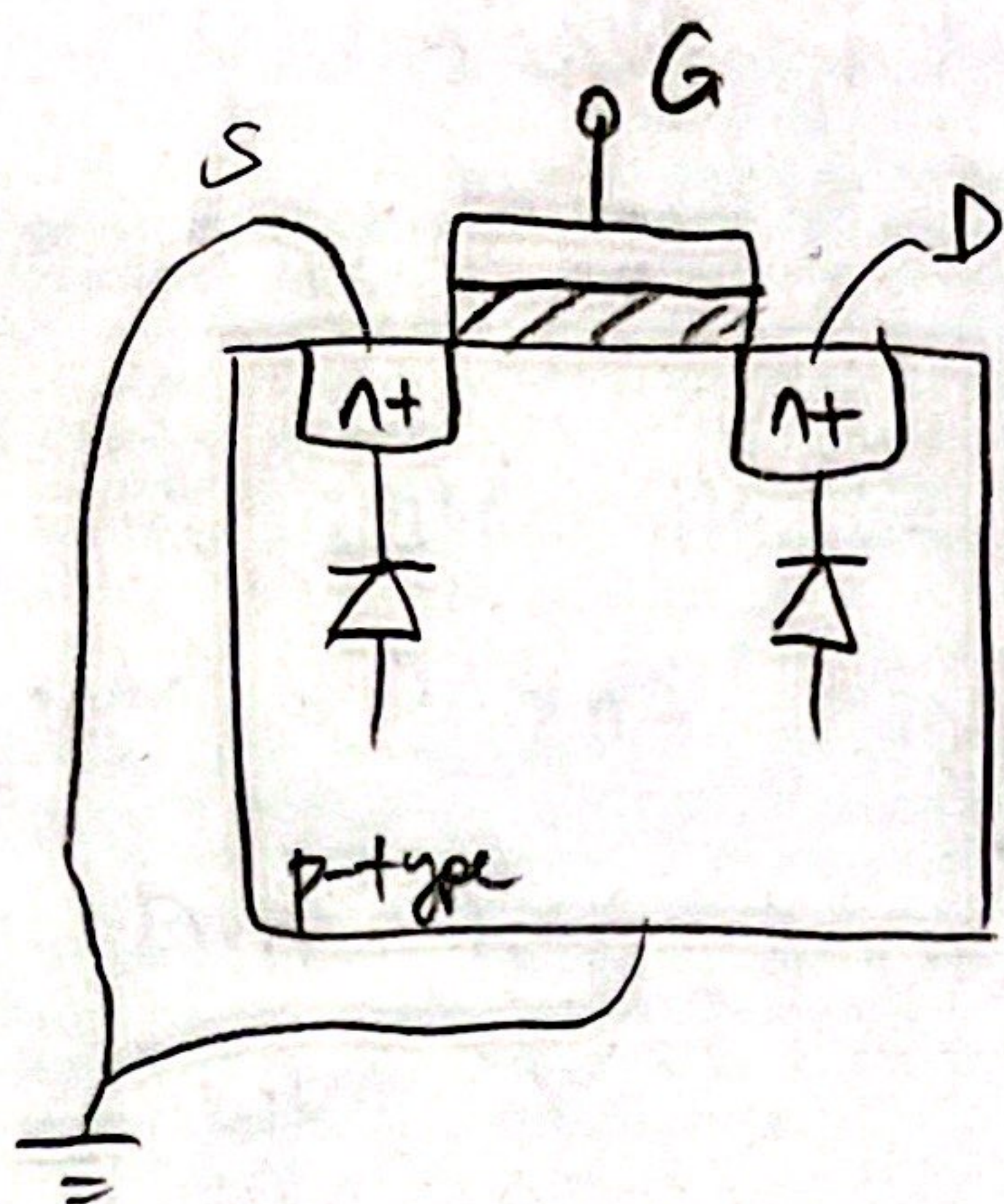



ECD- HW 1

Vigitt Narter
22102718


- ① a) $V_{GS} < V_{th}$ →
 ⇒ no e^- inversion layer
 ⇒ drain current is zero, since no inversion layer.


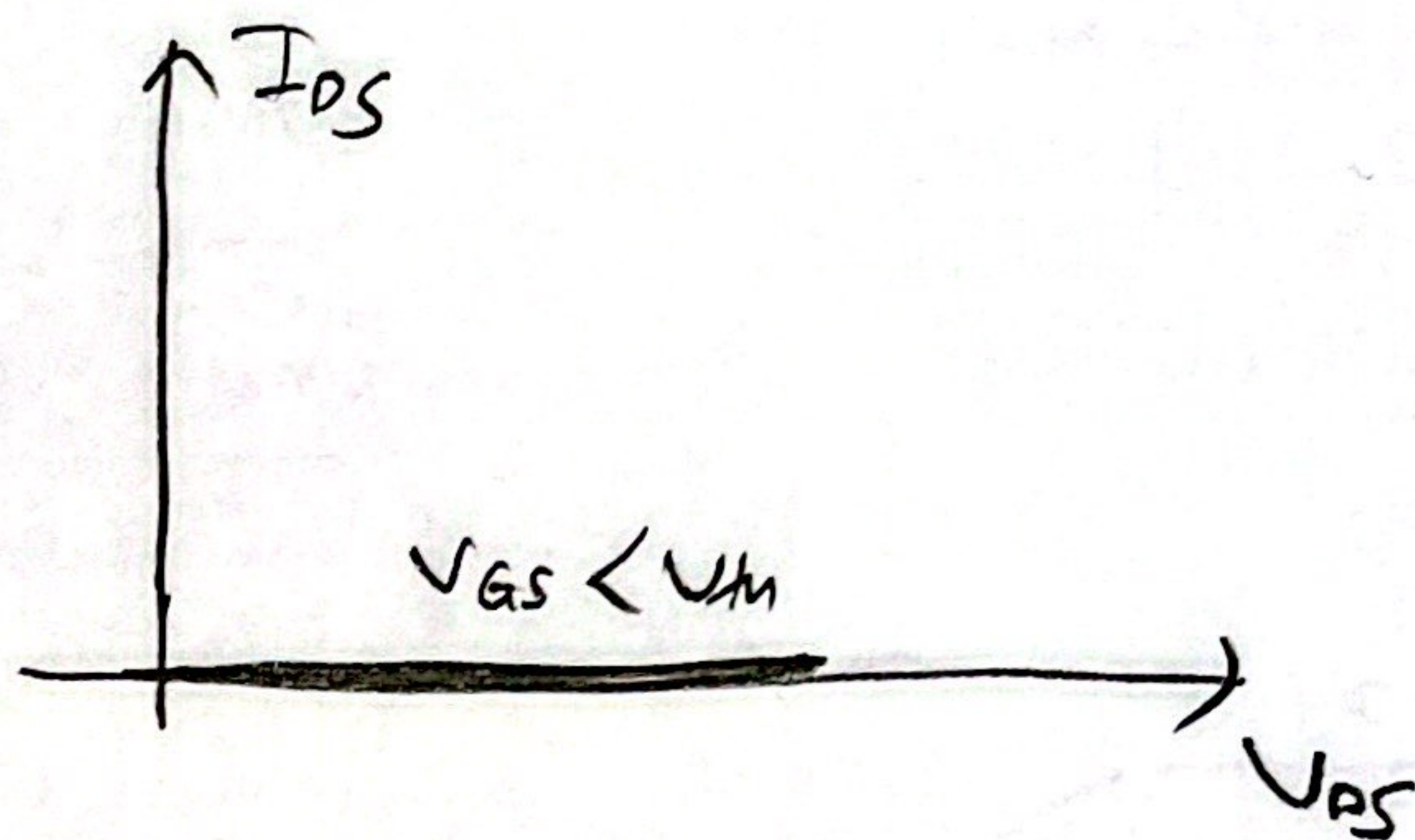
$$I_{DS} = 0 \Rightarrow \text{OFF mode}$$




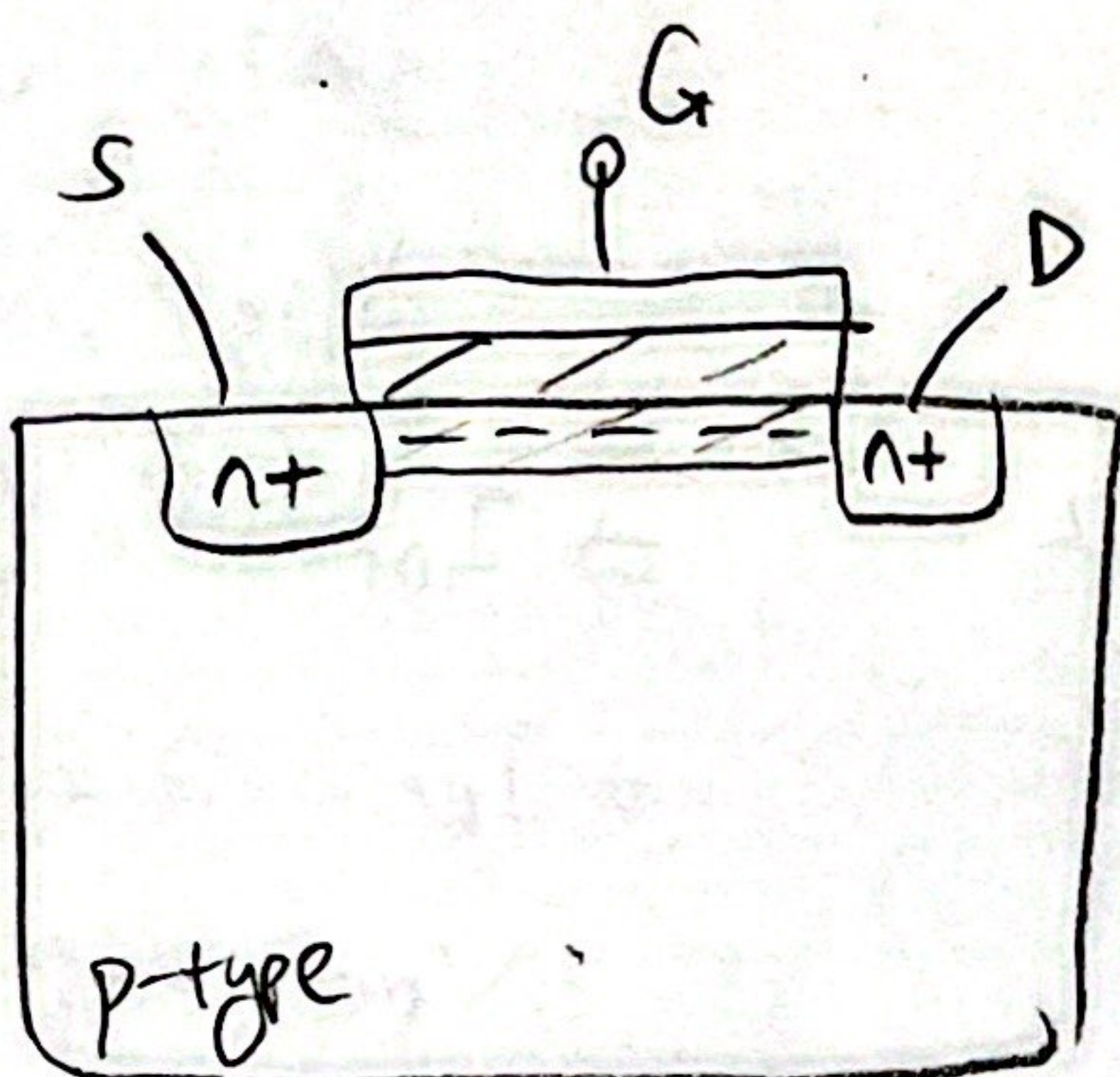- b) $V_{GS} > V_{th}$
 small V_{DS}
 ⇒ e^- inversion layer is created.




$$I_{DS} = K_n (2(V_{GS} - V_{th})V_{DS} - V_{DS}^2)$$

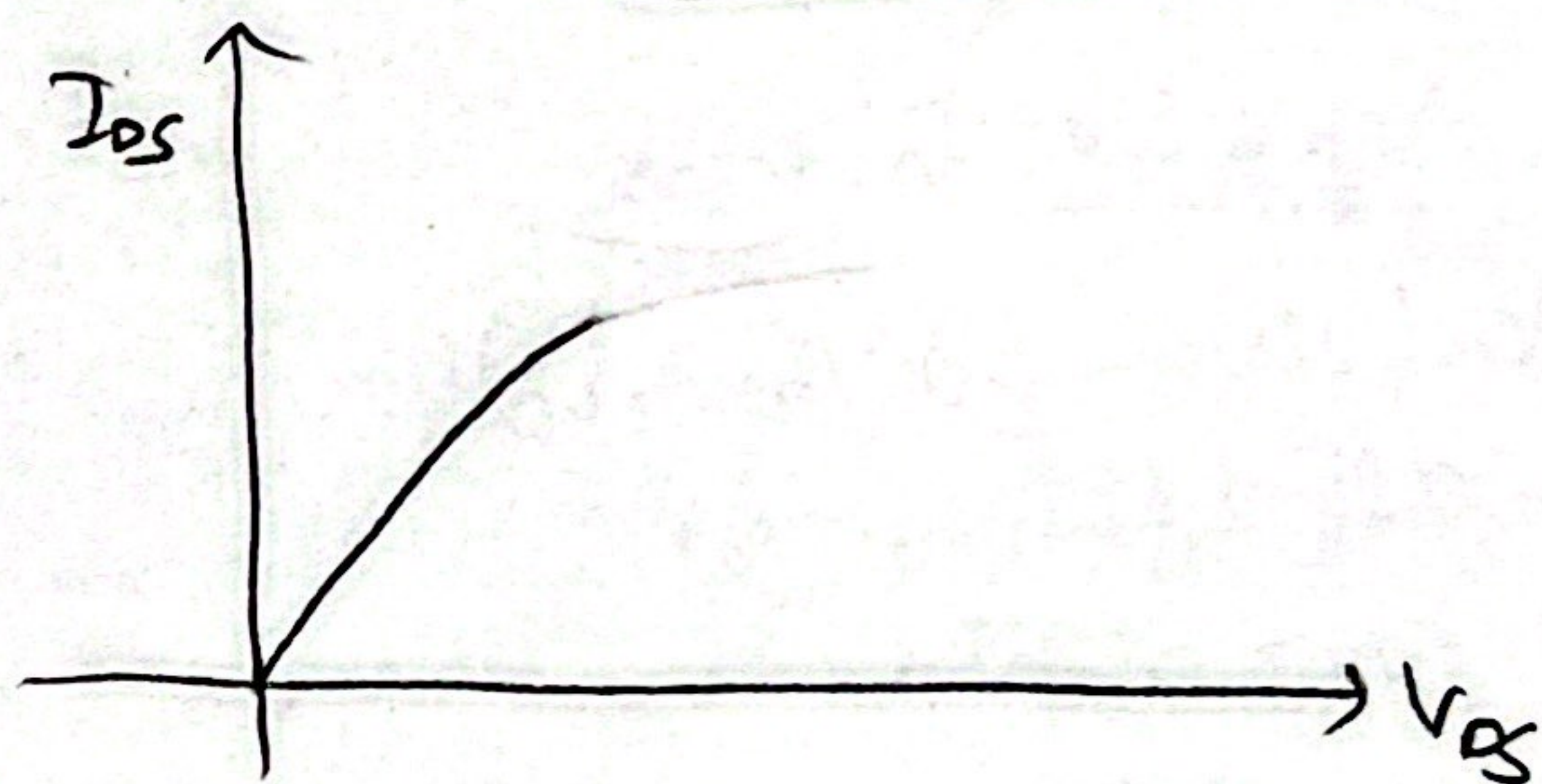for $V_{DS} < V_{GS} - V_{th}$
 ⇒ TRIODE mode




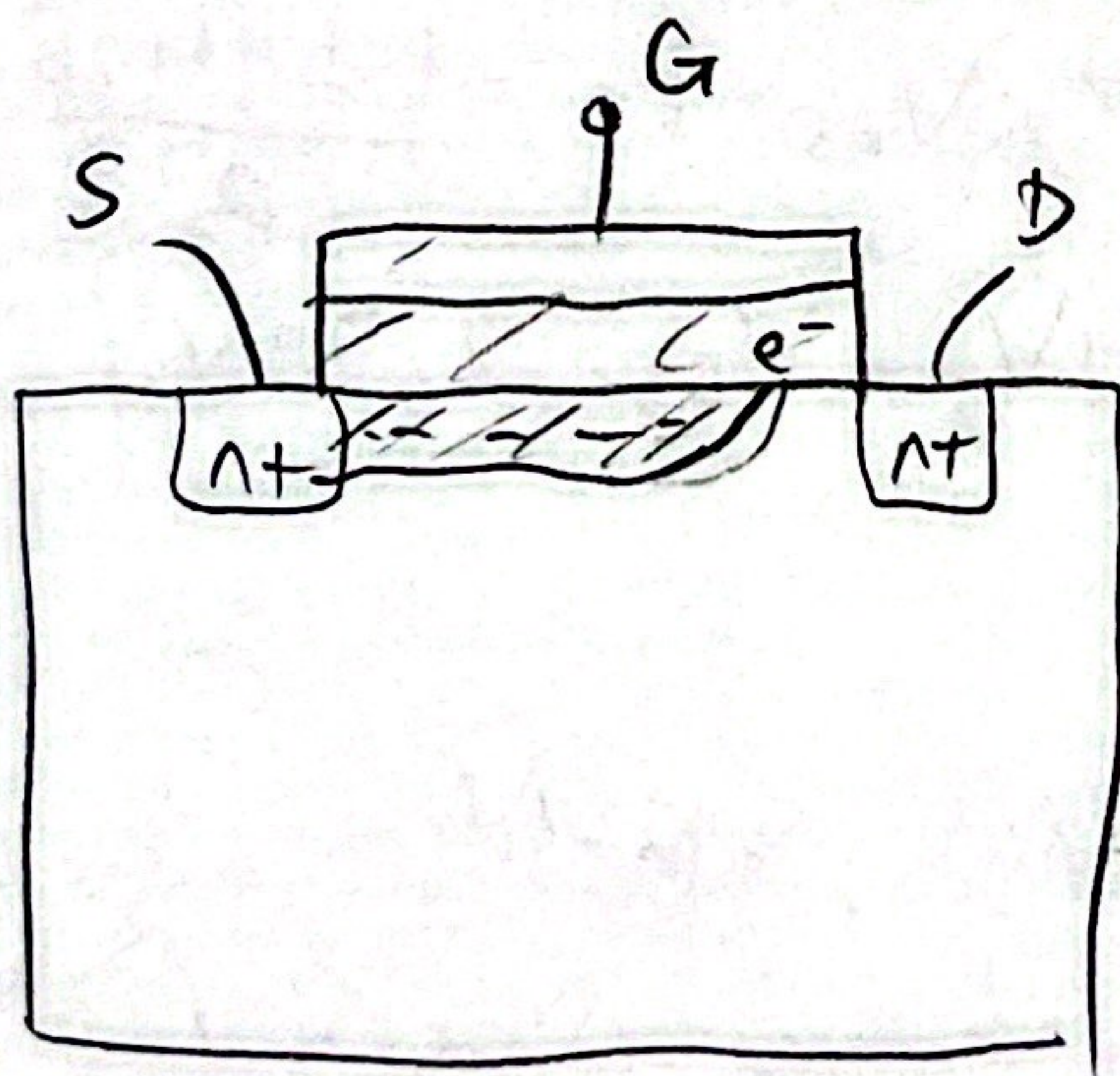- c) $V_{GS} > V_{th}$
 large V_{GS}
 ⇒ when $V_{DS} > V_{DSsat}$
 $V_{DSsat} = V_{GS} - V_{th}$
 the e^- inversion layer moves to the source terminal, e^- 's are swept by \vec{E} field.



$$I_{DS} = K_n (V_{GS} - V_{th})^2$$

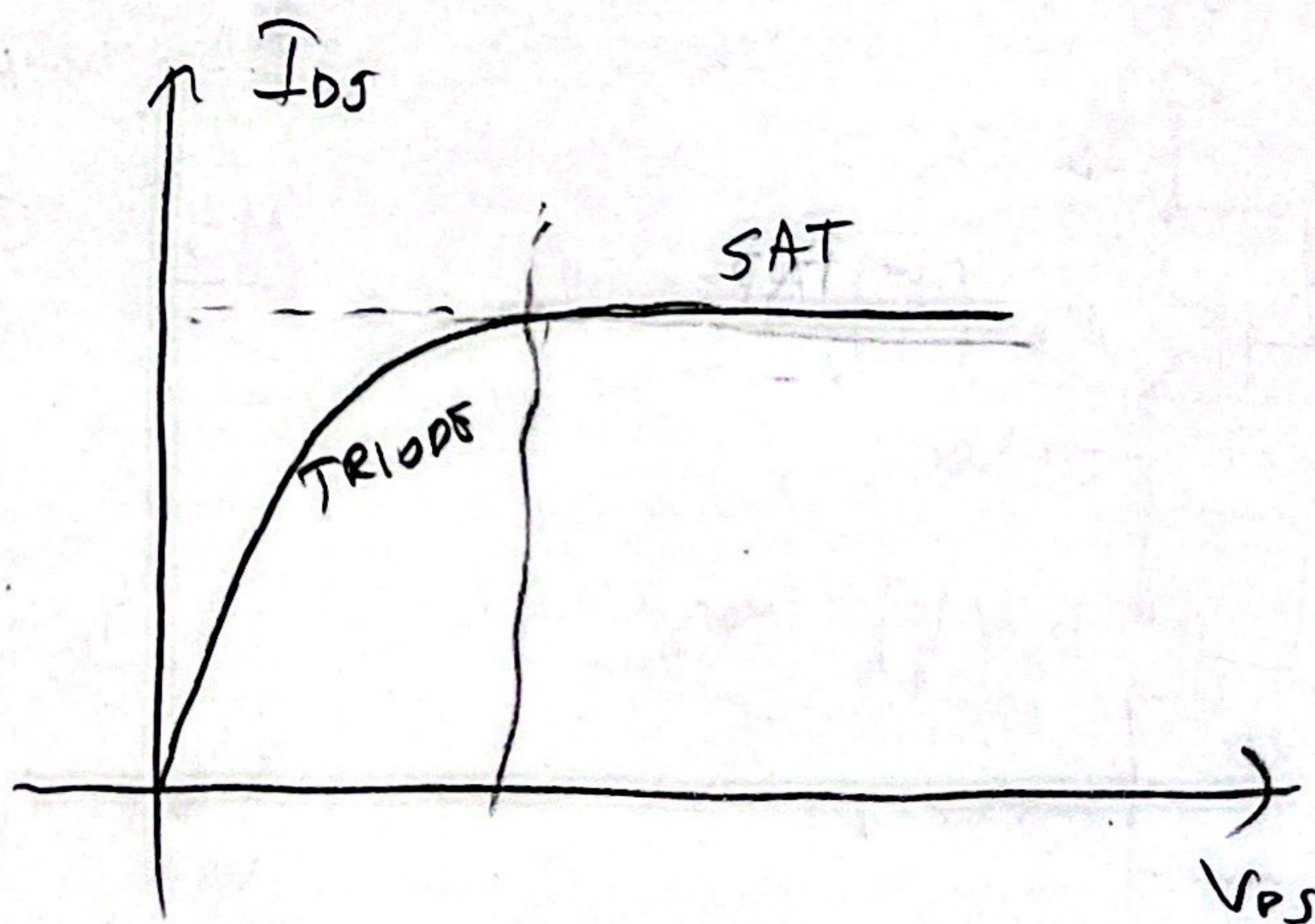
for $V_{DS} > V_{GS} - V_{th}$
 ⇒ SAT mode



⇒ The gate is isolated with an oxide so there is no DC gate current.

⇒ No source-substrate or drain-substrate currents since those p-n junctions (diodes) are OFF.

2

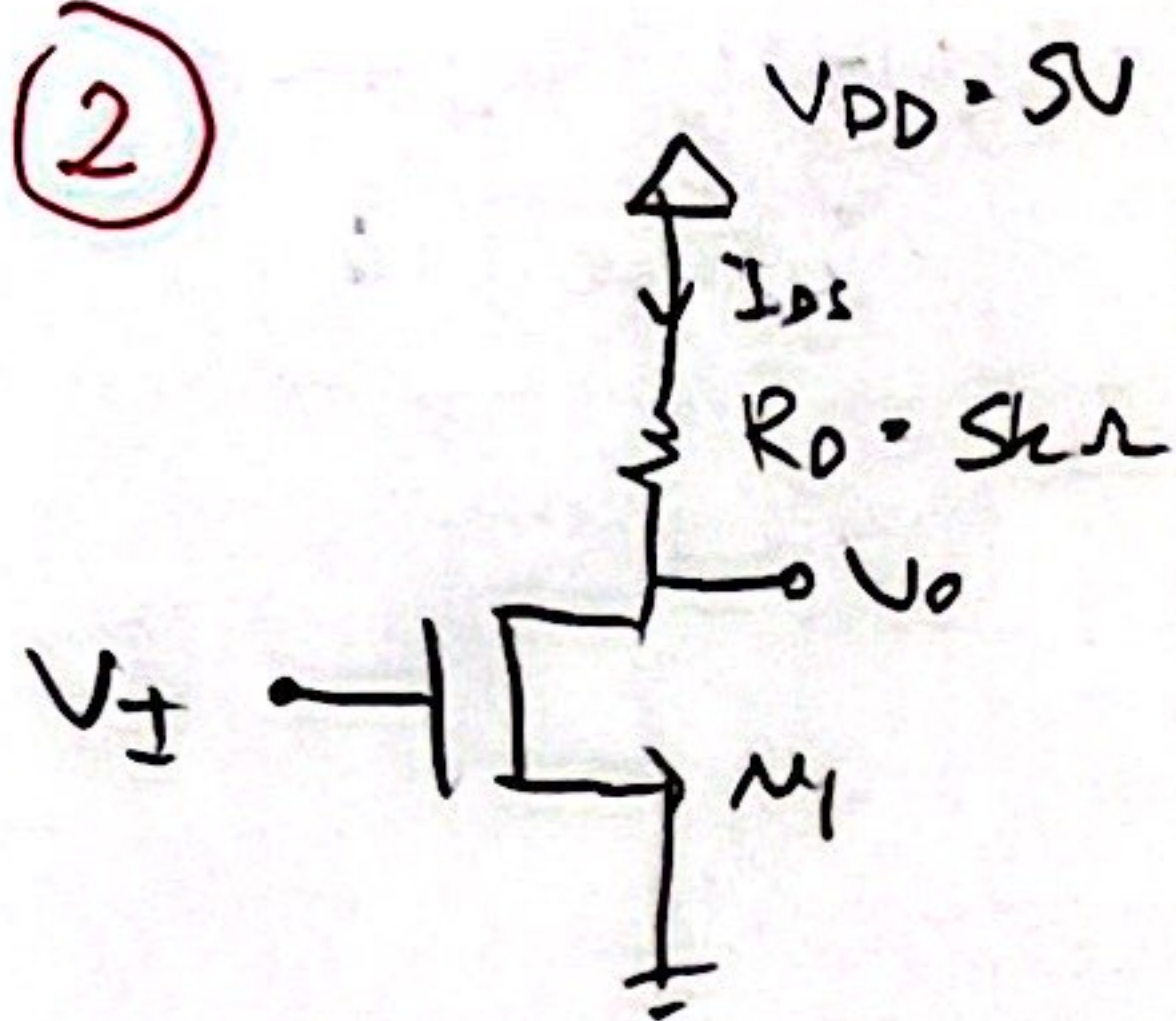


$$V_{TH} = 1V, K_n = 0.2 \text{ mA/V}^2$$

From KVL: $V_{DD} = I_D R_D + V_O$

$$\Rightarrow V_O = V_{DS} = 5 - 5I_{DS} \quad \dots (1)$$

when $V_I < \underline{V_{TH}} \Rightarrow \underline{I_{DS}} = 0, \underline{V_{DS}} = 5V \rightarrow \text{nmos is OFF}$

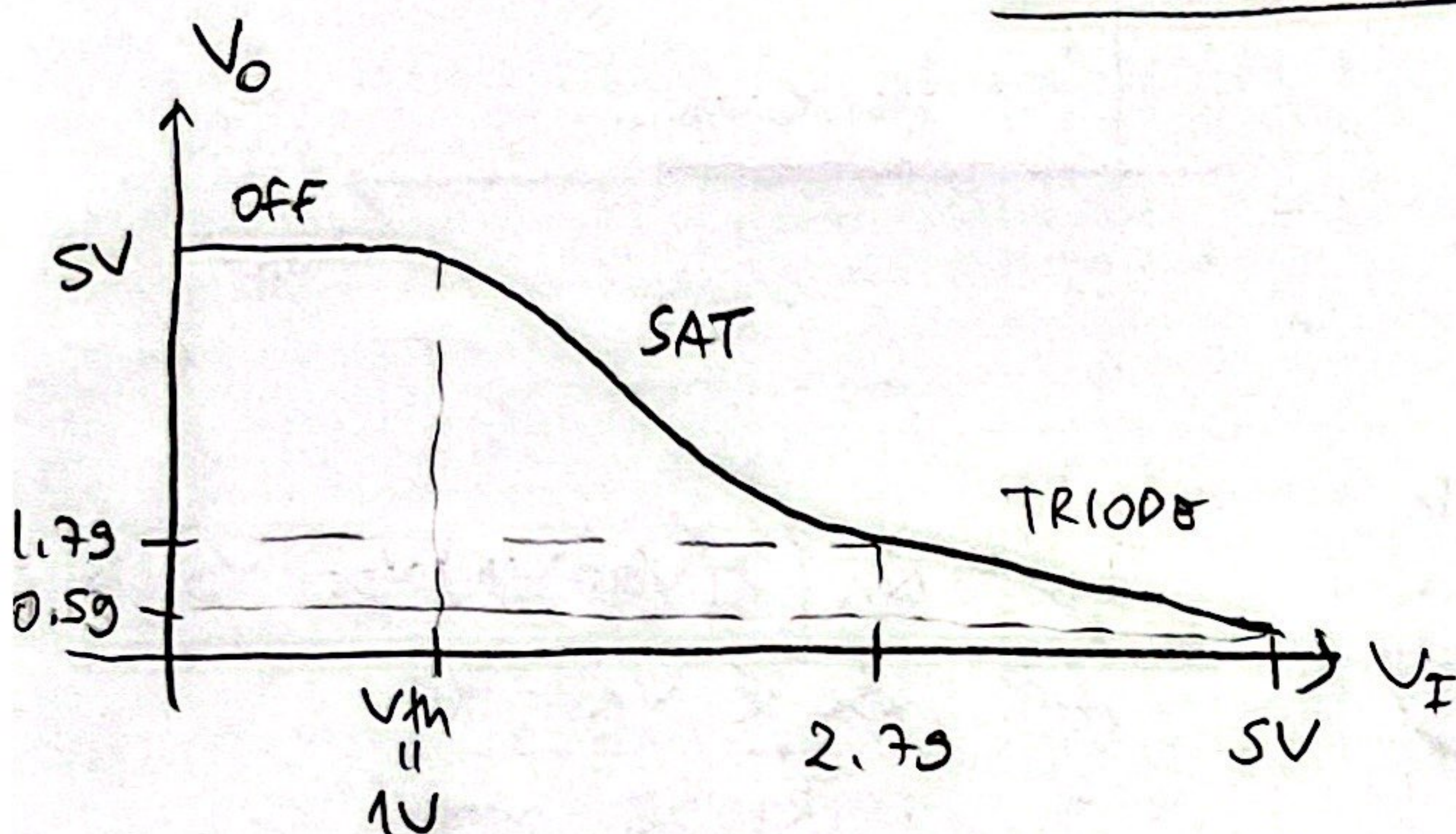when $V_I > \underline{V_{TH}} = 1V \Rightarrow$ first start from SAT since the V_{DS} is large (close to 5V) and V_I is close to V_{TH} ($V_I - V_{TH}$ is small)



When changing from TRIODE to SAT, we need:

$$V_{DS} = V_{GS} - V_{TH} = V_{GS} - 1$$

$$\Rightarrow I_{DS} = K_n (2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2)$$

$$\Rightarrow I_{DS} = 0.2(V_{GS} - 1)^2 \text{ and}$$

$$V_{DS} = V_{GS} - 1 \text{, insert into (1):}$$

$$V_{GS} - 1 = 5 - 5 \cdot 0.2(V_{GS} - 1)^2$$

$$\Rightarrow (V_{GS} - 1)^2 + (V_{GS} - 1) - 5 = 0$$

$$\Rightarrow V_{GS} - 1 = \frac{-1 \pm \sqrt{1 + 20}}{2} \approx 1.79 \text{ (take positive since } V_{GS} - 1 > 0 \text{ for ON)}$$

$$\Rightarrow \boxed{V_I = V_{GS} = 2.79V}, \boxed{V_{DS} = 1.79V = V_O}, \boxed{I_{DS} = 0.64 \text{ mA}}$$

when $V_I = 5V$: in triode.

$$I_D = K_n (2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2)$$

$$\Rightarrow I_D = 0.2[2(5-1)V_O - V_O^2]$$

$$\text{and } V_O = 5 - 5I_D$$


$$\Rightarrow 5 - V_O = 0.1(8V_O - V_O^2)$$

$$\Rightarrow V_O^2 - 8V_O + 5 = 0$$

$$V_O = 8.4V \text{ or } \boxed{V_O = 0.59V}$$

- since in triode $V_{DS} < V_{GS} - V_{TH}$

3

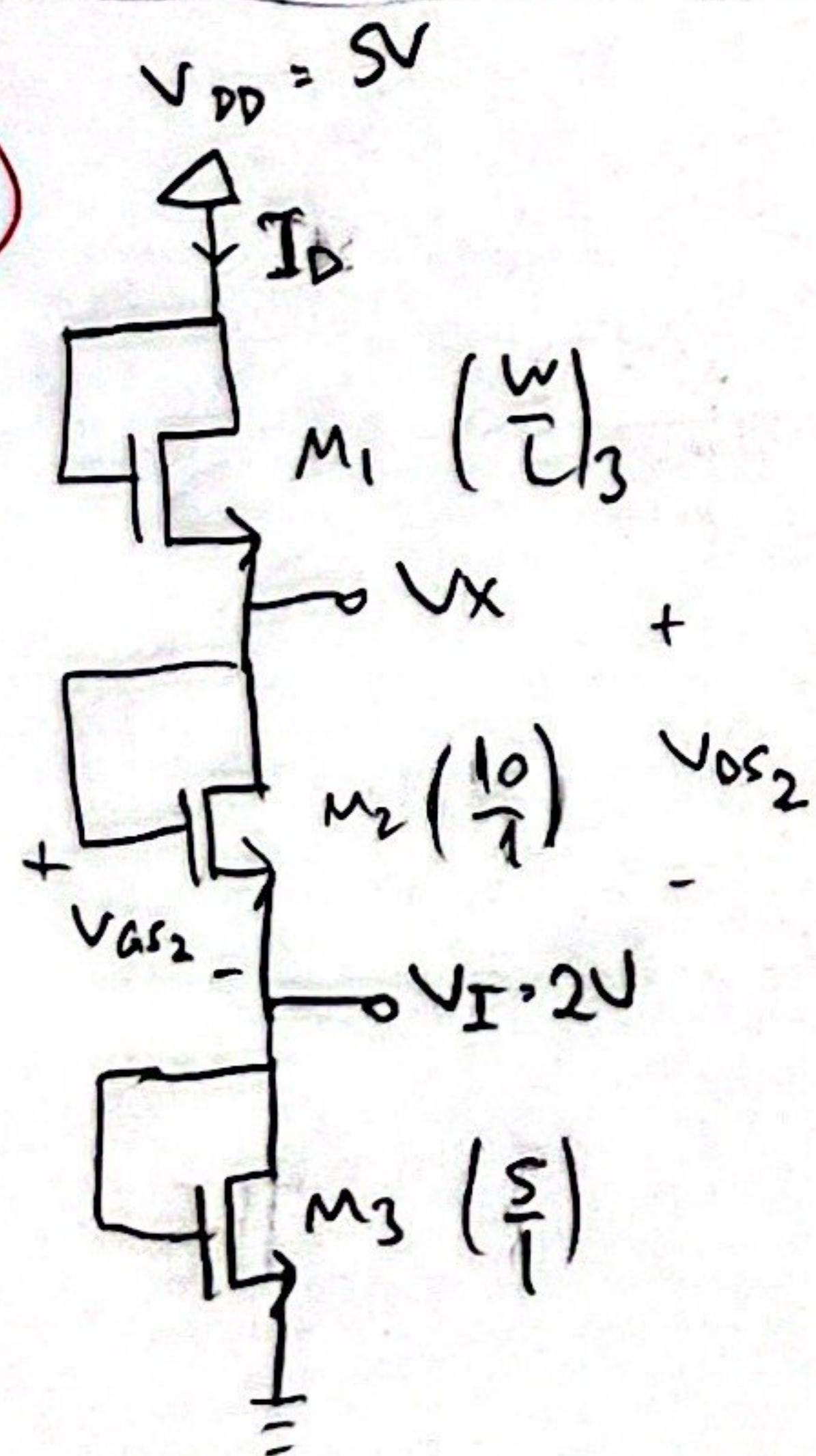

$$\frac{K_n'}{2} = 100 \mu\text{A/V}^2, V_{TH} = 1V$$

M3: ON since $V_{GS3} = 2V > V_{TH} = 1V$
in SAT since $V_{DS3} = V_{GS3} = 2V$ (diode connected)
and $\underline{V_{DS3}} > \underline{V_{GS3} - V_{TH}}$ ✓

$$\Rightarrow I_D = \frac{K_n'}{2} \left(\frac{W}{L}\right) \cdot (V_{GS} - V_{TH})^2 = 100 \cdot 5 \cdot (2-1)^2 = 500 \mu\text{A}$$

M2: Assume SAT:

$$I_{DS2} = I_D = \frac{K_n'}{2} \left(\frac{W}{L}\right) (V_{GS2} - V_{TH})^2 = 500 \mu\text{A}$$

$$\Rightarrow (V_{GS2} - 1)^2 = 0.5$$

$$\Rightarrow \underline{V_{GS2} = 1.71V}$$

2

and $V_X = V_{GS2} + 2V = \underline{3.71V}$ (from KVL) $\overbrace{1.71V}^{0.71V}$

$V_{DS2} = \overbrace{V_X}^{3.71V} - \underbrace{V_I}_{2V} = \underline{1.71V} = V_{GS2}$ Check: $\overbrace{V_{DS2}}^{1.71V} > \underbrace{V_{GS2}}_{1.71V} - \underbrace{V_{th}}_1$ ✓ in SAT mode (diode connected)
and $\overbrace{V_{GS2}}^{1.71V} > \underbrace{V_{th}}_1$ ✓

M1: Assume SAT:

$I_{DS1} = I_D = \frac{K_1}{2} \left(\frac{W}{L}\right)_3 (V_{GS1} - V_{th})^2 = 500 \mu A$ and $V_{GS1} = V_{DD} - V_X = \underline{1.29V}$ (from KVL)

$= 100 \left(\frac{W}{L}\right)_3 (1.29 - 1)^2 = 500 \mu A \Rightarrow \left(\frac{W}{L}\right)_3 = \underline{59.45}$

Check: $V_{DS1} = V_{DD} - V_X = 1.29V = V_{GS1}$ $\overbrace{V_{GS1}}^{1.29V} > \underbrace{V_{th}}_1 \Rightarrow ON$

$\overbrace{V_{GS1}}^{1.29V} > \underbrace{V_{DS1}}_{1.29V} - \underbrace{V_{th}}_1$ ✓ in SAT mode

$\Rightarrow \boxed{V_X = 3.71V}, \boxed{I_D = 500 \mu A}, \left(\frac{W}{L}\right)_3 = 59.45$

All transistors are in SAT mode (diode connected)

(4) $K_p = 0.25 \text{ mA/V}^2$, $V_{tp} = -1V \Rightarrow |V_{tp}| = 1V$

$V_G = 10 \cdot \frac{30k}{30k + 70k} = \underline{3V}$ (by voltage div. and $I_G = 0$)

By KVL: $10 = I_D (R_S + R_D) + V_{SD} = I_D (R_S + 3) + V_{SD} \Rightarrow V_{SD} = 10 - I_D (R_S + 3)$

$V_S = 10 - I_D R_S$, $V_D = 3 I_D$, $V_{SG} = 7 - I_D R_S$

a) $R_S = 5k\Omega$, $V_S = 10 - 5 I_D$

Assume SAT: $I_D = 0.25 (V_{SG} - |V_{tp}|)^2 = 0.25 (6 - 5 I_D)^2$

$\Rightarrow -6.25 I_D^2 + 16 I_D - 9 = 0$

$\Rightarrow \boxed{I_D = 0.83 \text{ mA}}$ or $I_D = 1.73 \text{ mA}$

since we need

$V_{SG} = 7 - I_D \cdot 5 > 1$

Check: $V_{SD} > V_{SG} - |V_{tp}| \Rightarrow V_{SD} = 10 - (0.83) \cdot 8 = 3.36V$
 $V_{SG} = 7 - (0.83) \cdot 5 = 2.85V$

$\Rightarrow \underbrace{V_{SD}}_{3.36V} > \underbrace{V_{SG}}_{2.85V} - \underbrace{|V_{tp}|}_1 \Rightarrow \text{in SAT mode} \checkmark$

$\Rightarrow \boxed{(V_{SD}, I_D) = (3.36V, 0.83 \text{ mA})}$

b) $R_S = 1k\Omega$, $V_{SD} = 10 - 4I_D$
 $V_{SG} = 7 - I_D$

Assume SAT:
 $I_D = 0.25(7 - I_D - 1)^2 = 0.25(6 - I_D)^2$
 $I_D = 2.71 \text{ mA}$ or $I_D = 13.3 \text{ mA}$
 since $V_{SG} > |V_{th}|$

Check: $V_{SD} = 0.84 \text{ V}$
 $V_{SG} = 4.29 \text{ V} \Rightarrow$ in TRIODE mode.

Triode $\Rightarrow I_D = 0.25(2(V_{SG} - |V_{th}|)V_{SD} - V_{SD}^2)$


$I_D = 0.25(2(6 - I_D)(10 - 4I_D) - (10 - 4I_D)^2)$
 $\Rightarrow 2I_D^2 - 2I_D - 5 = 0 \Rightarrow I_D = -1.5 \text{ mA}$ or $I_D = 2.16 \text{ mA}$

and $V_{SD} = 10 - 4I_D = 1.36 \text{ V}$

Check: $\frac{V_{SD}}{1.36} < \frac{V_{SG} - 1}{3.84} \checkmark \Rightarrow$ in TRIODE

$\Rightarrow (V_{SD}, I_D) = (1.36 \text{ V}, 2.16 \text{ mA})$

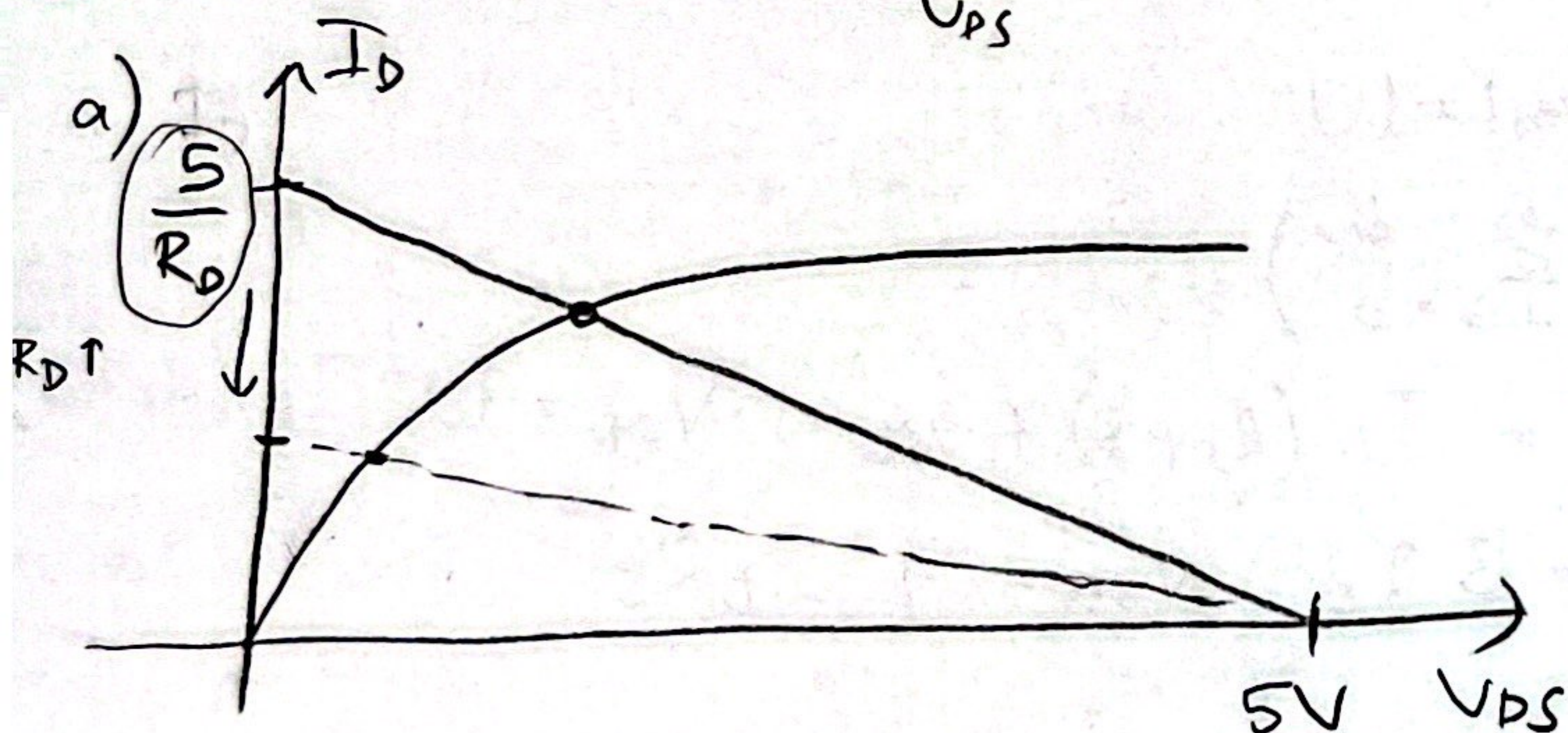5) KVL: $5 = I_D R_D + \underbrace{V_{DS}}_{V_{DS}} \Rightarrow V_{DS} = 5 - I_D R_D$



Use load line approach:

For SAT, we need
 $V_{DS} > V_{GS} - V_{th}$
 $5 - I_D R_D > 3.5$
 $\Rightarrow R_D I_D < 1.5$

As the value of R_D is increased, the state of M1 is approaching NON-SAT (TRIODE). It can be seen from the plot ($\frac{5}{R_D}$ decreases and the line intersects in the NON-SAT mode).

b) Just when $V_{DS} < V_{GS} - V_{th}$, M1 will go to NON-SAT mode $\Rightarrow V_{DS} = 5 - I_D R_D$ and $I_D = 0.2(5 - 1.5)^2 = 2.45 \text{ mA}$ (in SAT)

hence we need:

$V_{DS} > V_{GS} - V_{th} \Rightarrow 5 - 2.45 R_D > 3.5$

$2.45 R_D < 1.5$

$R_D < 0.612 k\Omega$
 612Ω

⑥ KVL: $V_{SD2} + V_{DS1} = 5V$, $V_{SG2} = 5 - V_b$

To have M2 in TRIODE: $V_{SD2} < \underbrace{V_{SG2} - |V_{th}|}_{5-V_b} = 4 - V_b$ ①

a) $V_I = 2V$, to have M2 in TRIODE: $V_{SD2} < 4 - V_b$ and to have ON: $V_{SG} > |V_{th}|$

and $I_D = K_p (2 \cdot V_{SD2} (4 - V_b) - V_{SD2}^2)$ ④

to have M1 in SAT: $\underbrace{V_{DS1}}_{5-V_{SD2}} > \underbrace{V_{GS1}}_{V_I=2V} - \underbrace{V_{th}}_{1V} \Rightarrow 5 - V_{SD2} > 1$
 $V_{SD2} < 4V$ ②

$V_{SG} > |V_{th}|$
 $5 - V_b > 1$
 $\Rightarrow V_b < 4V$ ③

and $I_D = K_n (\underbrace{V_{GS2}}_{2V} - \underbrace{V_{th}}_{1V})^2 = \cancel{K_n} = \cancel{K_p} (2 V_{SD2} (4 - V_b) - V_{SD2}^2)$
 $\Rightarrow V_{SD2}^2 - (8 - 2V_b) V_{SD2} + 1 = 0$

To have real solutions: $(8 - 2V_b)^2 - 4 \geq 0 \Rightarrow (4 - V_b)^2 - 1 \geq 0$

$4 - V_b \geq 1$ or $4 - V_b \leq -1$
 $V_b \leq 3$ or $V_b \geq 5$
 by ④, but check

$V_{SD2} = \frac{8 - 2V_b \pm \sqrt{4(4 - V_b)^2 - 4}}{2} = 4 - V_b \pm \sqrt{(4 - V_b)^2 - 1}$ to satisfy ①

\Rightarrow Insert into 2: $4 - V_b - \sqrt{(4 - V_b)^2 - 1} < 4 \Rightarrow V_b - \sqrt{(4 - V_b)^2 - 1} > 0$
 holds true for all $V_b \leq 3$

$0 < V_b < 3V$

④ Check limit:

At $V_b = 3V$:

$\Rightarrow V_{SD}^2 - 2V_{SD} + 1 = 0 \Rightarrow V_{SD} = 1V$

Ineq. ① isn't satisfied!: $\underbrace{V_{SD2}}_{1V} \not< \underbrace{4 - V_b}_{1V}$

b) $V_I = 3V$, to have M2 in TRIODE: $V_{SD2} < 4 - V_b$ ①

and $I_D = K_p (2 V_{SD2} (4 - V_b) - V_{SD2}^2)$

to have M1 in SAT: $V_{GS2} > \underbrace{V_{GS2} - 1}_{3V} \Rightarrow 5 - V_{SD2} > 2$
 $\Rightarrow V_{SD2} < 3V$ ②

to have the PMOS ON: $V_{SG} > |V_{tp}| \Rightarrow 5 - V_b > 1$
 $V_b < 4V$ ③

and $I_D = K_n (\underbrace{V_{GS2}}_3 - \underbrace{V_{tn}}_1)^2 \Rightarrow 4K_n = K_p (2 V_{SD2} (4 - V_b) - V_{SD2}^2)$
 $\Rightarrow V_{SD2}^2 - (8 - 2V_b) V_{SD2} + 4 = 0$

To have real solutions: $(8 - 2V_b)^2 - 16 \geq 0 \Rightarrow (4 - V_b)^2 - 4 \geq 0$

$4 - V_b \geq 2$ or $4 - V_b \leq -2$
 $V_b \leq 2$ or $V_b \geq 6$
 by ③, but check

$V_{SD2} = \frac{8 - 2V_b \pm \sqrt{4(4 - V_b)^2 - 16}}{2} = 4 - V_b - \sqrt{(4 - V_b)^2 - 4}$ to satisfy ①

\Rightarrow Insert into 2: $4 - V_b - \sqrt{(4 - V_b)^2 - 4} < 4 \Rightarrow \underbrace{V_b - \sqrt{(4 - V_b)^2 - 4}}_{\text{holds for all } V_b \leq 2} > 0$

Check limits:

⊗ At $V_b = 2$:

$V_b = 2 \Rightarrow V_{SD}^2 - 4V_{SD} + 4 = 0$
 $V_{SD} = 2V \Rightarrow \frac{V_{SD}}{2V} \neq \frac{4 - V_b}{2V}$

Ineq. ① isn't satisfied!

$0 < V_b < 2V$