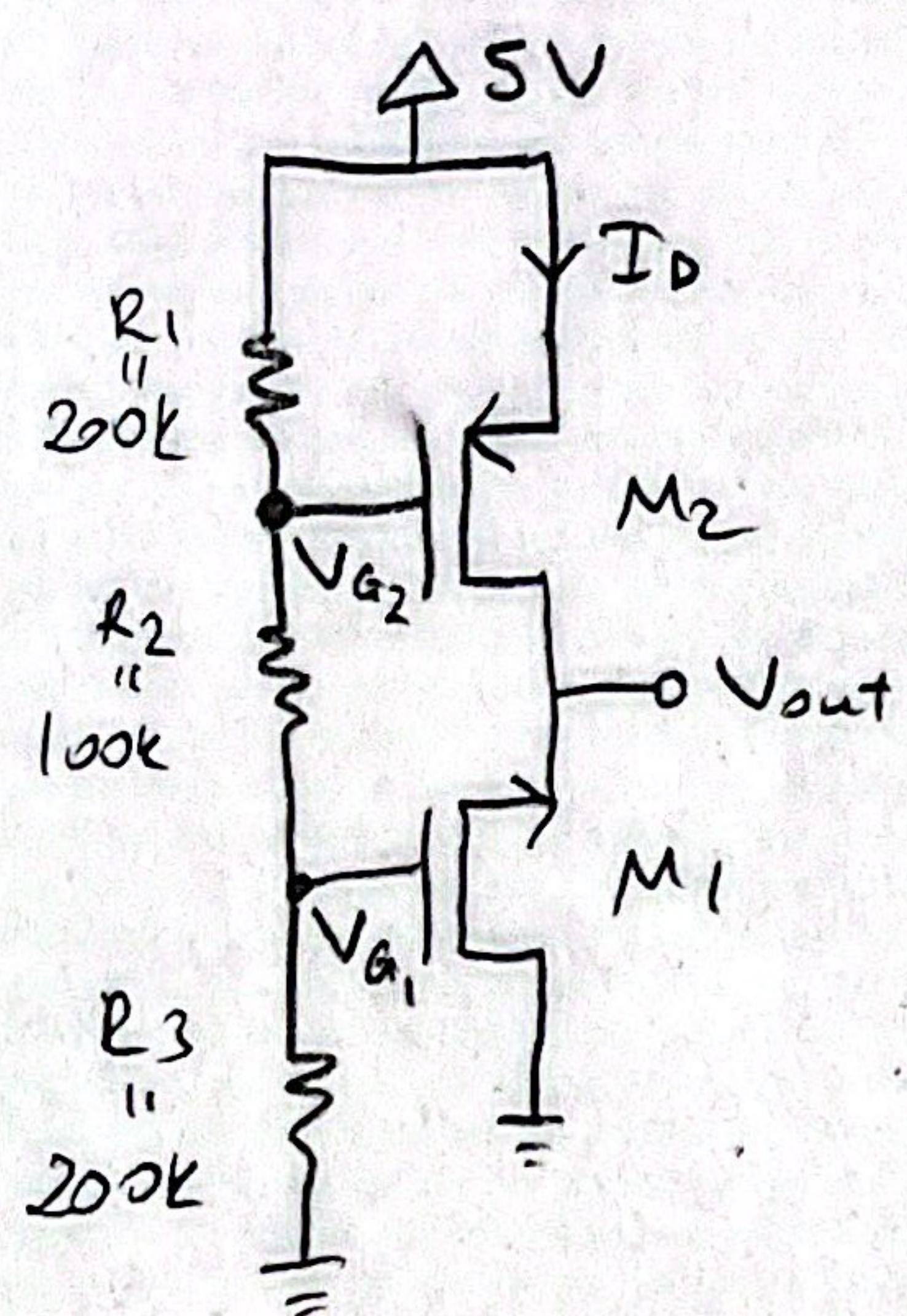


① a) DC analysis: Open-circuit the capacitors:



By voltage dividers (since gate currents are 0):

$$V_{G1} = \frac{R_3}{R_1 + R_2 + R_3} \cdot 5V = 2V$$

$$V_{G2} = \frac{R_3 + R_2}{R_1 + R_2 + R_3} \cdot 5V = 3V$$

$$\Rightarrow V_{GS1} = 2V, V_{DS1} = V_{out}$$

$$V_{SG2} = 2V, V_{SD2} = 5 - V_{out}$$

} by KVL.

Assume SAT for both  $M_1$  and  $M_2$ :

$$\text{For } M_1: I_D = \frac{k_n}{0.25} \left( \frac{V_{GS1} - V_{tp}}{2} \right)^2 = 0.25 \text{ mA}$$

Currents match

but how to find  
 $V_{DS}(V_{out})?$

$$\text{For } M_2: I_D = \frac{k_p}{0.25} \left( \frac{V_{SG2} - V_{tp}}{2} \right)^2 = 0.25 \text{ mA}$$

| DON'T ignore  $\lambda$ 's!

Write again the saturation currents:

$$I_D = k_n (V_{GS1} - V_{tp})^2 (1 + \lambda V_{DS}) = 0.25 (1 + 0.02 V_{out}) \rightarrow \text{for } M_1$$

$$\text{and } I_D = k_p (V_{SG2} - V_{tp})^2 (1 + \lambda V_{SD}) = 0.25 (1 + 0.01 (5 - V_{out})) \rightarrow \text{for } M_2$$

$$\Rightarrow I_D = 0.25 (1 + 0.02 V_{out}) = 0.25 (1 + 0.01 (5 - V_{out}))$$

$$\Rightarrow V_{out} = \frac{5}{3} \sqrt{1.67} \approx 1.67V, \Rightarrow I_D = 0.25 (1 + 0.02 (1.67)) = 0.258 \text{ mA}$$

Check:  $\frac{V_{DS1}}{1.67V} > \frac{V_{GS1} - V_{tp}}{2V - 1V = 1V} \checkmark \Rightarrow M_1 \text{ in SAT}$

$$\frac{V_{SD2}}{3.33V} > \frac{V_{SG2} - V_{tp}}{2V - 1V = 1V} \checkmark \Rightarrow M_2 \text{ in SAT}$$

Now,

$$I_D = 0.258 \text{ mA}$$

$$V_{DS} = 1.67V$$

$$g_{m1} = 2\sqrt{k_n \cdot I_D} = 0.51 \frac{\text{mA}}{\text{V}}$$


$$r_{o1} = \frac{1}{\lambda_1 I_{DQ}} = 193.8 \text{ k}\Omega$$

$$g_{m2} = 2\sqrt{k_p \cdot I_D} = 0.51 \frac{\text{mA}}{\text{V}}$$

$$r_{o2} = \frac{1}{\lambda_2 I_{DQ}} = 387.6 \text{ k}\Omega$$

①

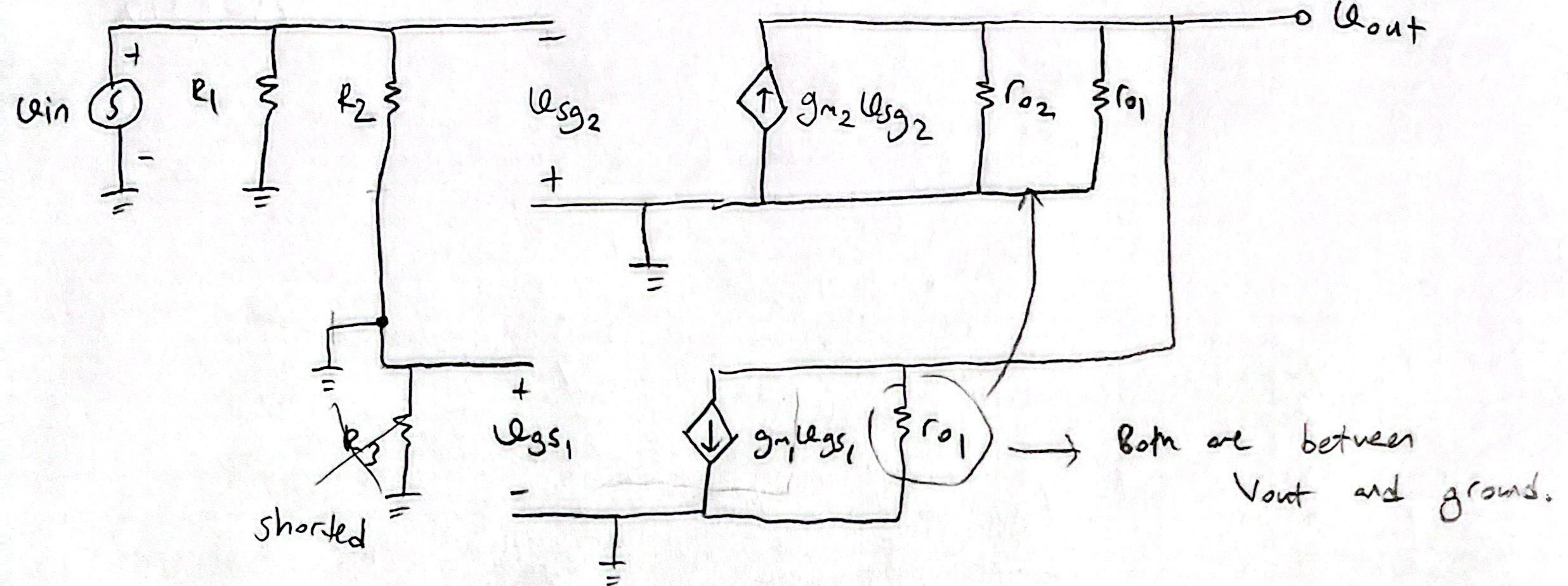b) In the small signal analysis, the capacitors will become shorted:



Note that  $U_{g_1} = U_{s_1} = 0 \Rightarrow U_{gs_1} = 0, g_{m_1} U_{gs_1} = 0 \rightarrow$  Nothing to do with M1.

Now,

$$U_{in} = -U_{sg_2} \quad \text{and} \quad U_{out} = g_{m_2} U_{sg_2} (r_{o_2} \parallel r_{o_1})$$


$$\Rightarrow \boxed{A_v = \frac{U_{out}}{U_{in}} = -g_{m_2} (r_{o_1} \parallel r_{o_2})} \Rightarrow \boxed{A_v = -65.892 \frac{V}{V}}$$

$$c) \boxed{R_{in} = R_1 \parallel R_2 = 200k \parallel 100k = 66.67k\Omega}$$

To find  $R_{out}$ , kill  $U_{in}$ , then  $U_{sg_2} = 0 \Rightarrow g_{m_2} U_{sg_2} = 0$ , open-circuit it

$$\Rightarrow \boxed{R_{out} = r_{o_2} \parallel r_{o_1} = 129.2 k\Omega}$$

(2) a) DC analysis → Open circuit caps

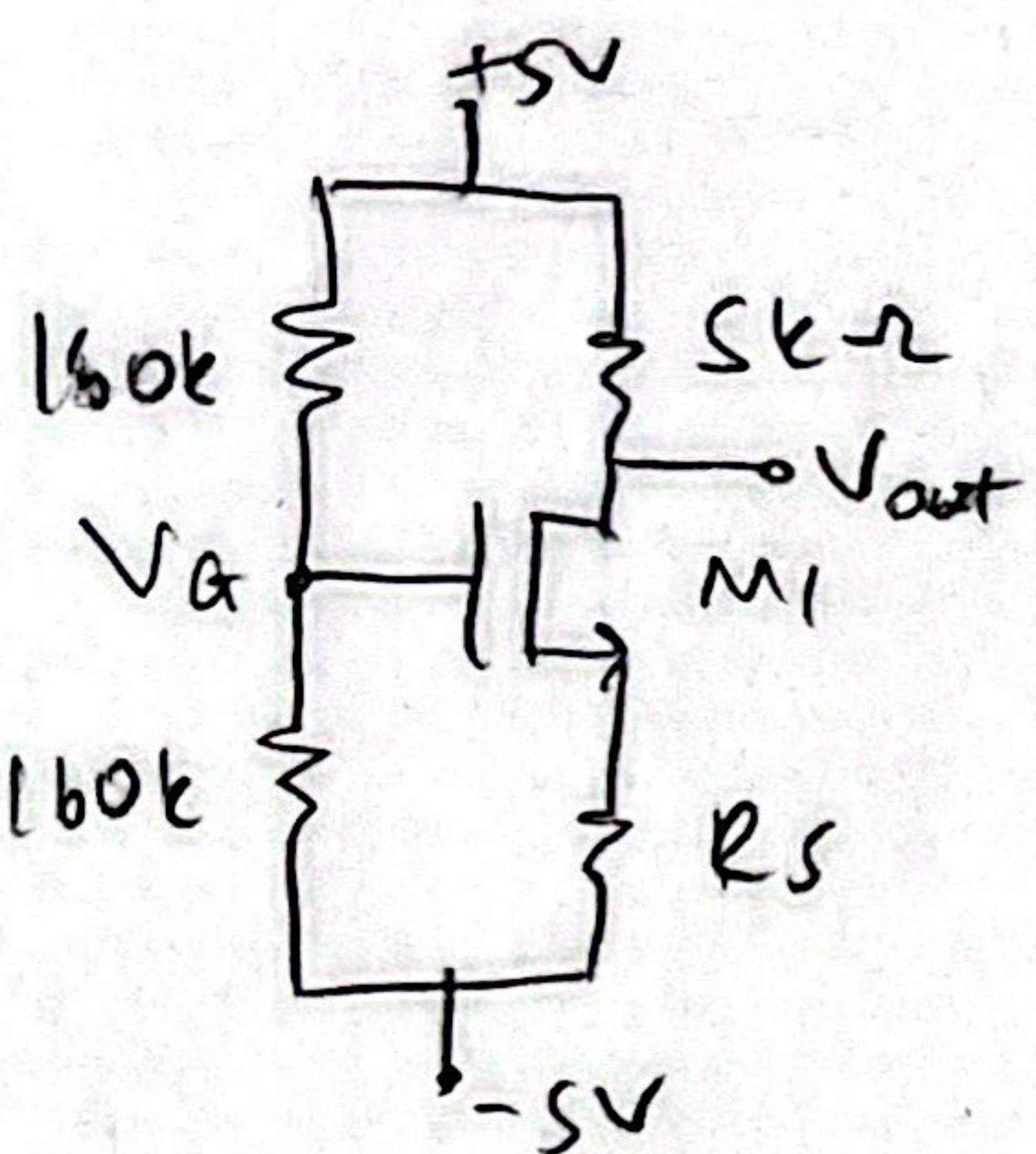

$$V_G = 5V \cdot \frac{160k}{320k} + (-5V) \cdot \frac{160k}{320k} = 0V \quad (\text{voltage divider})$$

superposition

$$V_S = I_D R_S - 5 \rightarrow V_{out} = V_{DS} + I_D R_S - 5 \Rightarrow V_{GS} = -I_D R_S + 5$$

or  $V_{out} = 5 - 5I_D$  by KVL

$$V_{out} = 5 - 5I_D = 0 \Rightarrow I_D = 1 \text{ mA} \quad \text{for } V_{out} = 0$$

$$\Rightarrow \text{Assume SAT: } I_D = k_n (V_{GS} - V_{th})^2 = 1 \text{ mA}$$

$$= 0.25(4 - I_D R_S)^2 = 1 \text{ mA}$$

$$\Rightarrow (4 - R_S)^2 = 4 \Rightarrow R_S = 12 \text{ k}\Omega \quad \text{we need } V_{GS} > V_{th}$$

$$\Rightarrow R_S = 12 \text{ k}\Omega \quad \text{for } V_{out} = 0 \text{ V DC.}$$

$$\text{or } R_S = 6 \text{ k}\Omega$$


Check:

$$V_{DS} = 5 - I_D R_S = 3V$$

$$V_{GS} = 5 - I_D R_S = 3V$$

$$V_{DS} > V_{GS} - V_{th} \Rightarrow \text{SAT}$$

b) S.S model:

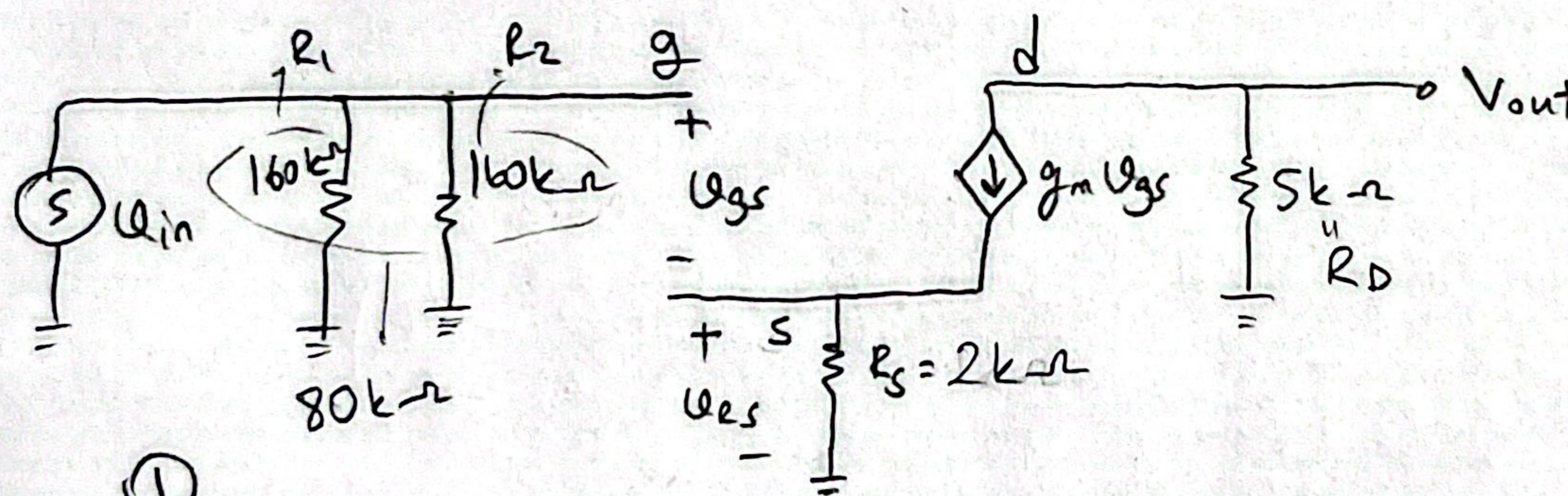

①

$$V_{out} = -g_m u_{gs} R_D, \quad u_{es} = g_m u_{gs} R_S$$


$$\text{by KVL: } u_{in} = u_{gs} + u_{es} = u_{gs}(1 + g_m R_S)$$

$$\Rightarrow u_{gs} = \frac{u_{in}}{1 + g_m R_S}, \quad \text{Insert into (1): } V_{out} = -g_m R_D \frac{u_{in}}{1 + g_m R_S}$$

$$A_V = \frac{V_{out}}{u_{in}} = -\frac{g_m R_D}{1 + g_m R_S}$$

$$\Rightarrow A_V = -\frac{1(5k\Omega)}{1 + (1)(2)} = -\frac{5}{3} \text{ V/V} \approx -1.67 \text{ V/V}$$

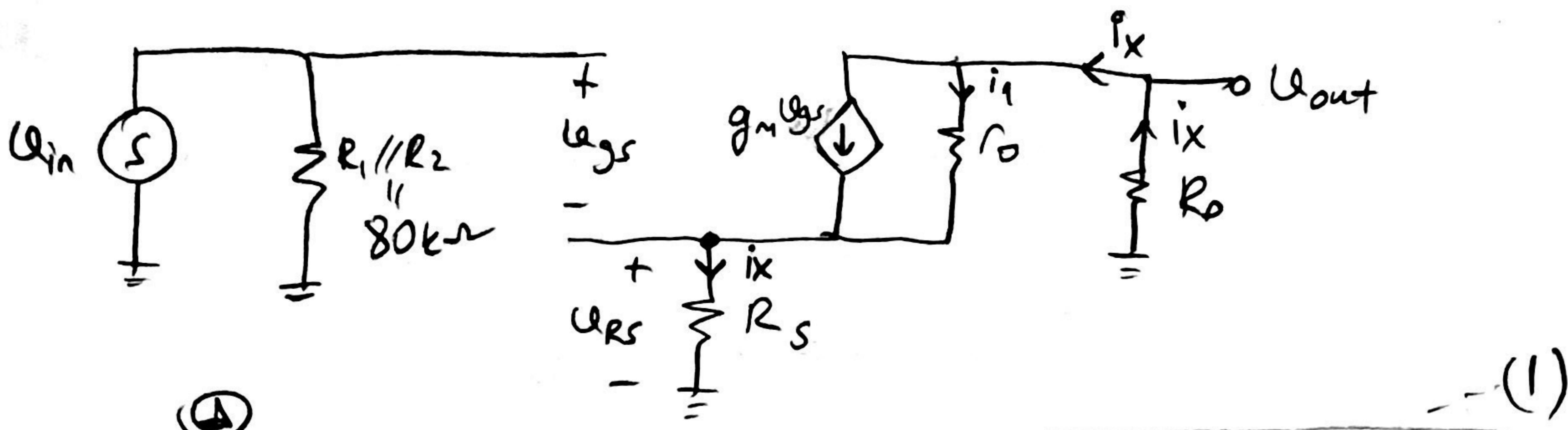c)  $r_o = 100k\Omega$  from previous part.  
S.S model with  $r_o$ :



$$\textcircled{1} \quad U_{gs} = U_{in} - U_{Rs}$$

$$\text{and } i_x = g_m U_{gs} + \frac{U_{out} - U_{Rs}}{r_o} \quad (\text{KCL at } V_{out})$$

$\Rightarrow$  We also know that  $U_{Rs} \geq R_s \cdot i_x$ , insert into (1):

$$i_x = g_m U_{gs} + \frac{U_{out} - R_s i_x}{r_o} \Rightarrow i_x = g_m U_{in} - g_m R_s i_x + \frac{U_{out}}{r_o} - \frac{R_s}{r_o} i_x$$

$$\text{from } \textcircled{1} \quad U_{in} - R_s i_x$$

$$\Rightarrow i_x \left( 1 + g_m R_s + \frac{R_s}{r_o} \right) = g_m U_{in} + \frac{U_{out}}{r_o}$$

$$\Rightarrow i_x = \frac{g_m U_{in} + \frac{U_{out}}{r_o}}{1 + g_m R_s + \frac{R_s}{r_o}}$$

Now,  $U_{out} = -R_o \cdot i_x$

$$\Rightarrow U_{out} = -R_o \left( \frac{g_m U_{in} + \frac{U_{out}}{r_o}}{1 + g_m R_s + \frac{R_s}{r_o}} \right) \Rightarrow U_{out} \left( 1 + g_m R_s + \frac{R_s}{r_o} + \frac{R_o}{r_o} \right) = -U_{in} (g_m R_o)$$

$$\Rightarrow A_V = \frac{U_{out}}{U_{in}} = - \frac{g_m R_o}{1 + g_m R_s + \frac{R_o + R_s}{r_o}}$$

Note that as  $\lambda \rightarrow 0, r_o \rightarrow \infty$  ( $r_o = \frac{1}{\lambda I_D}$ )

$$\Rightarrow \lim_{r_o \rightarrow \infty} A_V = \frac{-g_m R_o}{1 + g_m R_s + \lim_{r_o \rightarrow \infty} \frac{R_o + R_s}{r_o}} = \frac{-g_m R_o}{1 + g_m R_s} \quad (\text{same as part b})$$

$$\Rightarrow A_V = - \frac{(1)(5k\Omega)}{1 + (1)(2k\Omega) + \frac{7}{100k\Omega}} = \frac{-5}{3 + 0.07} = -1.63 \text{ V/V}$$

d)  $R_{in} = R_1 // R_2 = 80 \text{ k}\Omega$

To find  $R_{out}$ , kill  $(\text{in})$ :

$$U_{gs} = U_g - U_s = -U_s = -I_{ds} R_{ds}$$

KCL at A:  $I_X = \frac{V_x - U_s}{R_o} + g_m U_{gs}$

$$\Rightarrow I_X = \frac{V_x - U_s}{R_o} - g_m U_s$$

and  $\boxed{U_s = I_X R_S}$ , insert:

$$\Rightarrow I_X = \frac{V_x - I_X R_S}{R_o} - g_m R_S I_X$$

$$\Rightarrow I_X \left( 1 + g_m R_S + \frac{R_S}{R_o} \right) = \frac{V_x}{R_o}$$


$$\Rightarrow R_{out} = \frac{V_x}{I_X} = R_o \left( 1 + g_m R_S \right) + R_S$$

Finally  $\boxed{R_{out} = R_{out} // R_D}$

$$= (R_o (1 + g_m R_S) + R_S) // R_D$$

$$\Rightarrow R_{out} = 4.89 \text{ k}\Omega$$

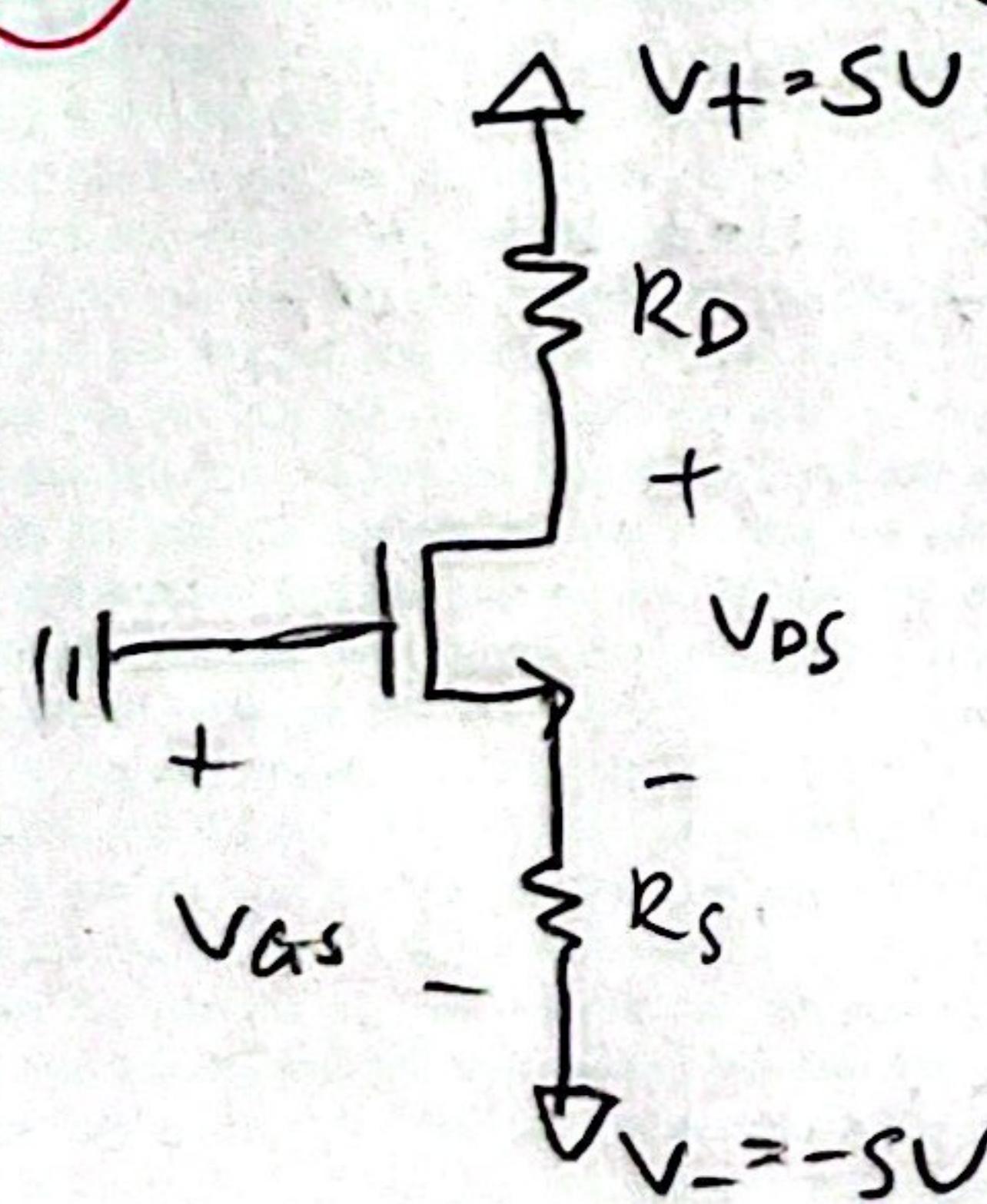③ a) DC analysis  $\rightarrow$  Open circuit ops.



Assume SAT, we want  $I_{DQ} = 0.2 \text{ mA}$  and  $V_{DQ} = 1 \text{ V}$

$$\text{KVL: } 10 = \underbrace{I_{DQ}}_{0.2 \text{ mA}} (R_D + R_S) + \underbrace{V_{DQ}}_{1 \text{ V}}$$

$$\Rightarrow \boxed{R_D + R_S = 45 \text{ k}\Omega}$$

and  $I_D = K_n (V_{GS} - V_m)^2$ ,  $V_{GS} = V_G - V_S$

$$\Rightarrow 0.2 = 0.5 (V_{GS} - 1)^2 = 5 - I_D R_S$$

$$\Rightarrow (V_{GS} - 1)^2 = \frac{2}{5} \Rightarrow V_{GS} = 1.63 \text{ V}$$

(to have  $V_{GS} > V_m$ , take the bigger root)

and  $V_{GS} = 5 - I_D R_S \Rightarrow 5 - 0.2 R_S = 1.63$


$$\Rightarrow \boxed{R_S = 16.85 \text{ k}\Omega}$$

$$g_m = 2 \sqrt{K_n I_D} = 0.632 \text{ mA/V}$$

$$r_o = \frac{1}{g_m I_D} = 500 \text{ k}\Omega$$

$$\Rightarrow \boxed{R_D = 45 - R_S = 28.15 \text{ k}\Omega}$$

b) S.S model:

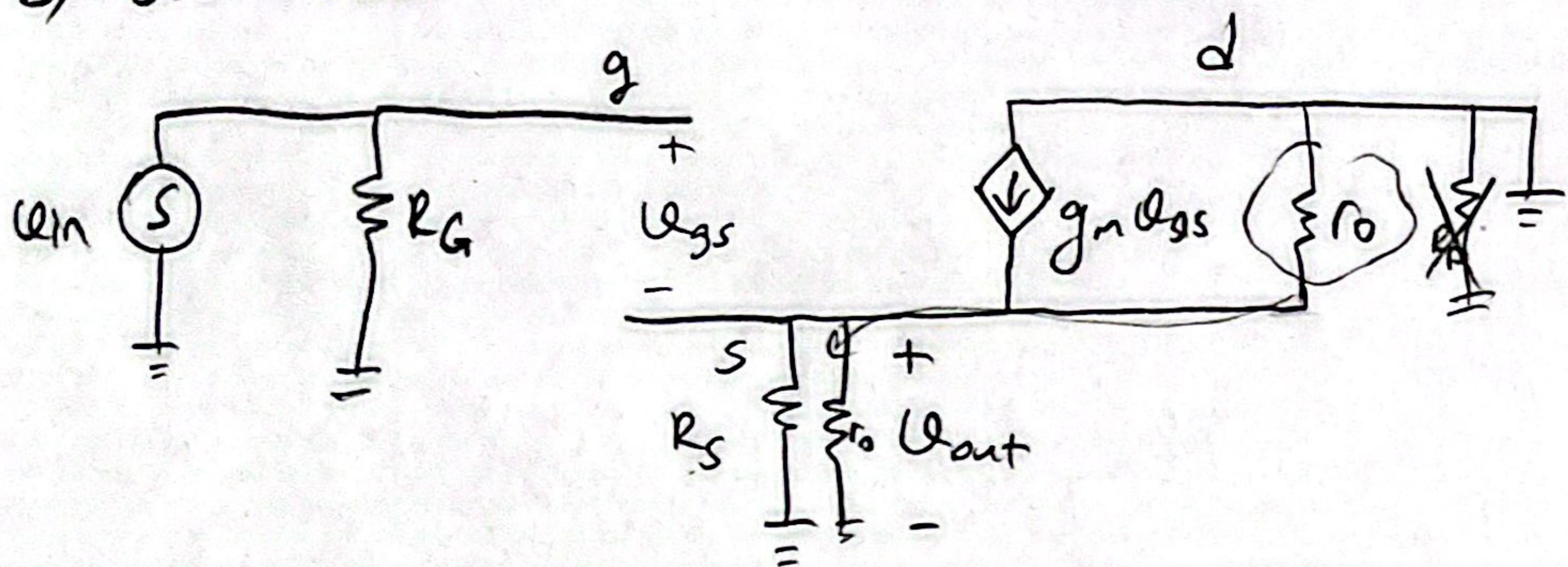

We can move  $r_o$  parallel with  $R_S$  since they are both connected between  $V_{out}$  and ground.

$$\Rightarrow V_{out} = g_m V_{gs} (R_S \parallel r_o) \quad \dots (1)$$

KCL:  $V_{in} = V_{gs} + V_{out}$

$$\Rightarrow V_{gs} = V_{in} - V_{out} \rightarrow \text{insert into (1):}$$


$$\Rightarrow V_{out} = g_m (R_S \parallel r_o) \cdot (V_{in} - V_{out})$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = \frac{g_m (R_S \parallel r_o)}{1 + g_m (R_S \parallel r_o)}$$

$$\Rightarrow A_v = \frac{0.632 (500 \parallel 16.85)}{1 + 0.632 (500 \parallel 16.85)} = \frac{0.632}{1 + 0.632} = 0.91 \frac{V}{V}$$

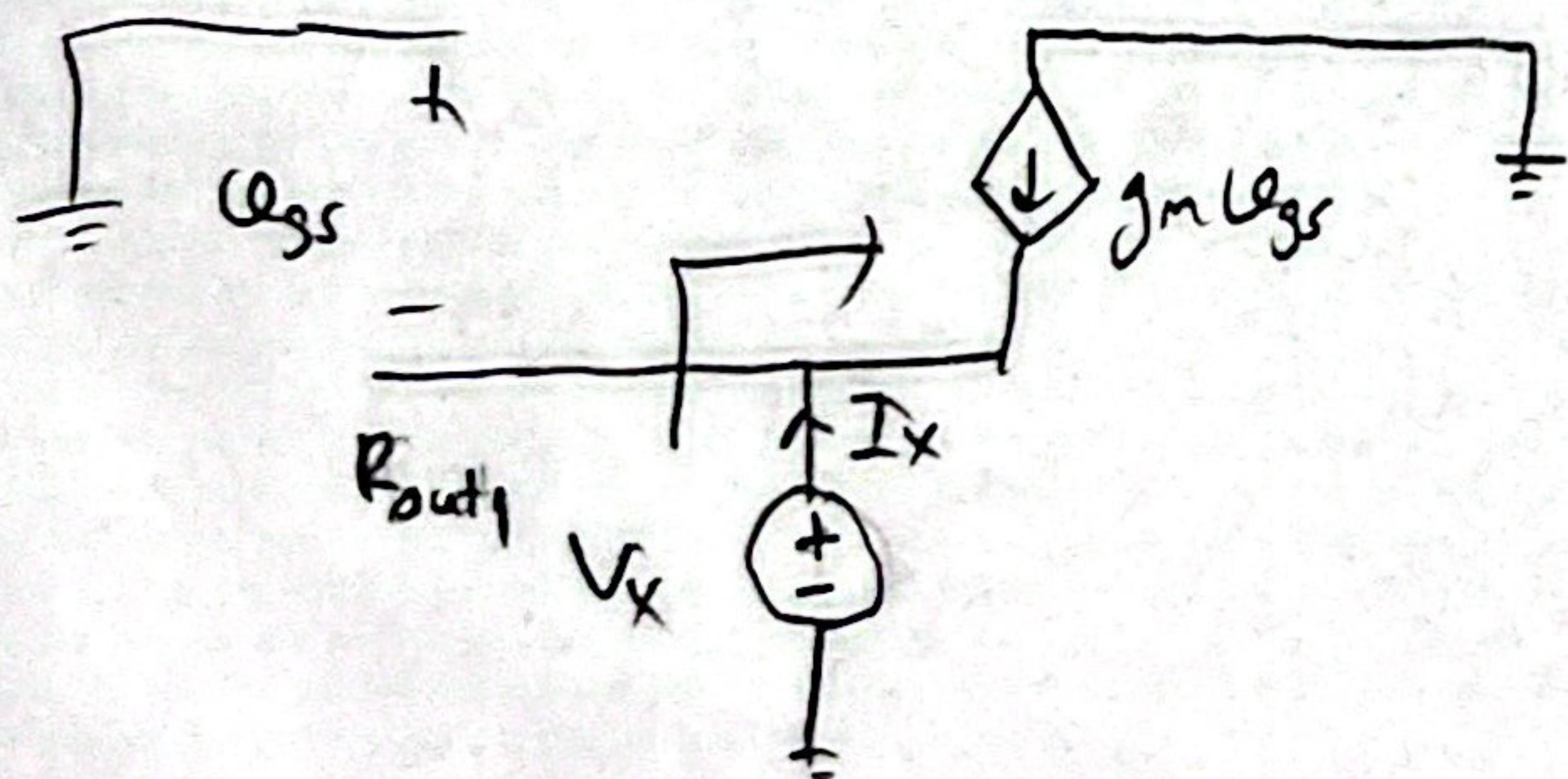c)  $R_{in} = R_G = 5M\Omega$ .

To find  $R_{out}$ : Kill  $V_{in}$ , determine  $R_{out}$  first (look from the source):



we know that  $V_{gs} = V_g - V_s = -V_s$   
and  $V_s = V_x$

$$\Rightarrow V_{gs} = -V_x$$

KCL at source:

$$I_x = -g_m V_{gs} = g_m V_x$$


$$\Rightarrow R_{in} = \frac{V_x}{I_x} = \frac{1}{g_m}$$

Now,  $R_{out} = R_{out} \parallel r_o \parallel R_S$

$$\Rightarrow R_{out} = \frac{1}{g_m} \parallel r_o \parallel R_S$$

$$R_{out} = \left( 0.632 + \frac{1}{100} + \frac{1}{16.85} \right)^{-1} = 1.426 k\Omega$$


d) Black box model:

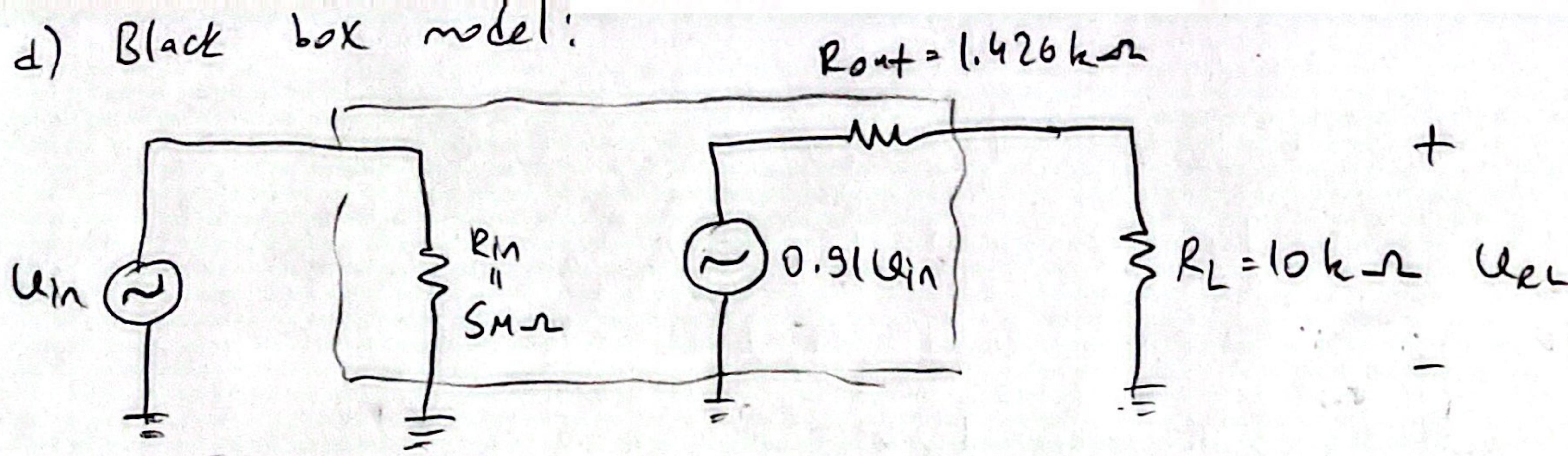

$$\text{Voltage divider: } \frac{u_{out}}{u_{in}} = \frac{R_L}{R_L + R_{out}} (0.91) u_{in} = 0.796 u_{in}$$

$$\Rightarrow A_v = \frac{u_{out}}{u_{in}} = 0.796 \frac{\text{V}}{\text{V}}$$

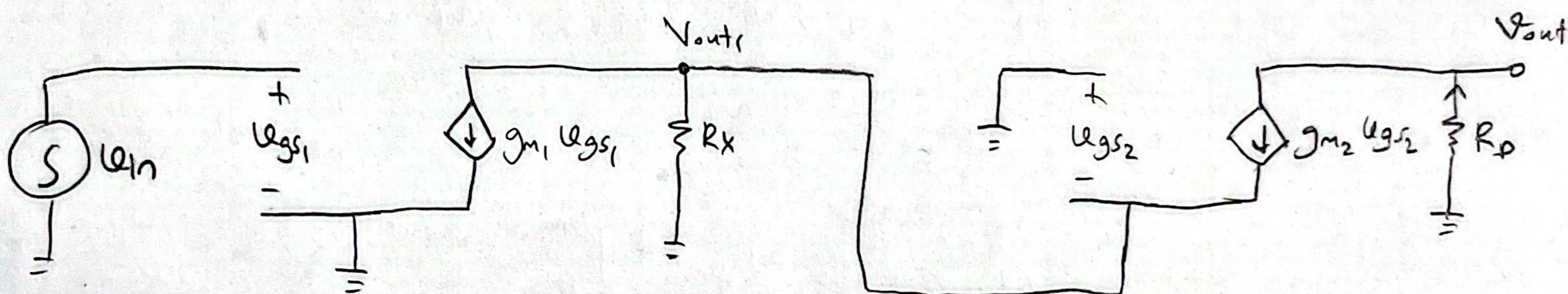④ Small signal model: (No DC analysis since assumed SAT and  
g\_m's are given)



$$\text{First, } V_{out} = -g_{m2} u_{gs2} R_D \text{ and } u_{gs2} = -V_{out}, \text{ since } u_{g2} = 0$$

$$\Rightarrow u_{out} = g_{m2} u_{out1} R_D \Rightarrow u_{out1} = u_{out} \frac{1}{g_{m2} R_D}$$

$$\text{Now, KCL at } V_{out1}: g_{m1} u_{gs1} + \frac{u_{out1}}{R_X} - g_{m2} u_{gs2} = 0$$

$$u_{in} = u_{gs1}$$


$$-u_{out1} = u_{gs2}$$

$$\Rightarrow g_{m1} u_{in} = -u_{out1} \left( \frac{1}{R_X} + g_{m2} \right)$$

$$g_{m1} u_{in} = -u_{out} \left( \frac{1}{R_D} \left( \frac{1}{g_{m2} R_X} + 1 \right) \right)$$

$$\Rightarrow \frac{u_{out}}{u_{in}} = - \frac{g_{m1} g_{m2} R_D R_X}{1 + g_{m2} R_X}$$

⑤ a) In DC, open circuit op-s:

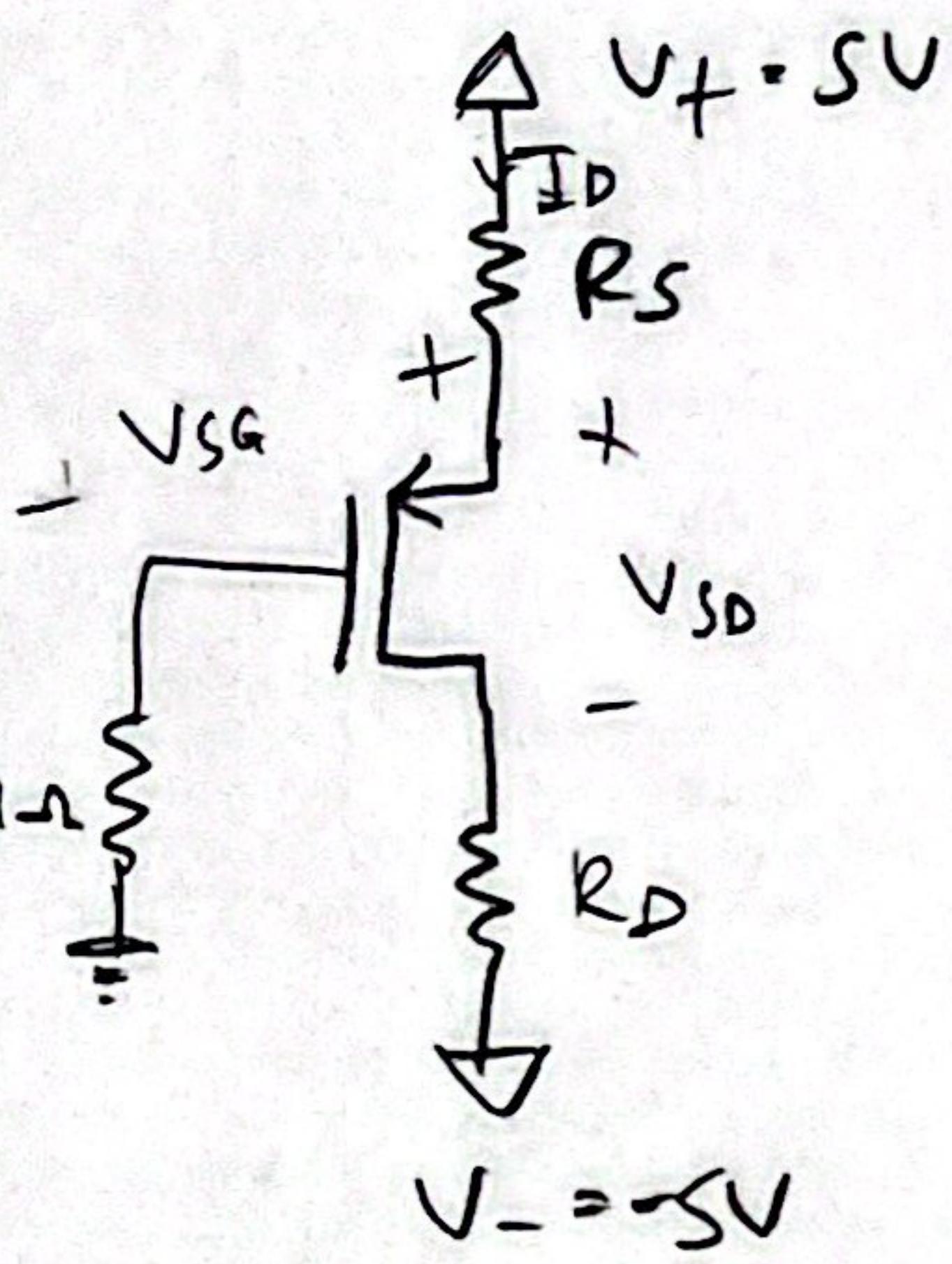

$$V_s = 5 - I_d R_s \\ = 5 - 0.5 R_s$$

$$\Rightarrow V_{SG} = 5 - 0.5 R_S$$

To have  $V_{SD} = SV$ , apply KVL

$$I_D = V_{SD} + I_d (R_S + R_D)$$

$$I_D = S + O.S (R_S + R_D)$$

$$\Rightarrow R_S + R_D = 10 \text{ k}\Omega$$

and  $I_{DQ} = K_P (V_{SG} - \frac{|V_{tpl}|}{V})^2$ , assuming SAT.

$$\Rightarrow O.S = O.S (4 - 0.5 R_S)^2$$

$$\Rightarrow R_S = 6 \text{ k}\Omega \quad \text{or} \quad R_S = 10 \text{ k}\Omega$$


$$\Rightarrow R_D = 4 \text{ k}\Omega$$

$$\text{Check! : } V_s = 5 - (0.5) 6 = 2 \text{ V}$$

$$V_{SG} = 2 \text{ V}, \quad V_{SD} = 5 \text{ V}$$

$$\frac{V_{SD}}{SV} > \frac{V_{SG} - |V_{tpl}|}{2V - 1V} \Rightarrow \text{SAT} \checkmark$$

b) s.s model:

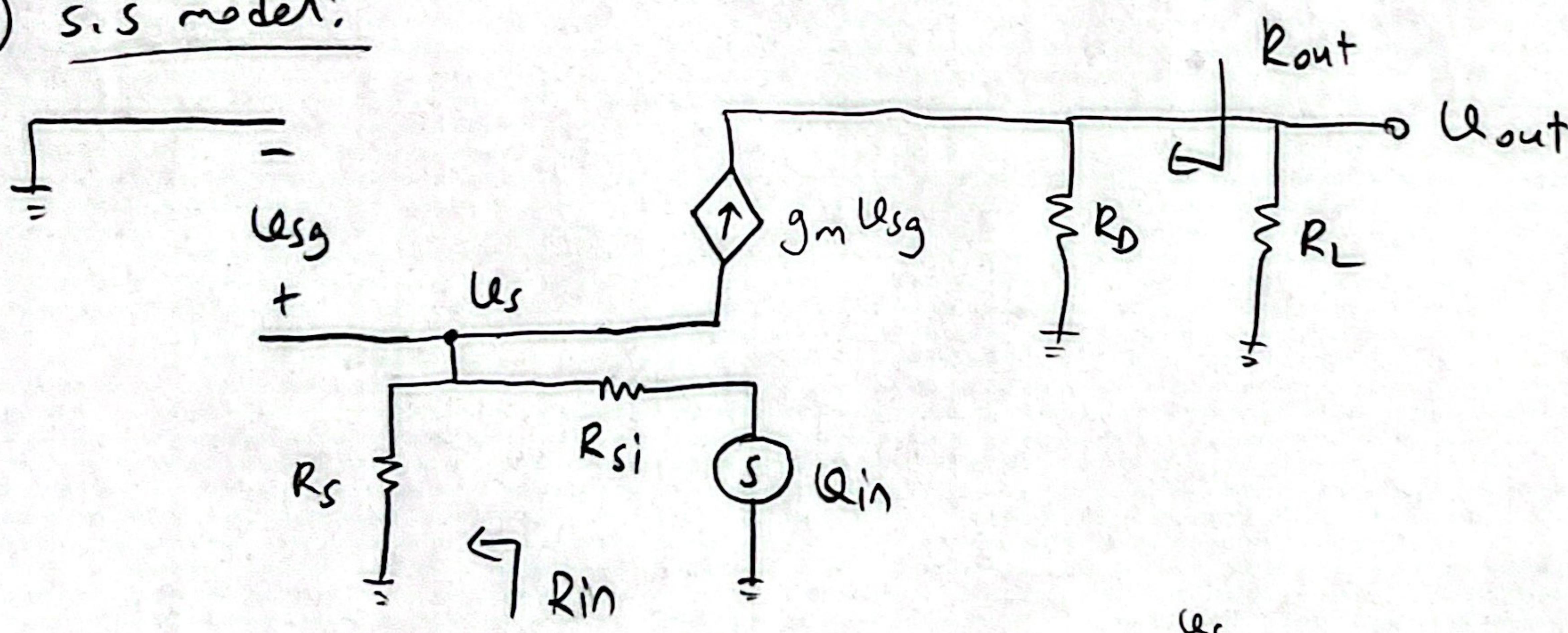

$$\text{First, KCL at } u_s: \quad \frac{u_s}{R_s} + \frac{u_s - u_{in}}{R_{si}} + g_m(u_{sg}) = 0 \quad \text{and } u_{sg} = u_s \text{ since } u_{sg} \approx 0$$

$$\Rightarrow u_s \left( \frac{1}{R_s} + \frac{1}{R_{si}} + g_m \right) \cdot R_{si} = u_{in}$$


$$\text{and } u_{out} = g_m u_{sg} (R_D // R_L) = g_m u_s (R_D // R_L) \\ = g_m (R_D // R_L) \cdot \frac{1}{R_{si} \left( \frac{1}{R_s} + \frac{1}{R_{si}} + g_m \right)} \cdot u_{in}$$

$$\Rightarrow A_V = \frac{u_{out}}{u_{in}} = \frac{g_m (R_D // R_L)}{1 + g_m R_{si} + \frac{R_{si}}{R_s}}$$

$$g_m = 2 \sqrt{\frac{K_p}{O.S} I_D} = 1 \text{ mA/V}$$

$$\Rightarrow A_V = \frac{2k // 4k}{1 + 1 \cdot (50k) + \frac{50k}{6k}} = 0.0225 \frac{\text{V}}{\text{V}}$$

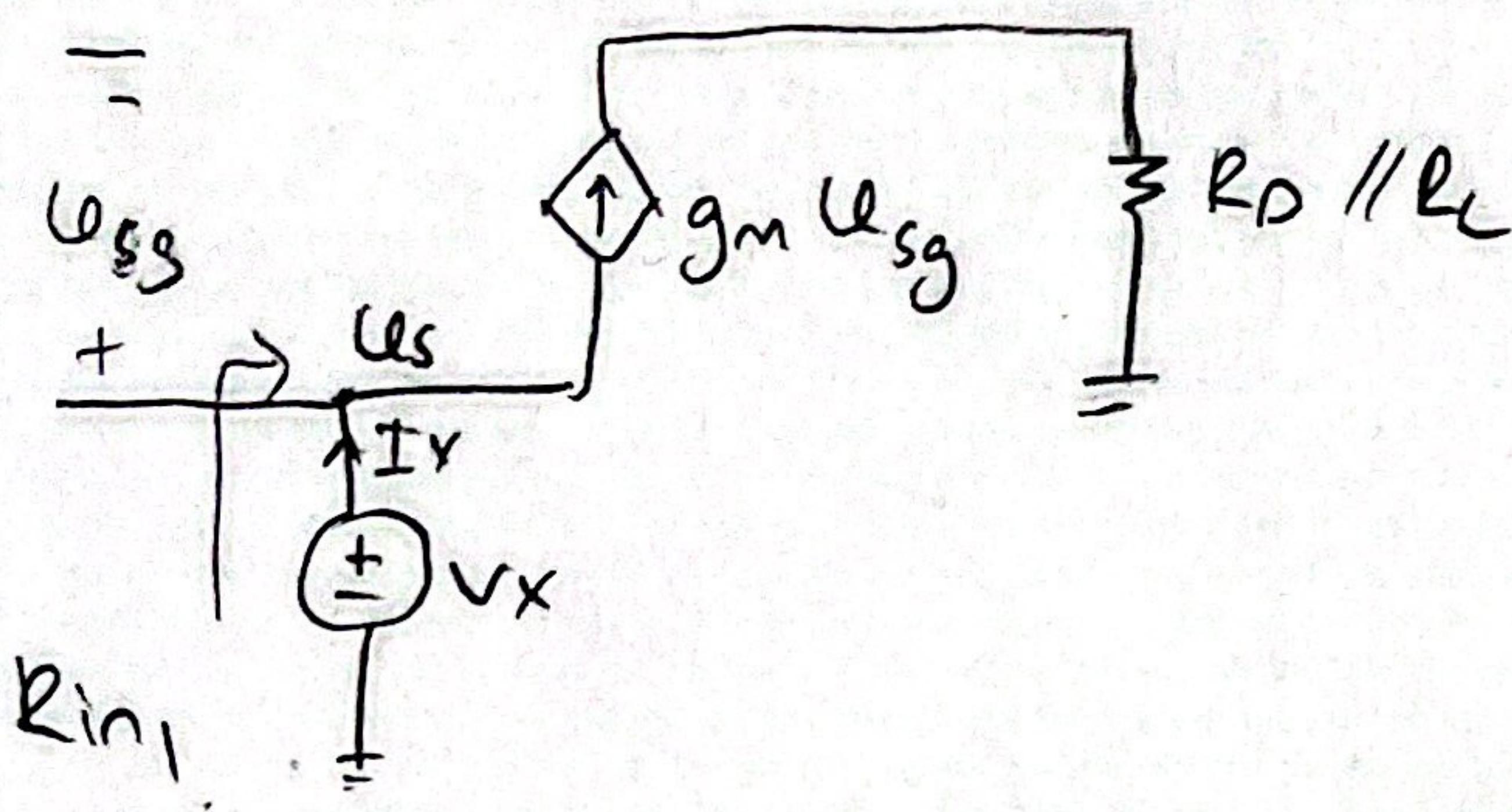To find  $R_{in}$ , first ignore  $R_s$ :



$$U_{sg} = U_s \text{ and } U_s = V_x \Rightarrow U_{sg} = V_x$$

KCL at source:  $I_x = g_m U_{sg} = g_m V_x$


$$\Rightarrow R_{in} = \frac{V_x}{I_x} = \frac{1}{g_m}$$

Now,

$$R_{in} = R_{in_1} // R_s = \frac{1}{g_m} // R_s$$

$$\Rightarrow R_{in} = \frac{b}{7} k\Omega \approx 0.86 k\Omega$$

To find  $R_{out}$ , kill  $R_{in}$ :

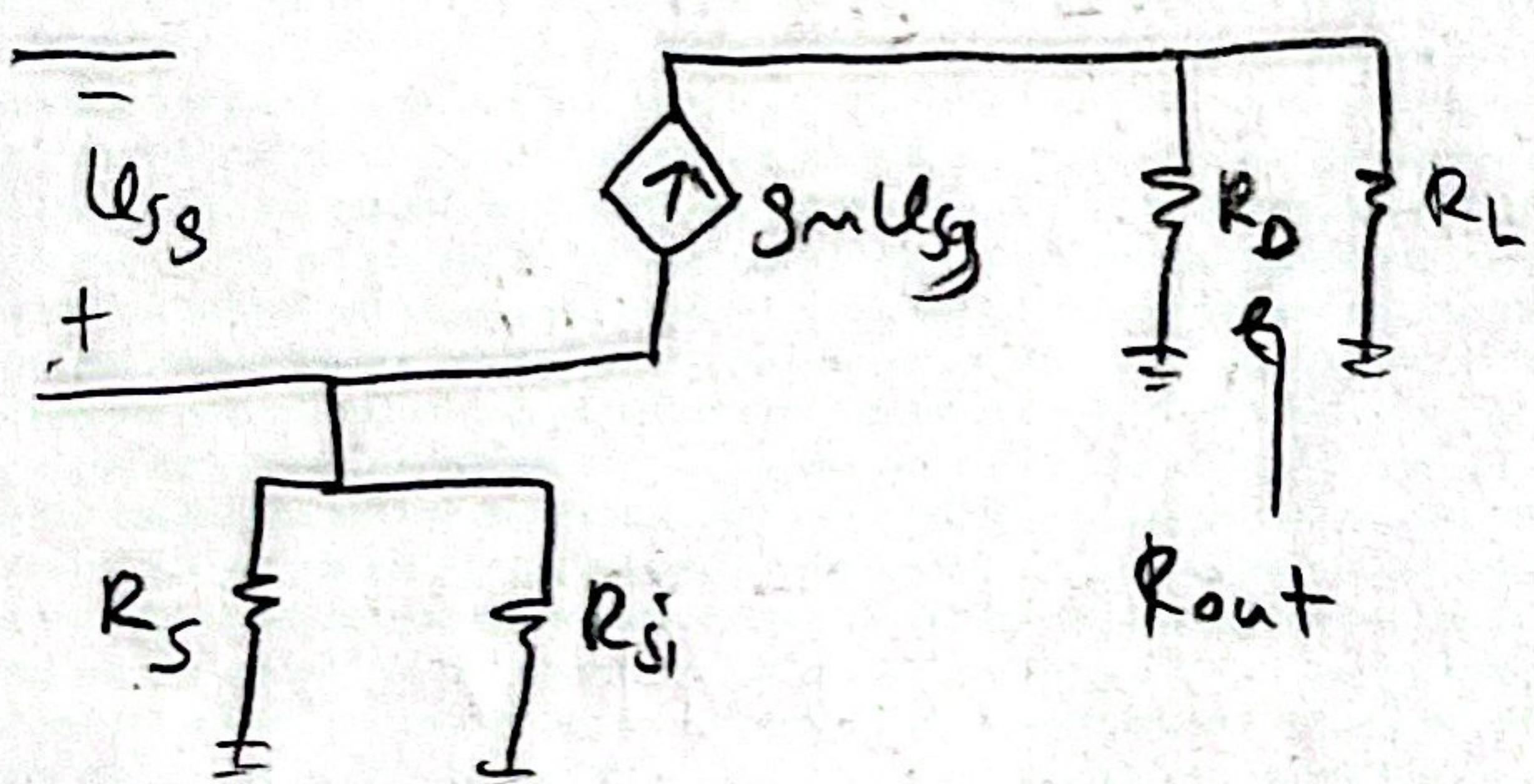

$$U_{sg} = 0 \text{ since } U_s = 0$$

$$\Rightarrow g_m U_{sg} = 0, \text{ open-circuit if}$$

$$\Rightarrow R_{out} = R_D = 4 k\Omega$$

c) Gain was calculated as  $0.0225$  from prev. part

$$\Rightarrow U_{out} = (R_{in} / 0.0225) = 0.011 \text{ mV cos (wt)}$$

and

$$i_{out} = \frac{U_{out}}{R_L} = 5.625 \text{ nA cos (wt)}$$

(6) a) For M1:

Assume SAT:

$$\Rightarrow I_{D1} = K_{n1} (V_{GS1} - V_{th})^2$$

$$\Rightarrow I_D = 0.1 (4 - 30 I_{D1})^2$$

$$I_D = 0.178 \text{ mA or } \boxed{I_D = 0.1 \text{ mA}}$$

since we need  $V_{GS1} > V_{th}$

$$\Rightarrow V_{GS1} = 5 - (0.1)(30) = 2 \text{ V}$$

$$\Rightarrow V_{DS1} = 2 \text{ V}$$

Check:  $\frac{V_{DS1}}{2 \text{ V}} > \frac{V_{GS1} - V_{th}}{1 \text{ V}} \Rightarrow M1 \text{ in } \boxed{\text{SAT}}$  (Diode connected)

$$\Rightarrow \boxed{I_{D1} = 0.1 \text{ mA}}, \boxed{V_{G1} = V_{D1} = 2 \text{ V}}$$

For M2: Assume SAT

$$\boxed{V_{G2} = 2 \text{ V}} \quad V_{S2} = (1.17) I_{D2} \Rightarrow V_{GS2} = 2 - 1.17 I_{D2}$$

$$I_{D2} = K_{n2} (V_{GS2} - V_{th})^2 = 0.5 (1 - 1.17 I_{D2})^2$$

$$\Rightarrow \boxed{I_{D2} = 0.25 \text{ mA}} \text{ or } \cancel{I_{D2} = 2.92 \text{ mA}} \Rightarrow \boxed{V_{GS2} = 1.71 \text{ V}}$$

we need  $V_{GS2} > V_{th}$

$$\boxed{V_{S2} = 0.29 \text{ V}}$$

Now, for M3 also assume SAT:

$$I_{D2} = I_{D3} = K_{n3} (V_{GS3} - V_{th})^2 \Rightarrow 0.25 = 1 (3.25 - V_{S3} - 1)^2$$

$$\boxed{V_{S3} = 1.75 \text{ V}} \text{ or } \cancel{V_{S3} = 2.75 \text{ V}}$$

since we need  $V_{GS3} > V_{th} \Rightarrow \boxed{V_{GS3} = 1.5 \text{ V}}$

Now, to find node voltages:

$V_{D3} = 5 - I_D (7k) = 5 - 7 (0.25)$

$$\Rightarrow \boxed{V_{D3} = 3.25 \text{ V}}$$

$V_{D2} = V_{S3} - I_D R_2 = 1.75 - (0.25) 1$


$$\Rightarrow \boxed{V_{D2} = 1.5 \text{ V}}$$

$$\text{Check: } V_{DS_2} = \frac{V_{D_2}}{1.5} - \frac{V_{S_2}}{0.25} = 1.21V, \quad V_{DS_3} = \frac{V_{D_3}}{3.25} - \frac{V_{S_3}}{1.75} = 1.5V$$


$$\Rightarrow \frac{V_{DS_2}}{1.21V} > \frac{V_{GS_2}}{1.7V} - \frac{V_{th}}{1V} \Rightarrow M_2 \text{ in SAT } \checkmark$$

$$\Rightarrow \frac{V_{DS_3}}{1.5V} > \frac{V_{GS_3}}{1.5V} - \frac{V_{th}}{1V} \Rightarrow M_3 \text{ in SAT } \checkmark$$

b) S.S model:

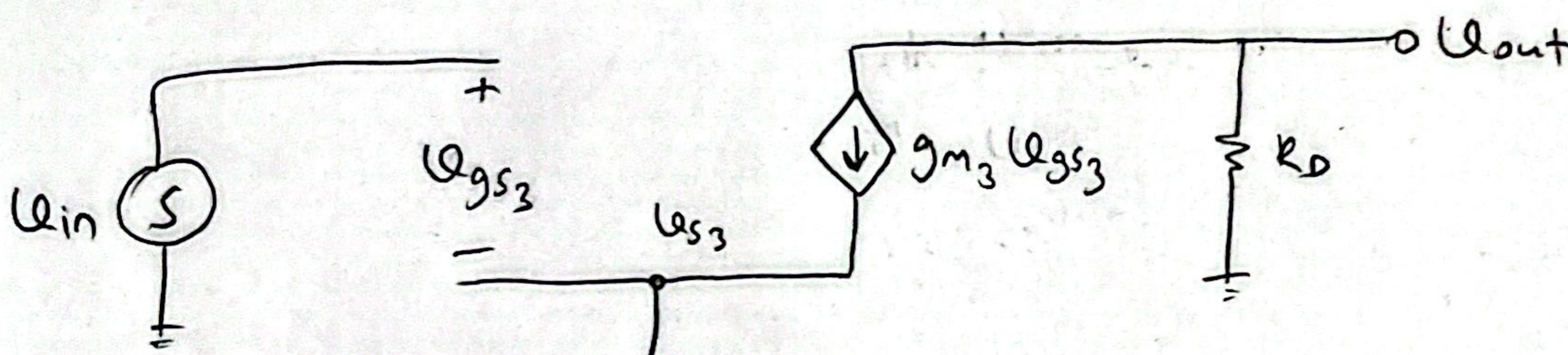

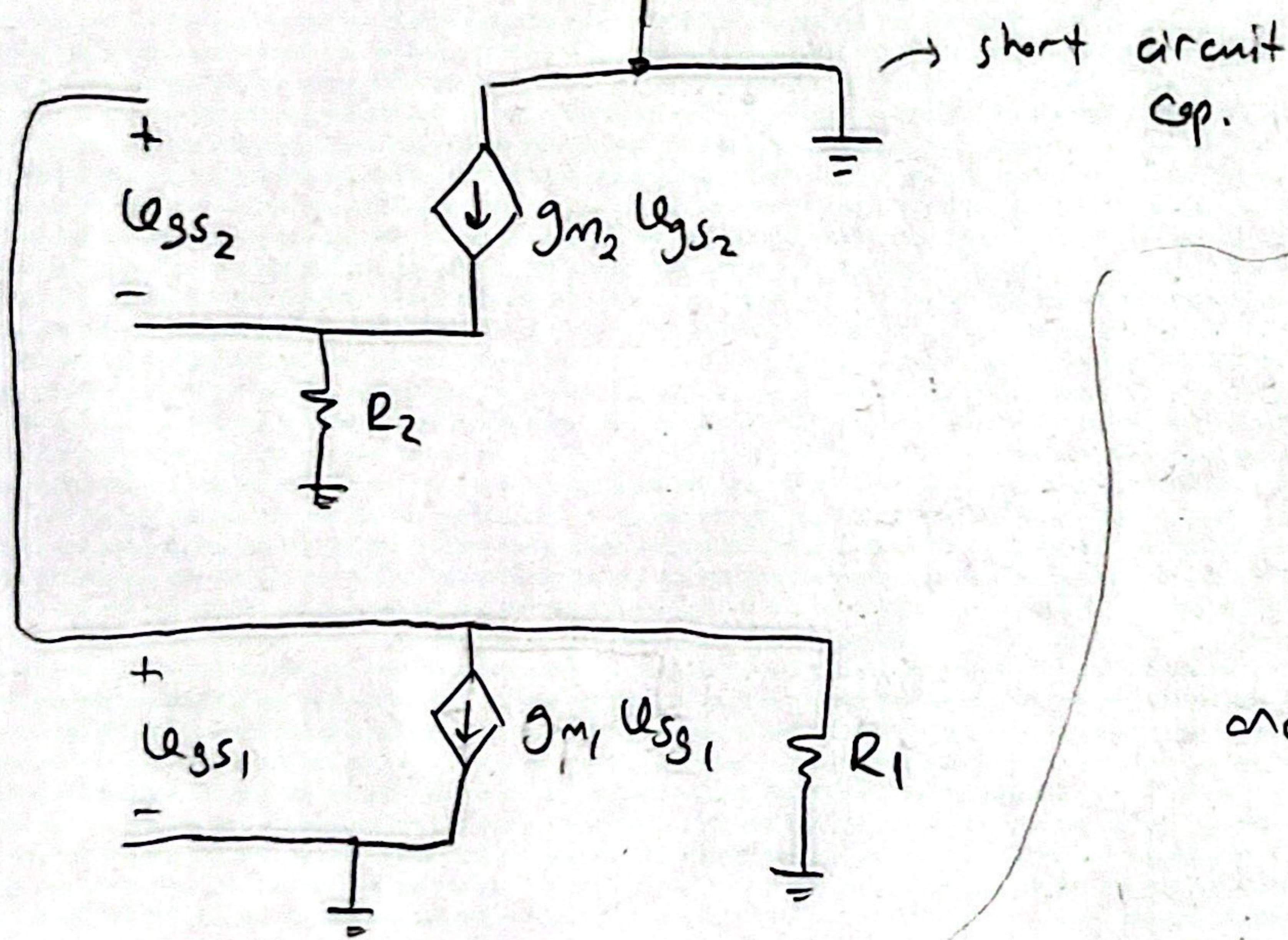$\Rightarrow M_1$  and  $M_2$  have no effect since  $R_S$  is grounded with the capacitor.



$$u_{in} = u_{gs_3} + u_{s_3}$$

$$\text{and } u_{s_3} = g_{m_2} u_{gs_3} R_S$$

$$\Rightarrow u_{in} = u_{gs_3} (1 + g_{m_2} R_S)$$

$$\text{and } u_{out} = -g_{m_3} u_{gs_3} R_D$$

$$\Rightarrow u_{gs_3} = -\frac{u_{out}}{g_{m_3} R_D}$$

$$\Rightarrow A_V = \frac{u_{out}}{u_{in}} = -\frac{g_{m_3} R_D}{1 + g_{m_2} R_S}$$

$$g_{m_3} = 2 \sqrt{k_{n_3} I_{D_2}} = 1 \text{ mA/V} \Rightarrow A_V = -\frac{7k\Omega}{1 + 1 \cdot (1k\Omega)} = -3.5 \frac{\text{V}}{\text{V}}$$