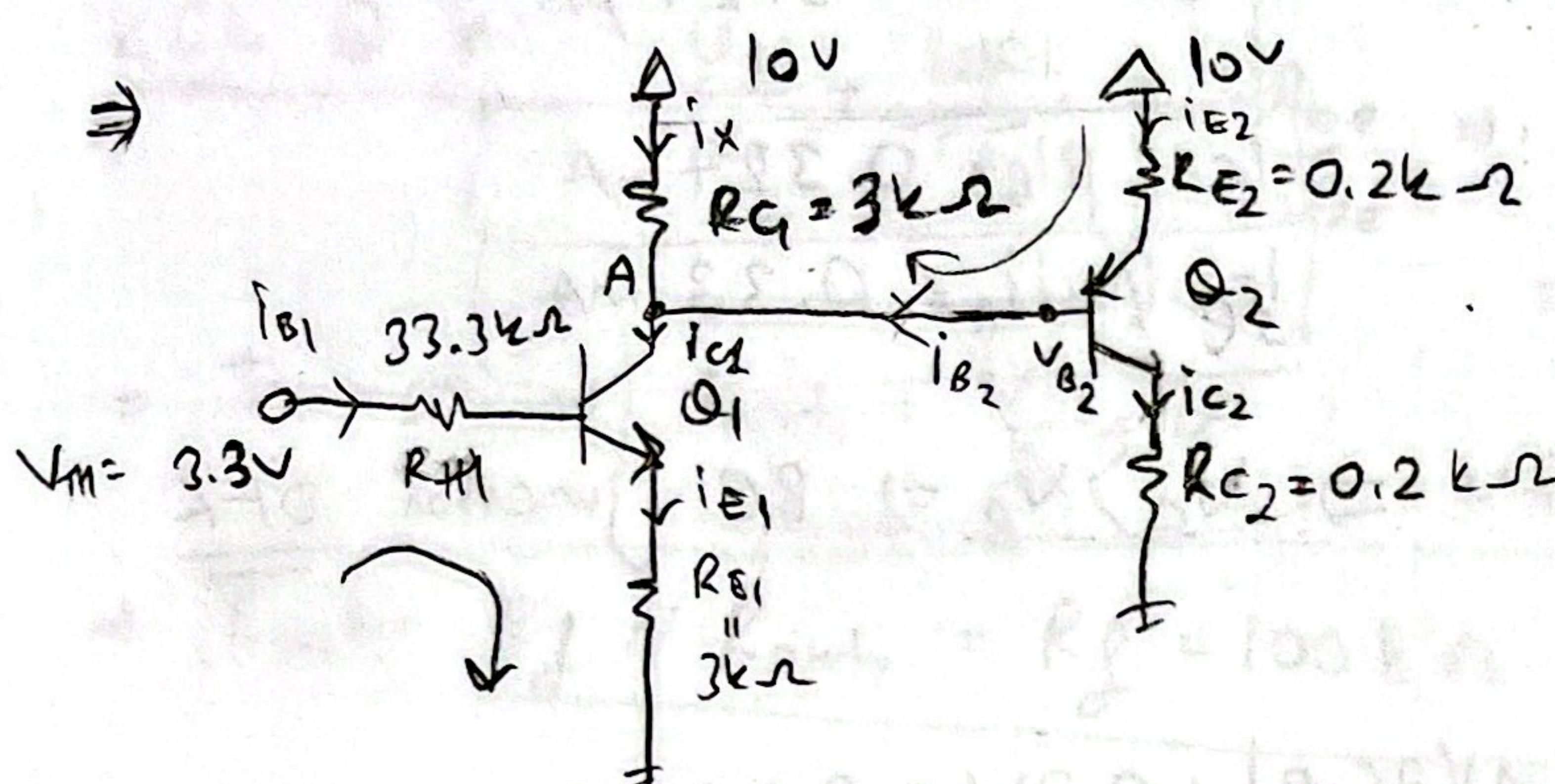


① Thévenin conversion for  $Q_1$ ,  $V_{TH} = 10V$ .  $\frac{R_1}{R_1+R_2} = 10V \cdot \frac{50k}{150k} = 3.3V$   
 $R_{TH} = (100k) // (50k) = 33.3 k\Omega$



Assume  $Q_1$  F.A.:

$$\text{KVL: } V_{TH} = i_{B1} R_{TH} + V_{BE1}(\text{ON}) + i_{E1} R_{E1} \\ (\beta+1) i_{B1}$$

$$\Rightarrow 3.3 = (33.3) i_{B1} + 0.7 + i_{B1} (101)(3)$$

$$\Rightarrow i_{B1} = 7.73 \mu A$$

$$\Rightarrow i_{E1} = (101)(7.73 \mu A) = 0.781 mA$$

$$i_{C1} = 100(7.73 \mu A) = 0.773 mA$$

$$V_A = V_{B2} = 10 - 3(i_{C1} - i_{B2}) = 7.681 + 3i_{B2} \quad \xrightarrow{\text{Note: KCL @ A:}} \quad i_x = i_{C1} - i_{B2}$$

Assume  $Q_2$  F.A.: KVL:  $10V = i_{E2} R_{E2} + V_{EB2}(\text{ON}) + V_A$

$$\Rightarrow -10 = (\beta+1) R_{E2} i_{B2} + 0.7 + 7.681 + 3i_{B2}$$

$$\Rightarrow i_{B2} = 69.8 \mu A$$

$$\Rightarrow i_{E2} = (101)(69.8 \mu A) = 7.05 mA$$

$$\Rightarrow i_{C2} = 100(69.8 \mu A) = 6.98 mA$$


$$\text{Check: } Q_2: V_{EC} = 10 - (0.2)(7.05) - (0.2)(6.98) = 7.194V \quad V_{CE(\text{SAT})} = 0.2V$$

$\Rightarrow Q_2 \text{ in F.A.} \checkmark$

$$Q_1: V_{CE} = 10 - \overbrace{\frac{R_{C1}}{3}(0.773 - 0.0698)}^{i_x} - \overbrace{\frac{R_{E1}}{3}(0.781)}^{i_{E1}} = 5.547V > V_{CE(\text{SAT})} = 0.2V$$

$\Rightarrow Q_1 \text{ in F.A.} \checkmark$

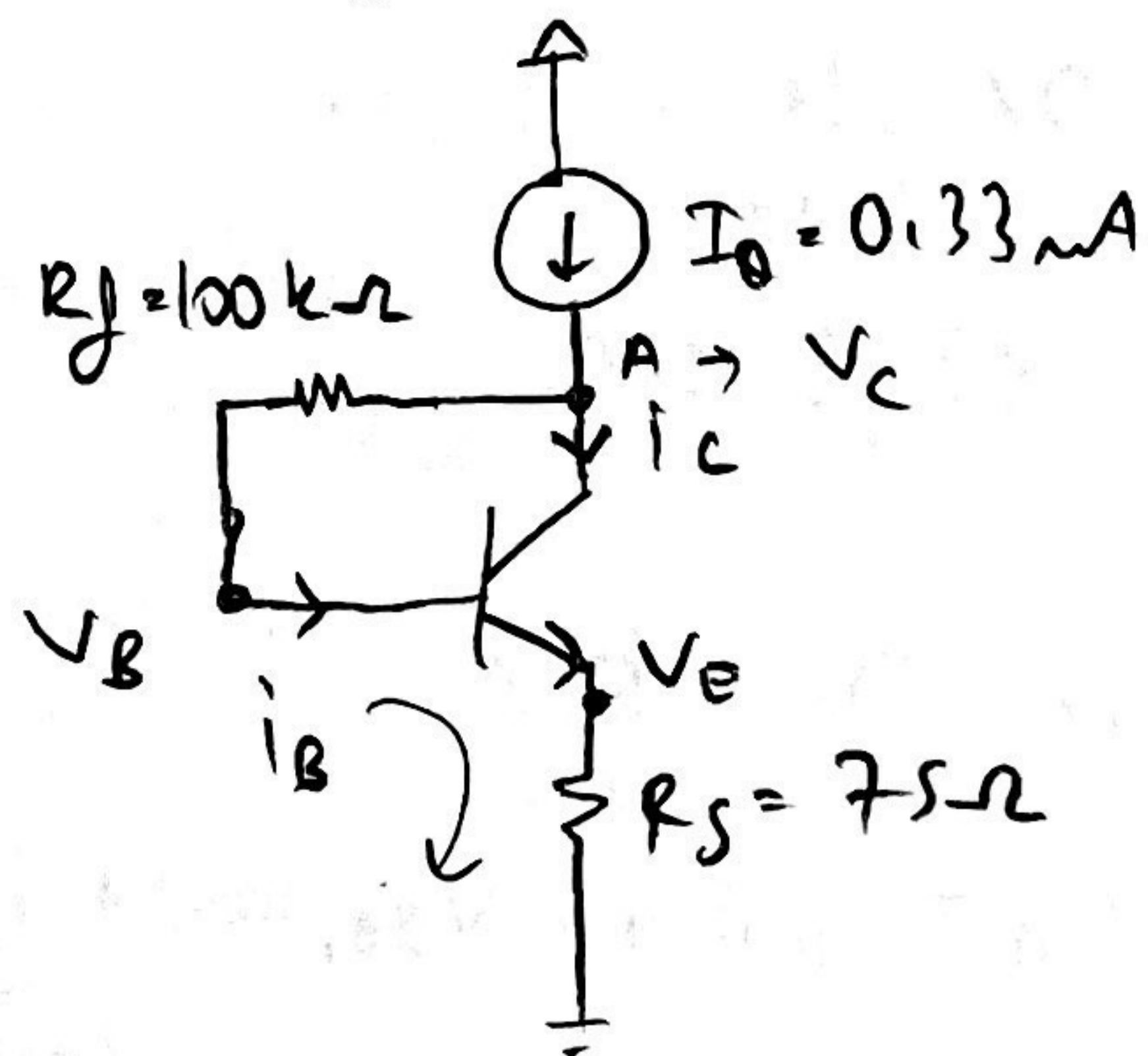② a) DC analysis: Kill  $U_S$ , open circuit caps.



Assume F.A:

$$KCL @ A: I_0 = i_C + i_B = (\beta + 1) i_B$$

$$\Rightarrow i_B = \frac{0.33}{101} = 3.27 \mu A$$

$$i_C = \beta i_B = 0.327 \text{ mA}$$

$$i_E = (\beta + 1) i_B = 0.33 \text{ mA}$$

Note that  $V_C - V_B = i_B R_f = 0.327 \text{ V} \Rightarrow V_C > V_B \Rightarrow \text{BC junction OFF}$   
 $\Rightarrow Q_1$  in F.A as long as ON.


$$\text{Check: } V_B = i_E R_s + V_{BE(\text{ON})} = (0.33 \text{ mA})(75 \Omega) + 0.7 \text{ V} = 0.724 \text{ V}$$

$$V_E = 0.0247 \text{ V} (R_s, i_0)$$

$$V_C = V_B + i_B \cdot R_f = V_B + 0.327 \text{ V} = 1.05 \text{ V}$$

$$\Rightarrow V_{CE} = V_C - V_E = 1.027 \text{ V} > V_{CO(\text{SAT})} = 0.2 \text{ V} \Rightarrow \text{in F.A} \checkmark$$

b) S.S model:

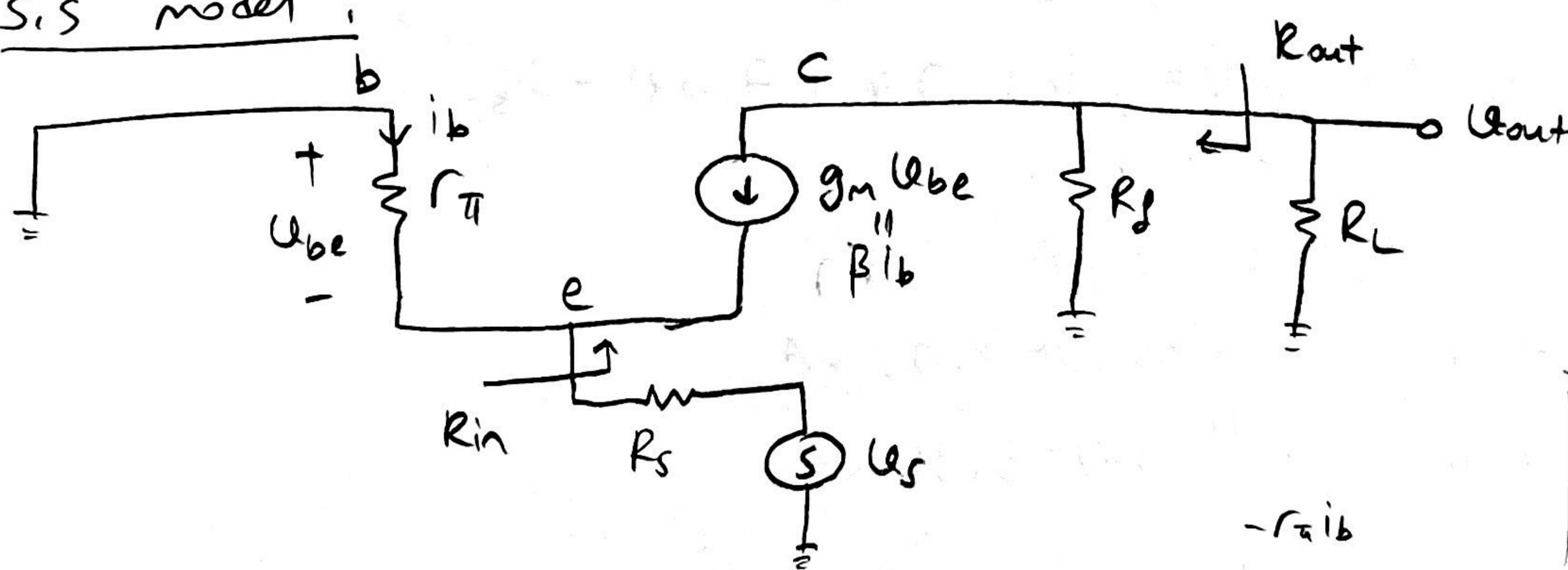

$$r_\pi = \frac{26 \text{ mV}}{3.27 \mu \text{A}} = 7.95 \text{ k}\Omega$$

$$g_m = \frac{\beta}{r_\pi} = 12.58 \text{ mA/V}$$


$$U_{out} = -\beta i_b (R_f \parallel R_L), \quad KCL @ e: i_b + \beta i_b = \frac{(U_e - U_s)}{R_s}$$

$$\text{and } U_e = -U_{be} \text{ since } U_b = 0 \Rightarrow U_e = -r_\pi \cdot i_b$$

$$\Rightarrow U_s = -(\beta + 1) R_s i_b + r_\pi i_b$$

$$\Rightarrow A_{le} = \frac{U_{out}}{U_s} = \frac{-\beta (R_f \parallel R_L)}{r_\pi + (\beta + 1) R_s}$$

To find  $R_{in}$ :

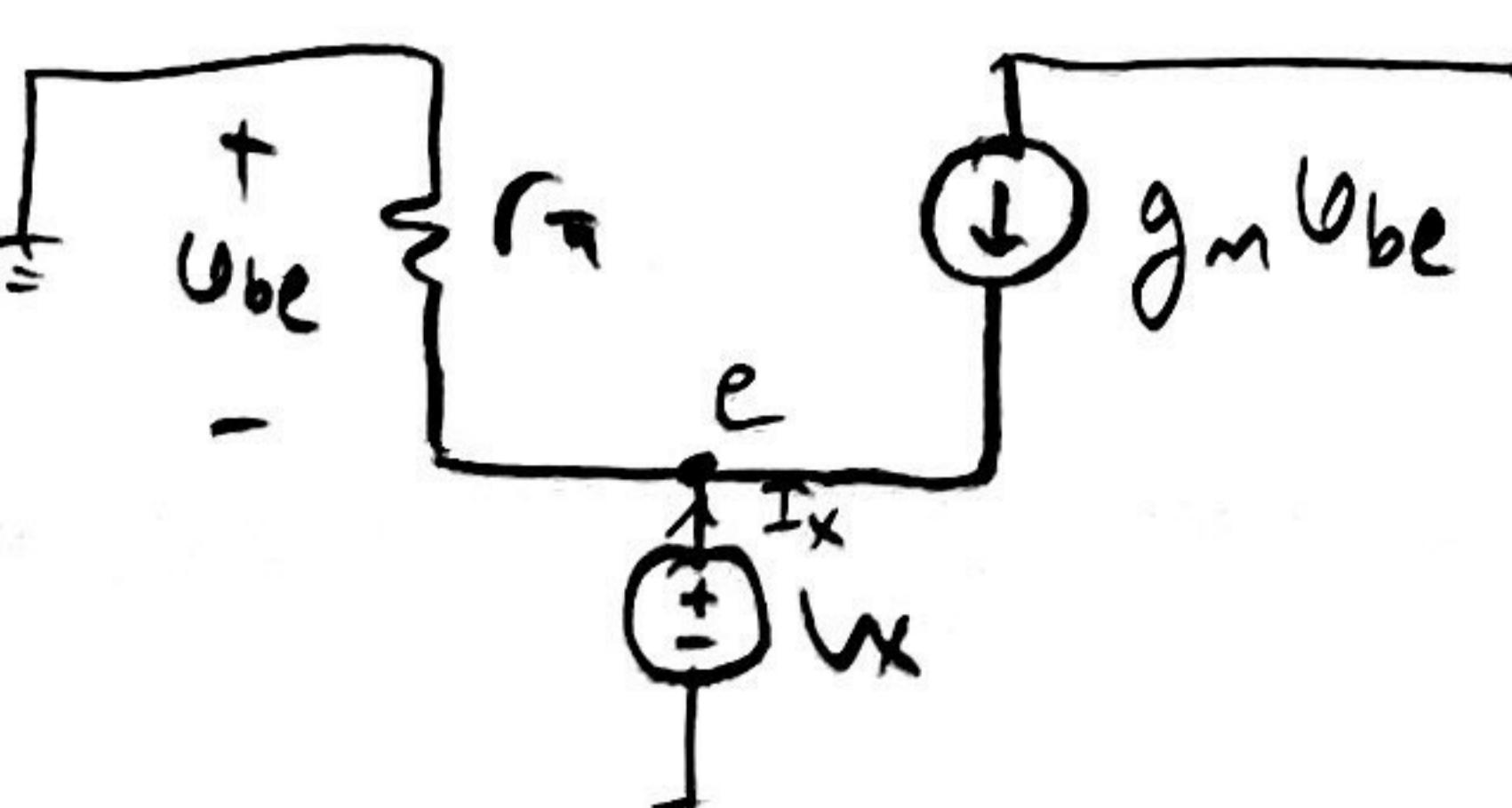

$$R_{in} = 7.95 \parallel 0.0795 = 78 \Omega$$


$$V_x = U_e, \quad U_{be} = -U_e \text{ since } U_b = 0$$

$$KCL @ e: I_x = -g_m U_{be} + \frac{U_e}{r_\pi}$$

$$\Rightarrow I_x = U_x \left( g_m + \frac{1}{r_\pi} \right)$$

$$\Rightarrow R_{in} = \frac{U_x}{I_x} = r_\pi \parallel \frac{1}{g_m}$$

To find Rout: Kill Lin:

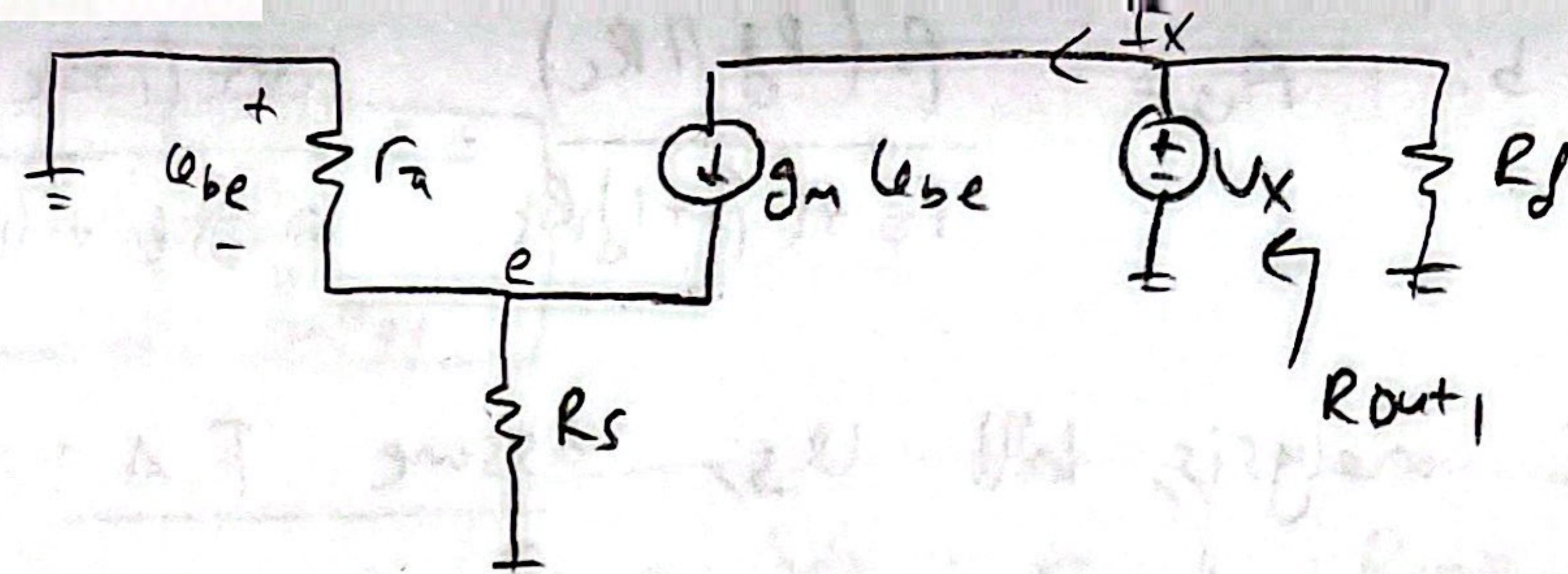

$$U_{be} = -U_e \text{ since } U_b = 0$$

$$I_x = g_m U_{be} = -g_m U_e$$


$$\text{KCL at e: } \frac{U_e}{R_s} + \frac{U_e}{r_a} = g_m U_{be} \Rightarrow U_e \left( g_m + \frac{1}{R_s} + \frac{1}{r_a} \right) = 0$$

$$\Rightarrow U_e = 0 \text{ since } g_m + \frac{1}{R_s} + \frac{1}{r_a} \neq 0.$$

$$\Rightarrow I_x = \infty \Rightarrow \boxed{R_{out,1} = \frac{V_x}{I_x} = \infty}$$

$$\Rightarrow \boxed{R_{out} = R_f // R_{out,1} = R_f = 100 \text{ k}\Omega}$$

c) With  $r_o$ :

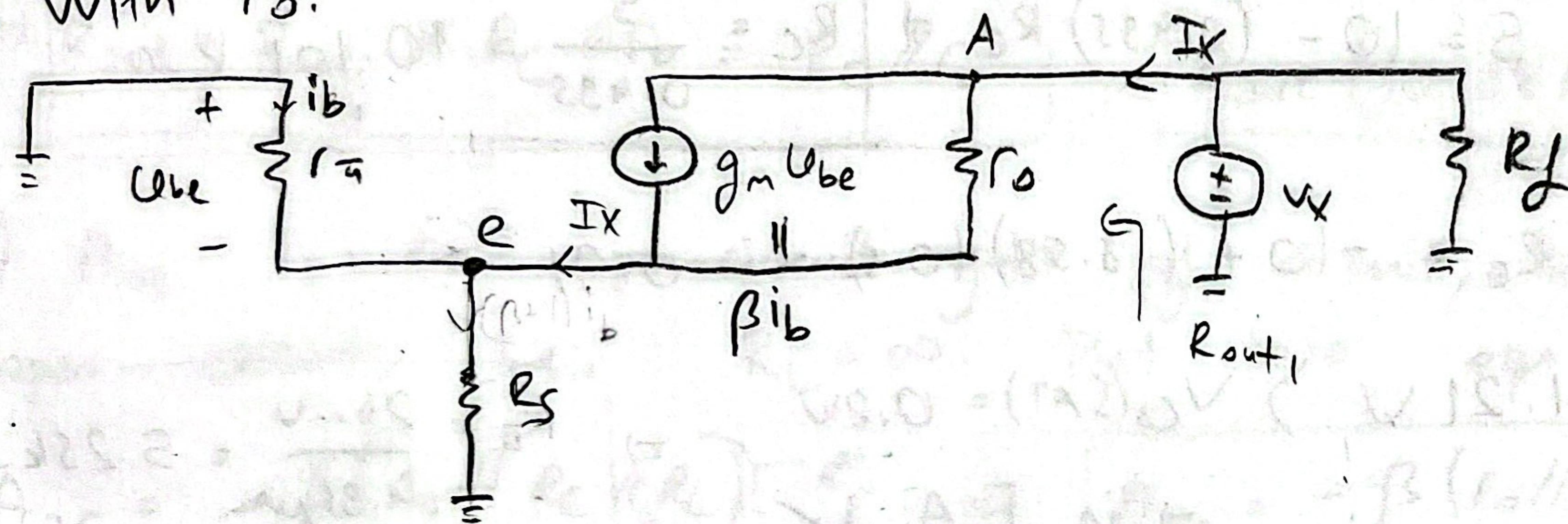

$$\text{KVL: } V_x = (I_x - g_m U_{be}) r_o + I_x (R_s // r_a)$$

$$\text{KCL at e and } U_{be} = -U_e \text{ since } U_b = 0, \quad U_e = I_x (R_s // r_a)$$

$$\Rightarrow V_x = (I_x + g_m I_x (R_s // r_a)) r_o + I_x (R_s // r_a)$$

$$\Rightarrow R_{out,1} = \frac{V_x}{I_x} = (1 + g_m (R_s // r_a)) r_o + (R_s // r_a)$$

$$\text{and } \boxed{R_{out} = R_{out,1} // R_f = [(1 + g_m (R_s // r_a)) r_o + (R_s // r_a)] // R_f}$$

$$\Rightarrow \boxed{R_{out} = 65.93 \text{ k}\Omega}$$

$$d) \text{ in part b: } A_{v2} = \frac{\beta (R_f // R_L)}{r_a + (\beta + 1)R_S} = \frac{100 (100k // 1.5k)}{7.95k + (10)(75\mu A)} \approx 9.52 \frac{V}{V}$$

③ a) in DC analysis, kill  $U_S$ , assume F.A:

$$\underline{i_E = 0.5mA} \Rightarrow i_B = \frac{i_E}{\beta + 1} = \frac{0.5}{101} = 4.95 \mu A$$

$$\text{KVL: } i_B R_S + V_{BE}(\text{ON}) + i_E R_E - 10V = 0$$

$$\Rightarrow (0.0049)(2.5) + 0.7 + (0.5)R_E = 10 \Rightarrow R_E = \frac{10 - 0.7 - i_B R_S}{i_E}$$

$$\Rightarrow \boxed{R_E = 18.58 k\Omega}$$

$$b) i_C = \beta i_B = 0.495mA$$

$$V_C = V_{CC} - i_C R_C \Rightarrow 5 = 10 - (0.495) R_C \Rightarrow \boxed{R_C = \frac{5}{0.495} = 10.101 k\Omega}$$

$$\text{Check: } V_E = -10 + i_E R_E = -10 + (18.58)(0.5) = -0.71$$


$$V_{CE} = \underbrace{V_C}_{0.5V} - \underbrace{V_E}_{-0.71V} = 1.21V \rightarrow V_{CE}(\text{SAT}) = 0.2V$$

in F.A

$$\Rightarrow r_\pi = \frac{26mV}{4.95\mu A} = 5.25k\Omega$$

$$g_m = \frac{\beta}{r_\pi} = 19.04 \mu A/V$$

c) S.S model:

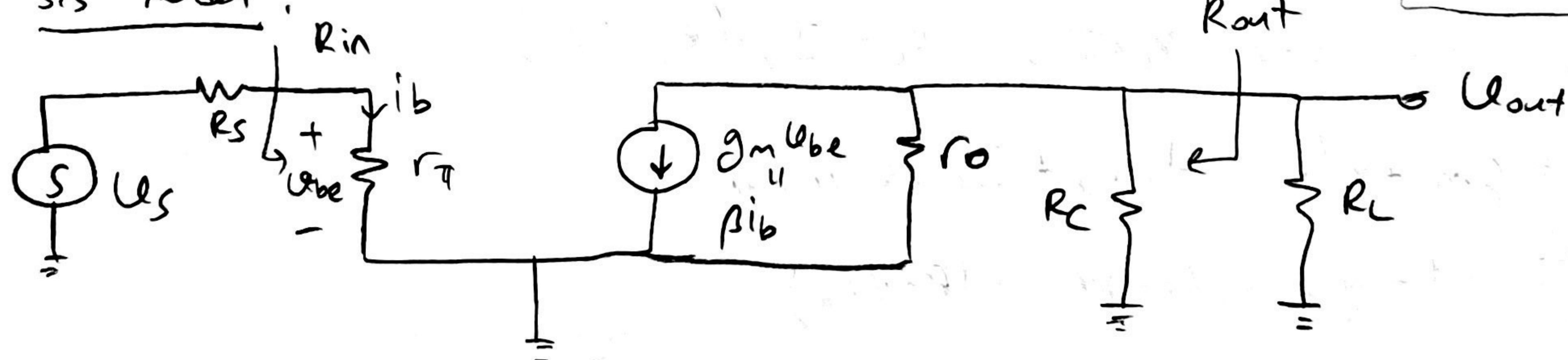


$$U_{be} = U_S \cdot \frac{r_\pi}{r_\pi + R_S} \quad (\text{voltage div.}) \quad \text{and} \quad U_{out} = -g_m (r_o // R_C // R_L) \cdot U_{be}$$

$$\Rightarrow A_{v2} = \frac{U_{out}}{U_S} = -\frac{r_\pi}{r_\pi + R_S} g_m (r_o // R_C // R_L) = -\frac{\beta (r_o // R_C // R_L)}{r_\pi + R_S}$$


$$A_{v2} = -\frac{100 \cdot (200k // 10.101k // 10k)}{5.25k + 2.5k} = -63.25 \frac{V}{V}$$

d) Find  $R_{in}$ :

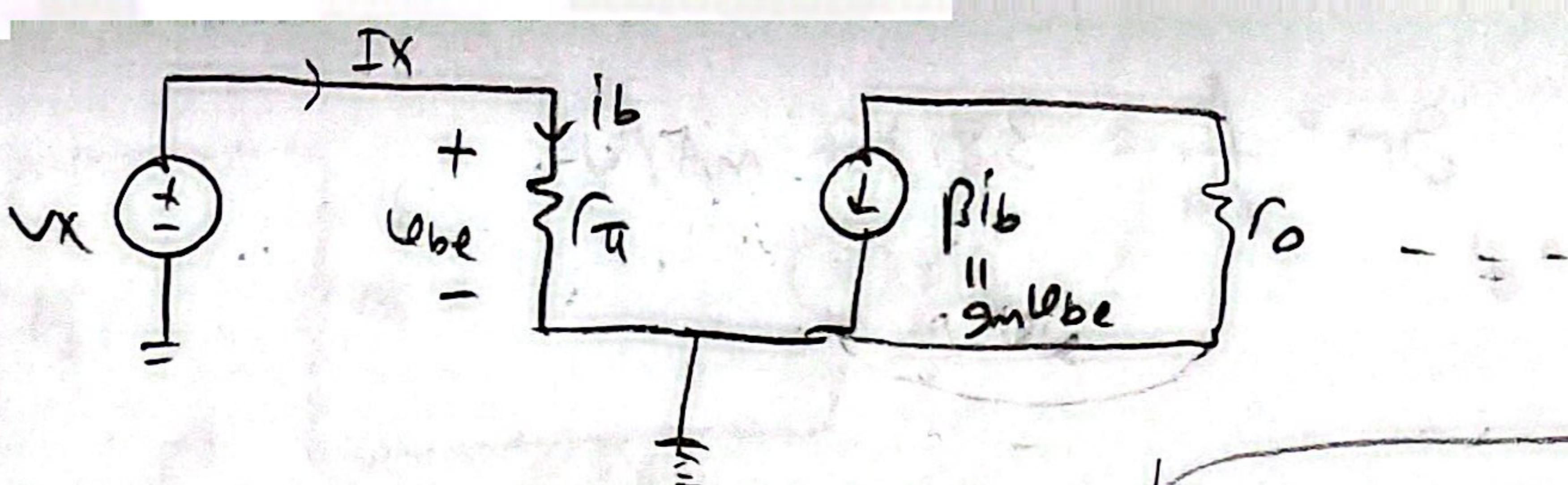

$$I_x = i_b \text{ and } V_x = V_{be} = i_b \cdot r_\pi \Rightarrow R_{in} = \frac{V_x}{I_x} = r_\pi \quad R_{in} = 5.25k\Omega$$

Find  $R_{out}$ : Kill  $V_{in}$

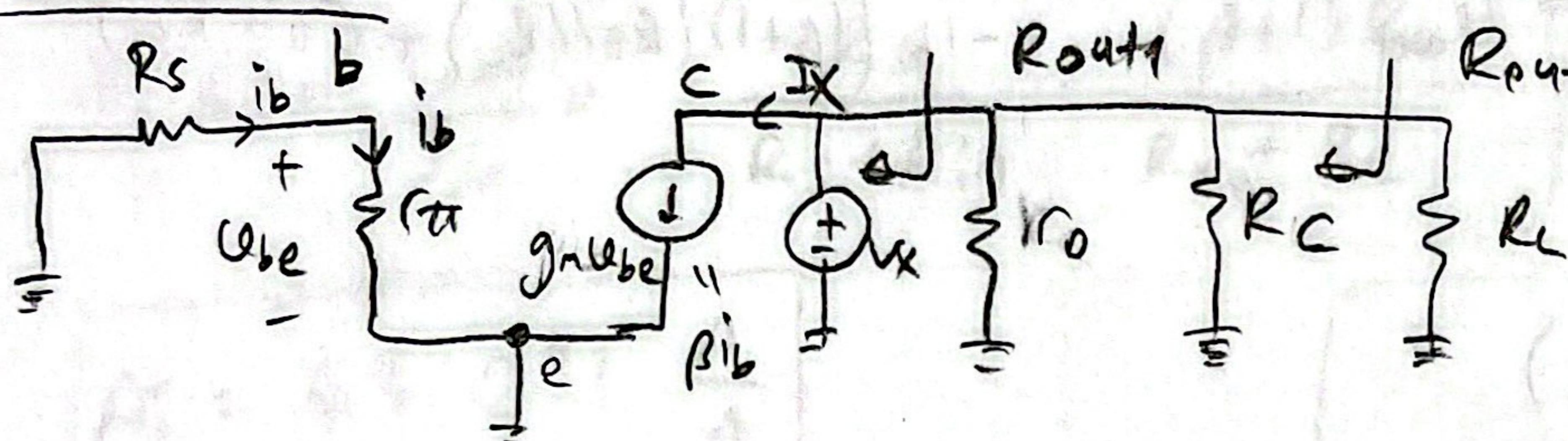

Note that since  $V_{ce} = 0$

$$V_b = -R_s i_b = r_\pi i_b \Rightarrow i_b = 0 \text{ since } R_s + r_\pi \neq 0$$

$$\Rightarrow I_x = \beta i_b = 0, R_{out} = \frac{V_x}{I_x} = \infty$$

$$\Rightarrow R_{out} = R_{out_i} \parallel R_C \parallel R_o = R_C \parallel R_o$$

$$R_{out} = (10.10k \parallel 200k) = 9.61k\Omega$$


e)  $A_{oc}$  is the open-circuit gain of circuit, so we have set  $R_L$  to open circuit, i.e.  $R_L = \infty$ . Put into eqn. found in pt. c:

$$A_{oc} = -\frac{\beta (r_o \parallel R_C \parallel R_L)}{r_\pi + R_s} \Rightarrow$$

$$A_{oc} = -\frac{\beta (r_o \parallel R_C)}{r_\pi + R_s}$$

$$\Rightarrow A_{oc} = -124.058$$

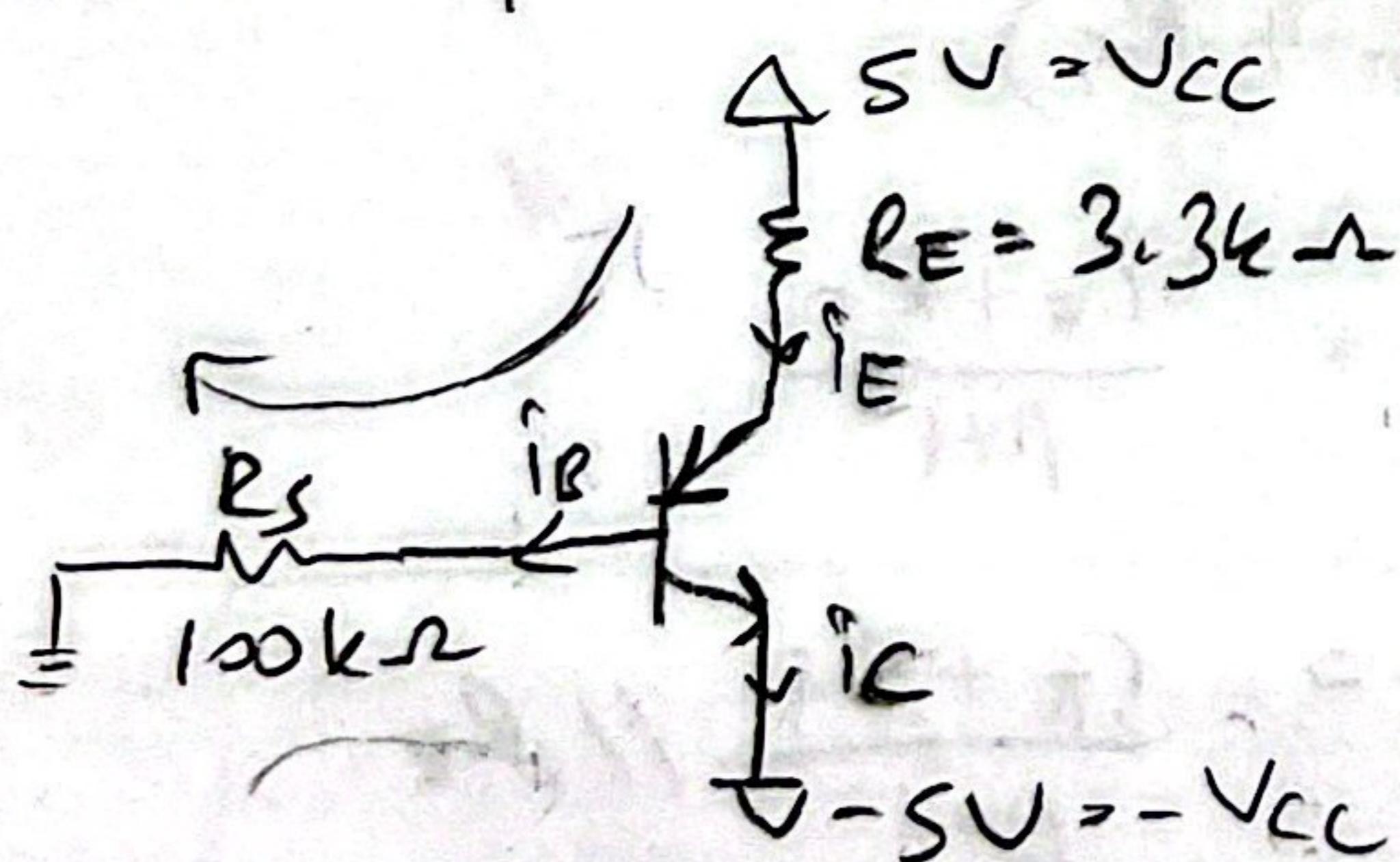④ a) DC comp. is zero  $\Rightarrow$  kill  $V_S$ , open circ. cap.s:



Assume F.A.:

$$\text{KVL: } i_E R_E + V_{EB(\text{on})} + i_B R_S = 5V$$

$$(\beta+1)i_B = 5 - 0.7$$

$$i_B = \frac{5 - 0.7}{101(3.3) + 100} = 9.92 \text{ mA}$$

$$i_E = (\beta+1) i_B = 1.00 \text{ mA}$$


$$\text{Check: } V_E = 5 - i_E R_E = 5 - 3.3 = 1.7V$$

$$V_{EC} = V_E - V_C = 6.7V > V_{EC(\text{SAT})} = 0.2V$$

$\Rightarrow$  in F.A. ✓

$$b) r_{\pi} = \frac{26mV}{9.92mA} = 2.62k\Omega, g_m = \frac{\beta}{r_a} = 38.17 \text{ mA/V}$$

S.S model:

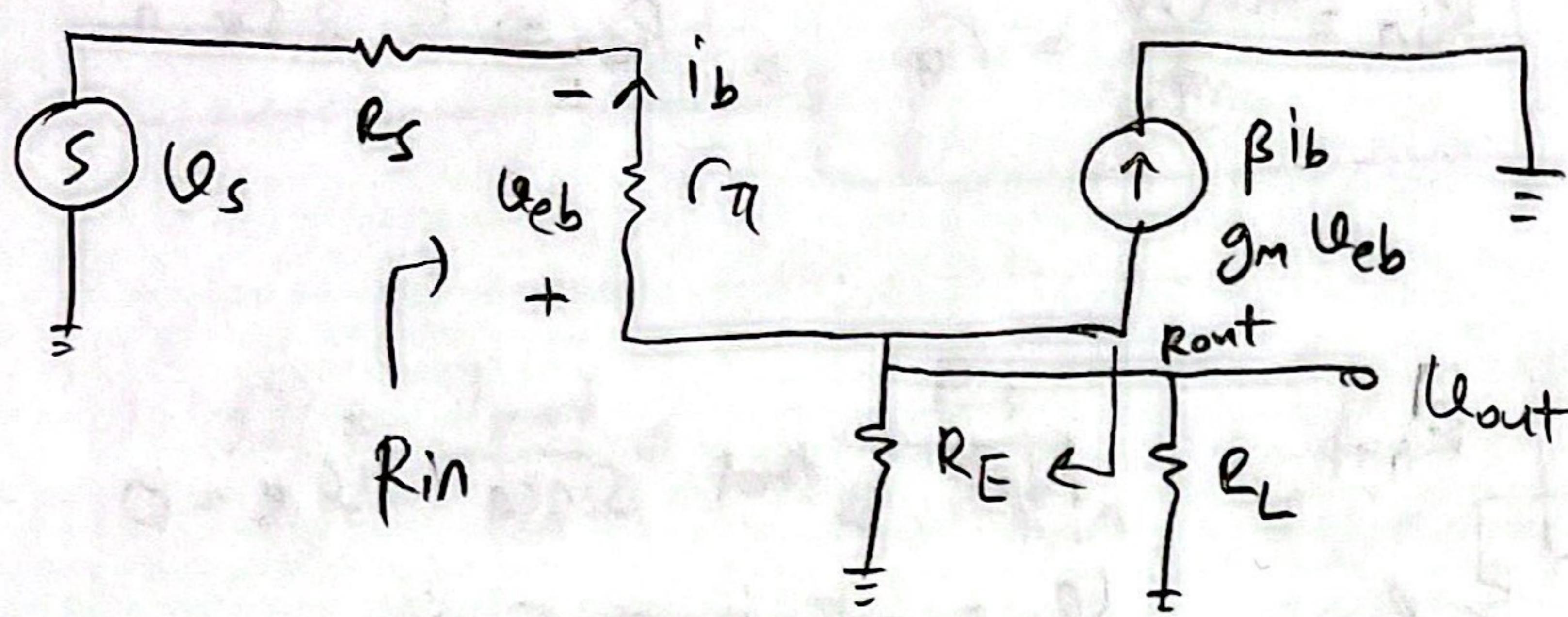


$$v_{out} = -(\beta + 1) i_b (R_E // R_L)$$

$$v_{os} = (v_{out} + v_{eb} + i_b R_s)$$

$$= -i_b ((\beta + 1)(R_E // R_L) + r_{\pi} + R_s)$$

$$\Rightarrow A_{vE} = \frac{v_{out}}{v_{os}} = \frac{(\beta + 1)(R_E // R_L)}{(\beta + 1)(R_E // R_L) + r_{\pi} + R_s}$$

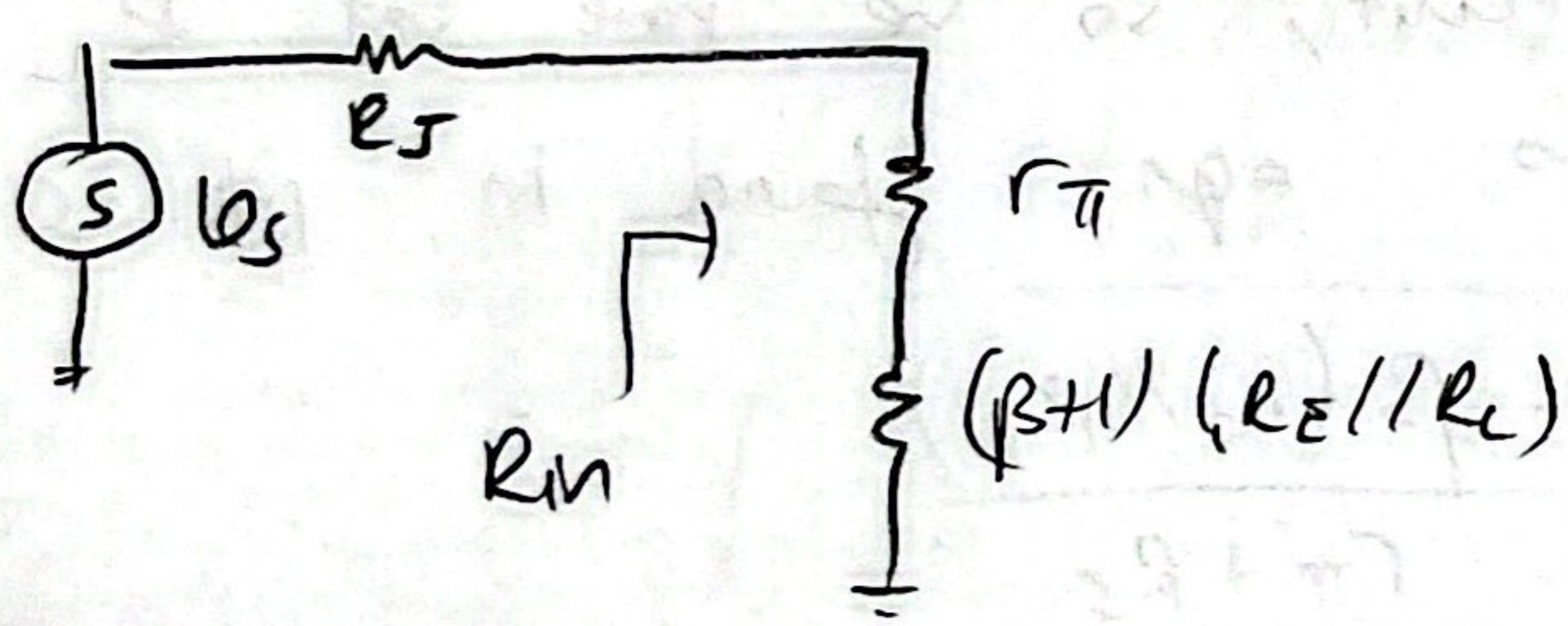
To find \$R\_{in}\$: we can move \$R\_E\$ and \$R\_L\$ directly to the base side as \$(\beta + 1)(R\_E // R\_L)\$ since the current over them is \$(\beta + 1)i\_b\$:



$$R_{in} = r_{\pi} + (\beta + 1)(R_E // R_L)$$

$$R_{in} = 80.13 k\Omega$$

To find \$R\_{out}\$; Kill \$v\_{in}\$

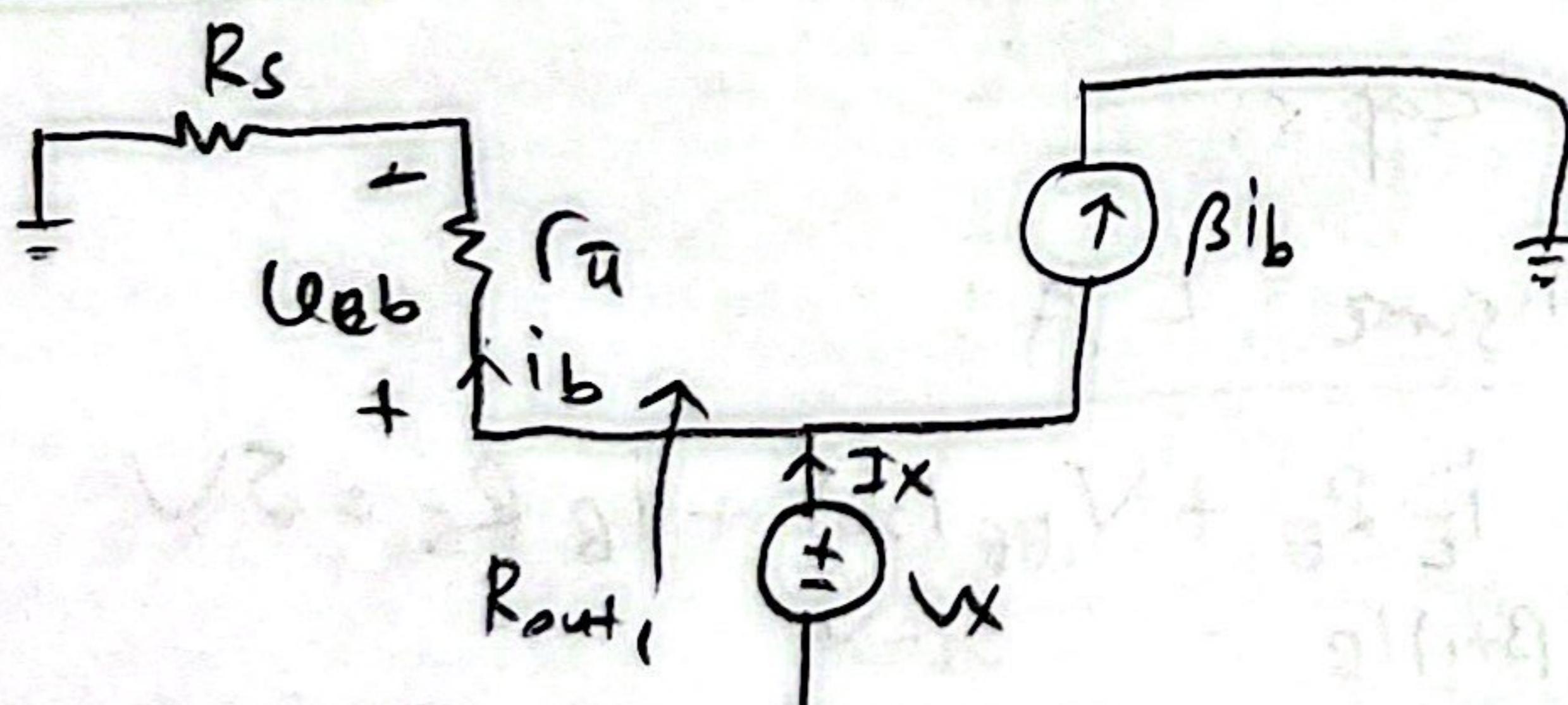

$$I_x = (\beta + 1) i_b$$

$$V_x = i_b (r_{\pi} + R_s)$$


$$\Rightarrow R_{out,1} = \frac{V_x}{I_x} = \frac{r_{\pi} + R_s}{\beta + 1}$$

$$\Rightarrow R_{out} = R_{out,1} // R_E = \frac{r_{\pi} + R_s}{\beta + 1} // R_E$$

$$\Rightarrow R_{out} = 0.77 k\Omega$$

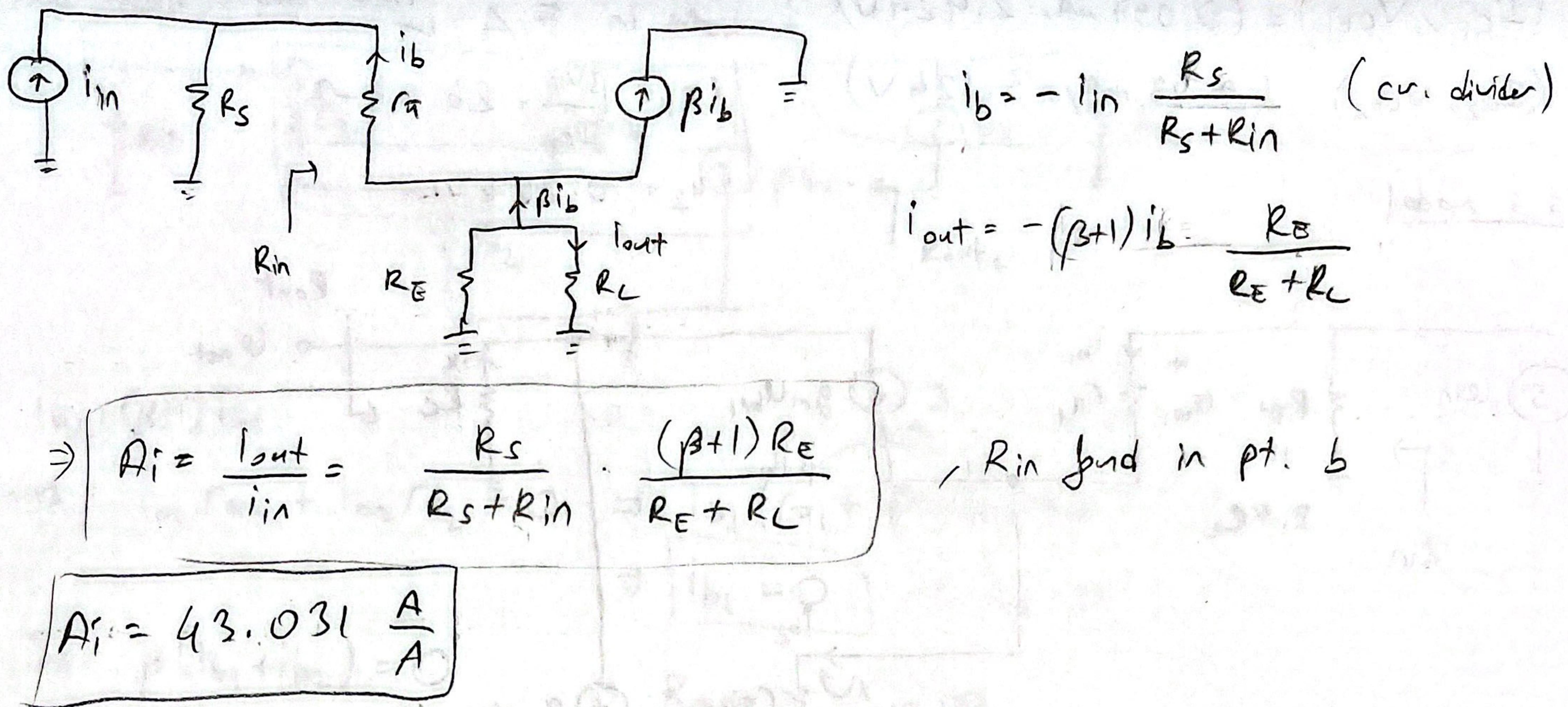
c) From prev. part:

$$A_{vE} = \frac{v_{out}}{v_{in}} = \frac{(\beta + 1)(R_E // R_L)}{(\beta + 1)(R_E // R_L) + r_{\pi} + R_s} = 0.43 \frac{V}{V}$$



⑤ a) Theor. eq. for Q<sub>1</sub>:  $V_{TH} = 20V, \frac{R_2}{R_1 + R_2} = 20, \frac{17}{17+83} = 3.4V$
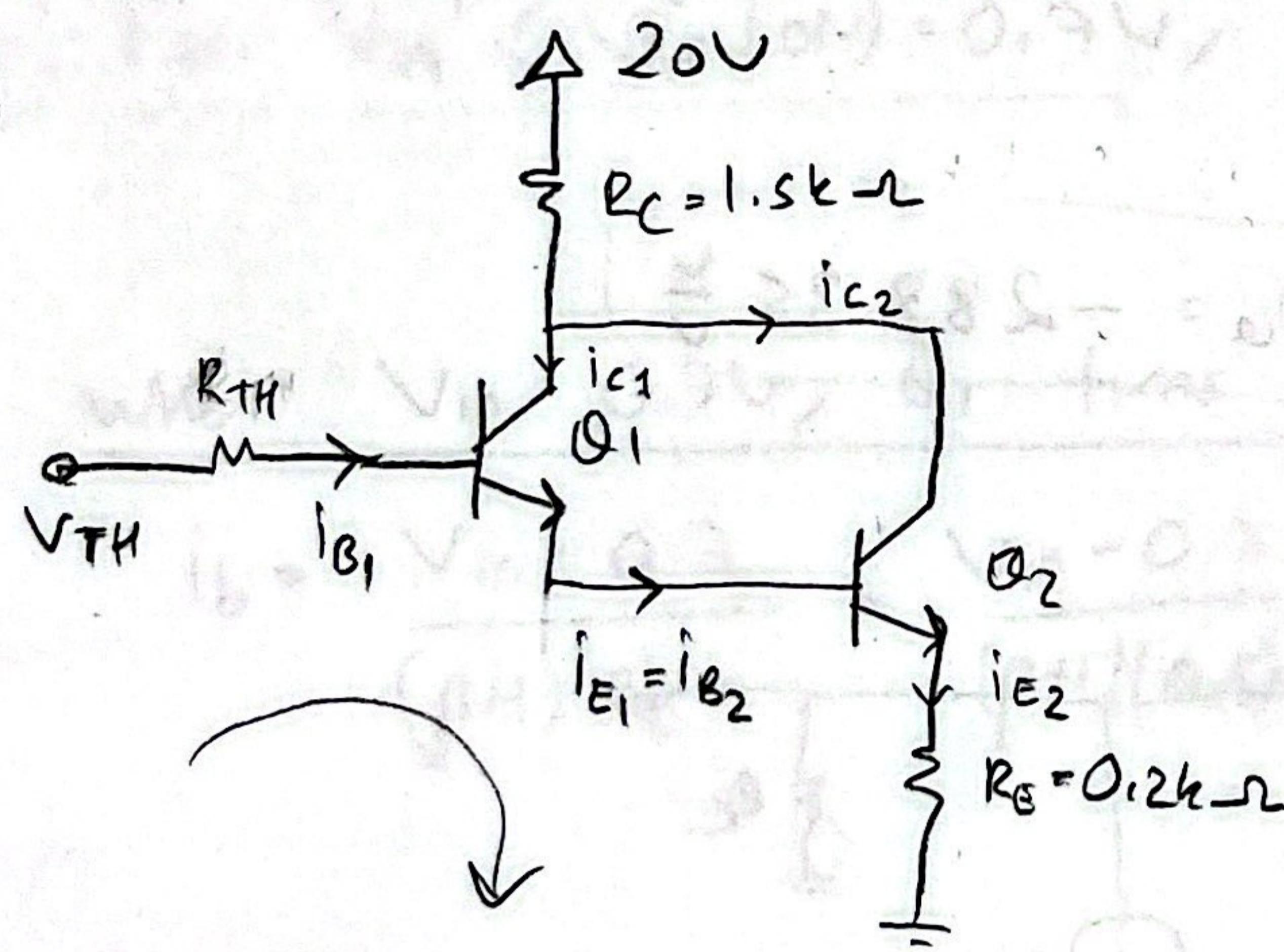
$$R_{TH} = 83k \parallel 17k = 14.11 k\Omega$$



Assume Q<sub>1</sub>, Q<sub>2</sub> F.A:

$$\text{KVL: } V_{TH} = R_{TH} i_{B1} + V_{BE1}(\text{ON}) + V_{BE2}(\text{ON}) + i_{E2} \cdot R_E$$

$$\text{and since } i_{E1} = i_{B2} = (\beta + 1) i_{B1}$$

$$\Rightarrow i_{E2} = (\beta + 1) i_{B2} = (\beta + 1)^2 i_{B1}$$

$$\Rightarrow | i_{B1} = \frac{3.4 - 2(0.7)}{14.11 + 101^2(0.2)} = 0.97 \mu A |$$

$$\Rightarrow | i_{E1} = i_{B2} = 0.098 \mu A |, | i_{C1} = 0.097 \mu A |$$

$$\Rightarrow | i_{E2} = 9.93 \mu A |, | i_{C2} = 9.83 \mu A |$$

$$\Rightarrow V_{C1} = V_{C2} \text{ and } V_{C1} = 20 - (i_{C1} + i_{C2}) R_C = 20 - (9.83 + 0.097) 1.5 = 5.11V$$

$$V_{E2} = i_{E2} R_E = 1.986V$$

$$\Rightarrow V_{CE2} = V_{C2} - V_{E2} = 3.124V > V_{CE}(\text{SAT}) = 0.2V \Rightarrow \underline{\underline{Q_2 \text{ in F.A}}} \checkmark$$

$$\Rightarrow V_{E1} = V_{BE}(\text{ON}) + V_{E2} = 2.686 \quad \Rightarrow \quad V_{CE1} = V_{C1} - V_{E1} = 2.424V > V_{CE}(\text{SAT}) = 0.2V$$


0.7 since Q<sub>2</sub> F.A

$$\Rightarrow \underline{\underline{Q_1 \text{ in f.a}}} \checkmark$$

$$\Rightarrow \begin{cases} (I_{C_1}, V_{CE_1}) = (0.097 \text{ mA}, 2.424 \text{ V}) \\ (I_{C_2}, V_{CE_2}) = (9.83 \text{ mA}, 3.124 \text{ V}) \end{cases}$$

both in F.A ✓

b) s.s model:

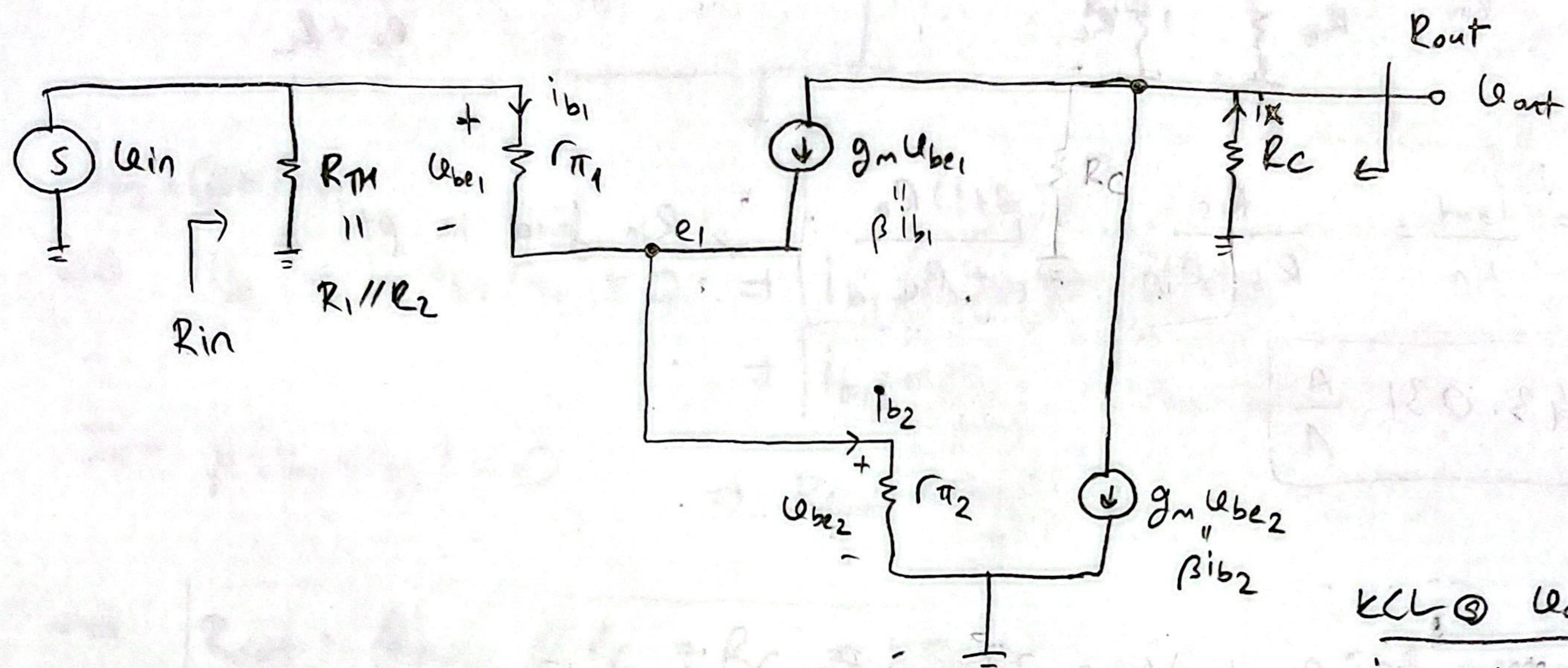


$$KCL @ e_1: i_{b2} = (\beta + 1) i_{b1}$$

$$KVL: u_{in} = r_{\pi_1} i_{b1} + r_{\pi_2} i_{b2} = (r_{\pi_1} + (\beta + 1) r_{\pi_2}) i_{b1} = \beta i_{b1} (\beta + 2)$$

$$u_{out} = -R_C i_x = -\beta R_C (\beta + 2) \cdot i_{b1}$$

$$\Rightarrow A_u = \frac{u_{out}}{u_{in}} = \frac{-\beta (\beta + 2) R_C}{r_{\pi_1} + (\beta + 1) r_{\pi_2}} \Rightarrow A_u = -288.35 \frac{V}{V}$$

c) Find  $R_{in}$ :

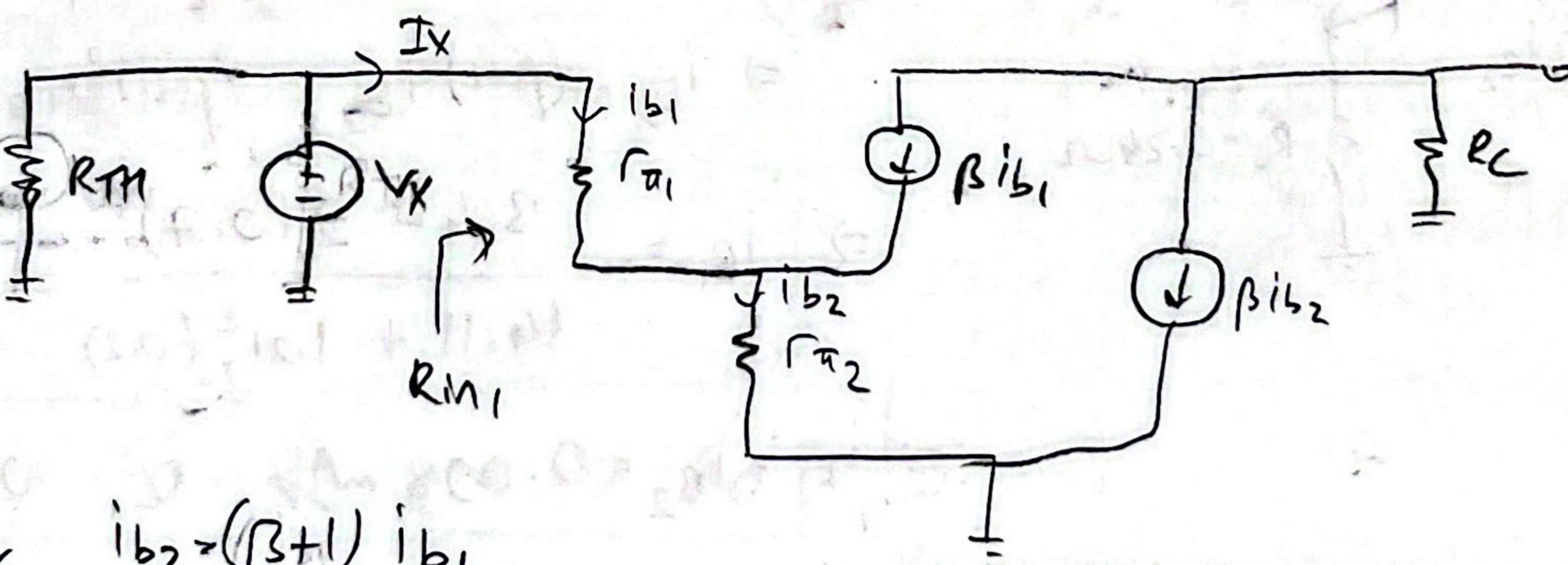

$$I_x = i_{b1}, \quad i_{b2} = (\beta + 1) i_{b1} = (\beta + 1) I_x$$


$$\Rightarrow V_x = I_x r_{\pi_1} + (\beta + 1) I_x r_{\pi_2} \text{ from KVL} \Rightarrow R_{in_1} = \frac{V_x}{I_x} = r_{\pi_1} + (\beta + 1) r_{\pi_2}$$

and

$$R_{in} = R_{in_1} // R_m = (r_{\pi_1} + (\beta + 1) r_{\pi_2}) // R_m$$

$$\Rightarrow R_{in} = 11.146 \text{ k}\Omega$$

d) Find Rout,  $V_{in}$

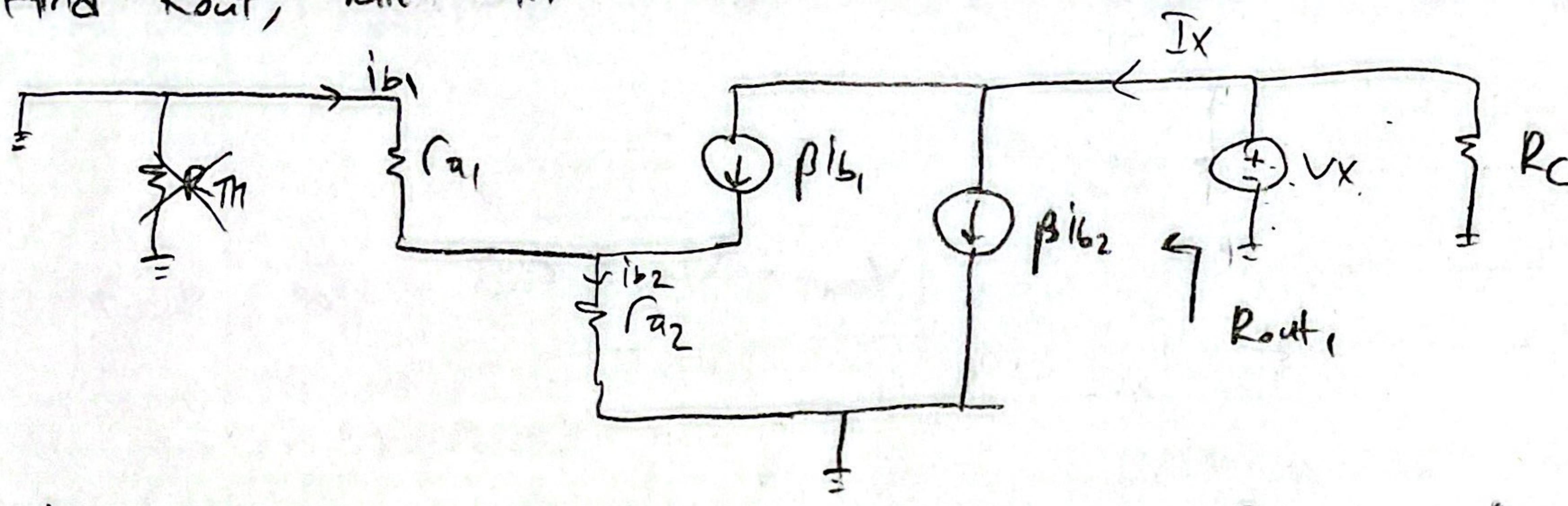

$$i_{b2} = (\beta+1) i_{b1}$$

$$\text{and } i_{b1} r_{a_1} + i_{b2} r_{a_2} = 0 \Rightarrow i_{b1} (r_{a_1} + (\beta+1)r_{a_2}) = 0$$

$$\Rightarrow i_{b1} = 0 \Rightarrow i_{b2} = 0$$

$$I_x = \beta(i_{b1} + i_{b2}) = 0 \Rightarrow \text{Rout}_1 = \frac{V_x}{I_x} = \infty$$

$$\text{and } \boxed{\text{Rout} = \frac{\text{Rout}_1 // R_C}{\infty} = R_C = 1.5k\Omega}$$

⑥ For  $V_{in} < V_{BE(on)} = 0.7V$ ,  $Q_1$  is OFF  $\Rightarrow i_B = i_C = i_E = 0$   
 $\Rightarrow V_{out} = 10V$

When  $V_{in} = 0.7V$ ,  $Q_1$  turns ON. With small  $i_B$  currents having value:

$$i_B = \frac{V_{in} - 0.7}{(\beta+1) R_E} = \frac{V_{in} - 0.7}{(\beta+1)(0.5)}$$

(by KVL), since  $V_{in}$  is close to 0.7  
 $\Rightarrow$  small  $i_C$  current  
 $\Rightarrow$  in F.A mode due to small  $V_E$  and large  $V_C$   
where  $V_C = 10 - R_C i_C$

$$\text{and } V_{out} = 10 - R_C i_C = 10 - R_C \beta i_B$$

$$= 10 - 2\beta \cdot \frac{(V_{in} - 0.7)}{(\beta+1)(0.5)}$$

while in F.A.

$Q_1$  is in F.A until BC turns ON, and  $V_{BC(on)} = 0.5V$

$\Rightarrow$  When  $V_{in} - V_{out} = 0.5$ ,  $Q_1$  goes to SAT mode.


$$\Rightarrow V_{in} - V_{out} = V_{in} - \left( 10 - 2 \left( \frac{\beta}{\beta+1} \right) \frac{V_{in} - 0.7}{0.5} \right) = V_{in} - (10 - 4V_{in} + 2.8) = 0.5$$

since  $\beta \approx 1$

$$\Rightarrow 5V_{in} = 12.8 + 0.5$$

$$\Rightarrow V_{in} = 2.66V$$

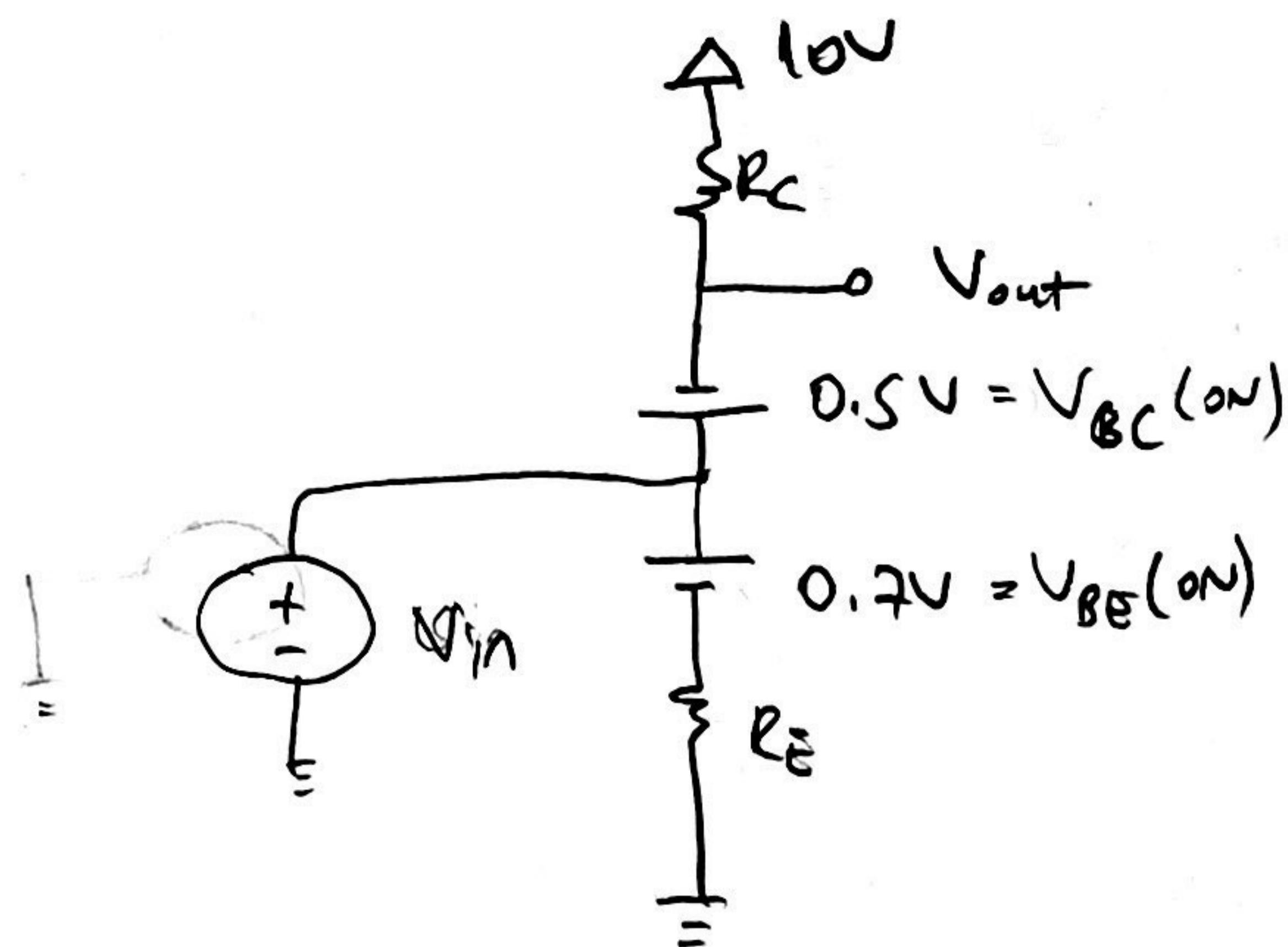After the transistor is in SAT: (both BE, BC on)



$$\Rightarrow V_{out} = V_{in} - 0.5 \quad \text{for } V_{in} > 2.66V$$

$$\Rightarrow V_{out} = \begin{cases} 10V & , V_{in} < 0.7 \\ 10 - 4 \frac{\beta}{\beta+1} (V_{in} - 0.7) & , 0.7 \leq V_{in} \leq 2.66 \\ V_{in} - 0.5 & , V_{in} > 2.66 \end{cases}$$

